

Industrial Automation

(Automação de Processos Industriais)

PLC Programming languages

Ladder Diagram

<http://users.isr.ist.utl.pt/~jag/courses/api1920/api1920.html>

Prof. Paulo Jorge Oliveira, original slides

Prof. José Gaspar, rev. 2019/2020

Syllabus:

Chap. 2 – Introduction to PLCs [2 weeks]

...

Chap. 3 – PLC Programming languages [2 weeks]

Standard languages (IEC-61131-3):

Ladder Diagram; Instruction List, and Structured Text.


Software development resources.

...

Chap. 4 - GRAFCET (*Sequential Function Chart*) [1 week]

PLC Programming languages*
IEC 1131-3 changed to IEC 61131-3

Ladder Diagram

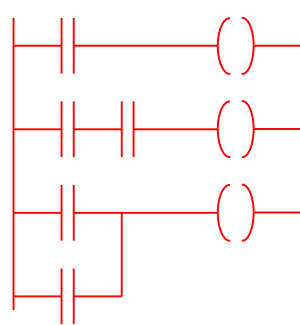

Structured Text


```

If %I1.0 THEN
  %Q2.1 := TRUE
ELSE
  %Q2.2 := FALSE
END_IF
    
```

Instruction List

LD	%M12
AND	%I1.0
ANDN	%I1.1
OR	%M10
ST	%Q2.0

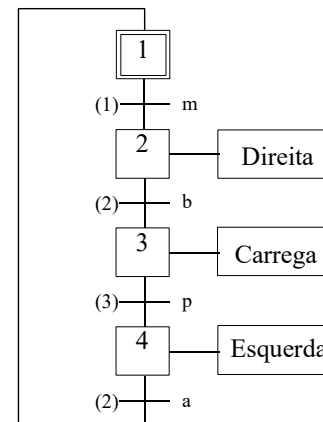***Sequential Function Chart
(GRAFCET)***





* [International Electrotechnical Commission \(IEC\)](http://www.iec.ch)

Ladder diagram

Relay ladder logic, i.e. electromagnetic relay control, was the basis to create a standard programming language.

A **Program** is a series of instructions that directs the PLC to execute actions.

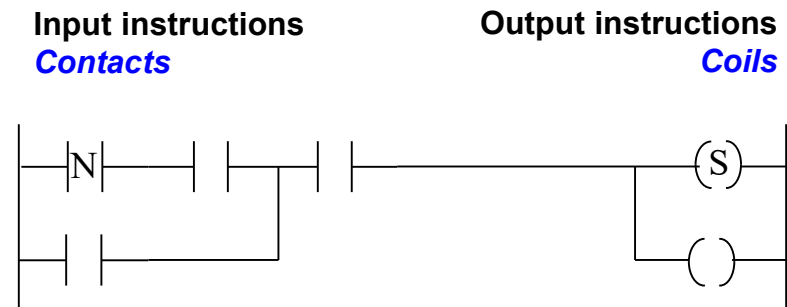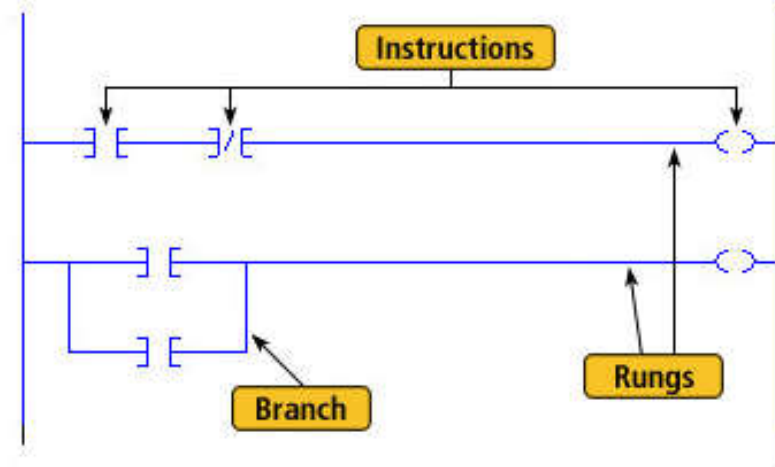Simplest programs are based in **physical addresses** naming **contacts** and **coils** or, in general, the so-called **operands**.




Ladder diagram

Unity Pro dev. environment

0- See: Unity Pro SW > Languages Ref > Programming Language > Ladder Diagram (LD)

1- Double click here to edit / see the hardware configuration

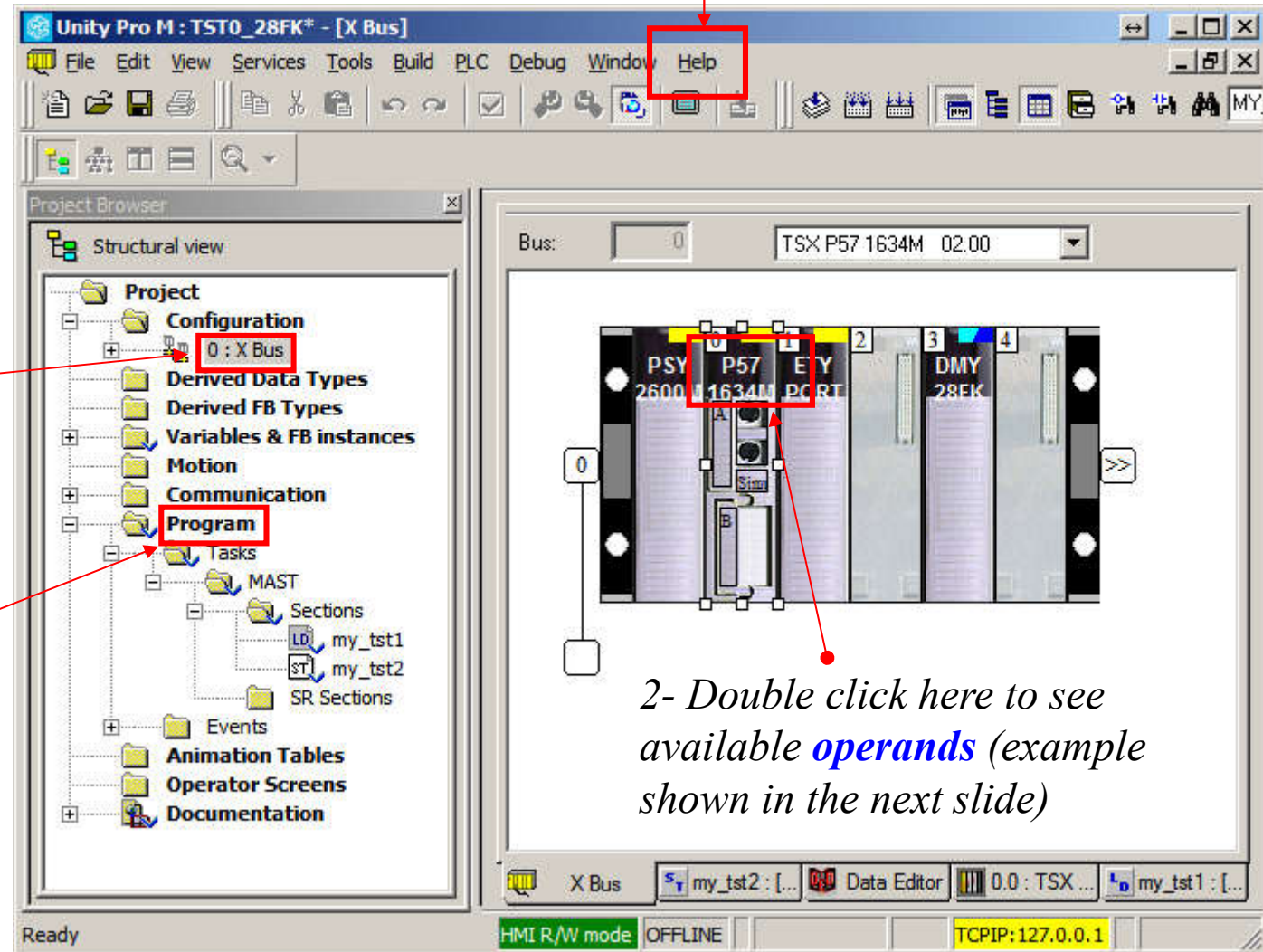3- Programs in Ladder (and other languages) are added here.



2- Double click here to see available operands (example shown in the next slide)

Ladder diagram Types of **operands** in Schneider DMY 28FK:

The screenshot shows the configuration interface for a Schneider DMY 28FK PLC. It is divided into three main sections: CPU objects, I/O Objects, and an Update section.

CPU objects:

- System: %S %SW [Select all]
- Memory: %M %MW %MD %MF %KW %KD %KF [Unselect all]

I/O Objects:

- Channel: %CH
- Configuration: %KW %KD %KF [Select all]
- System: %MW [Unselect all]
- Status: %MW [Unselect all]
- Parameter: %MW %MD %MF
- Command: %MW %MD %MF
- Implicits: %I %IW %ID %IF %IERR
- %Q %QW %QD %QF

Update section:

- Update grid with: addresses, names, types and comments, usages
- Filter on usage

I/O Objects Table:

	Address	Name	Type	Comment
1	%I0.3.0		EBOOL	
2	%I0.3.1		EBOOL	
3	%I0.3.2		EBOOL	
4	%I0.3.3		EBOOL	
5	%I0.3.4		EBOOL	
6	%I0.3.5		EBOOL	
7	%I0.3.6		EBOOL	
8	%I0.3.7		EBOOL	
9	%I0.3.8		EBOOL	
10	%I0.3.9		EBOOL	
11	%I0.3.10		EBOOL	
12	%I0.3.11		EBOOL	
13	%I0.3.12		EBOOL	
14	%I0.3.13		EBOOL	
15	%I0.3.14		EBOOL	
16	%I0.3.15		EBOOL	
17	%Q0.3.16		EBOOL	
18	%Q0.3.17		EBOOL	
19	%Q0.3.18		EBOOL	
20	%Q0.3.19		EBOOL	
21	%Q0.3.20		EBOOL	
22	%Q0.3.21		EBOOL	
23	%Q0.3.22		EBOOL	
24	%Q0.3.23		EBOOL	
25	%Q0.3.24		EBOOL	
26	%Q0.3.25		EBOOL	


Ladder diagram Types of operands:

Bits	Description	Examples	Write access
Immediate values	0 or 1 (False or True)	0	-
Inputs/outputs	<p>These bits are the "logic images" of the electrical states of the inputs/ outputs. They are stored in the data memory and updated each time the task in which they are configured is polled.</p> <p>Note: The unused input/output bits may not be used as internal bits.</p>	%I23.5 %Q51,2	No Yes
Internal	The internal bits are used to store the intermediary states during execution of the program.	%M200	Yes
System	The system bits %S0 to %S127 monitor the correct operation of the PLC and the running of the application program.	%S10	According to i
Function blocks	<p>The function block bits correspond to the outputs of the function blocks or DFB instance. These outputs may be either directly connected or used as an object.</p>	%TM8.Q	No
Word extracts	With the PL7 software it is possible to extract one of the 16 bits of a word object.	%MW10:X5	According to the type of words
Grafcet steps and macro-steps	The Grafcet status bits of the steps, macro-steps and macro-step steps are used to recognize the Grafcet status of step i, of macro-step j or of step i of the macro-step j.	%X21 %X5.9	Yes Yes


Ladder diagram

Basic Instructions


Load

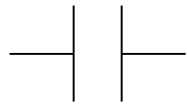

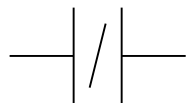
Normally open contact: contact is active (result is 1) when the control bit is 1.



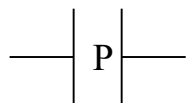
Normally closed contact: contact is active (result is 1) when the control bit is 0.



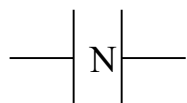Contact in the **rising edge**: contact is active during a scan cycle where the control bit has a rising edge.



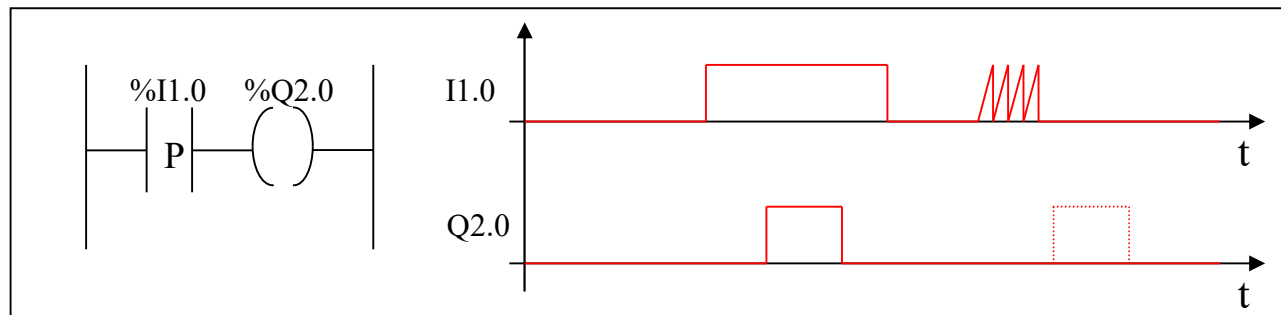Contact in the **falling edge**: contact is active during a scan cycle where the control bit has a falling edge.




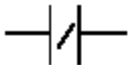
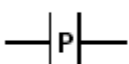
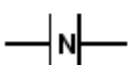
Ladder diagram

Basic Instructions

Load operands


Permitted operands


The following table gives a list of the operands used for these instructions.


Ladder	Instruction list	Structured text	Operands
	LD	:=	%I,%Q,%M,%S,%BLK,%•:Xk, %Xi, (True and False in instruction list or structured text)
	LDN	:=NOT	%I,%Q,%M,%S,%BLK,%•:Xk, %Xi, (True and False in instruction list or structured text)
	LDR	:=RE	%I,%Q,%M
	LDF	:=FE	%I,%Q,%M

Ladder diagram


Basic Instructions

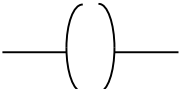Store  The result of the logic function activates the coil.

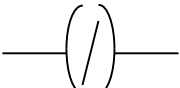 The inverse result of the logic function activates the coil.

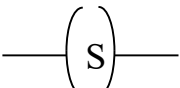 The result of the logic function energizes the relay (sets the latch).

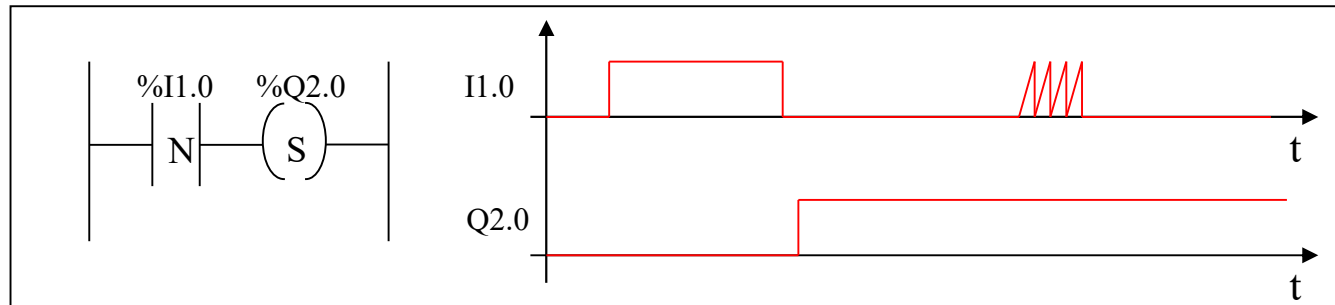 The result of the logic function de-energizes the relay (resets the latch)..







Ladder diagram

Basic Instructions

Store operands

Permitted operands

The following table gives a list of the operands used for these instructions

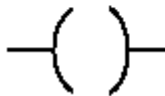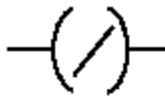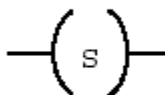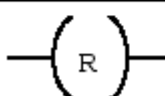Language data	Instruction list	Structured text	Operands
	ST	:=	%I,%Q,%M,%S,%•:Xk
	STN	:=NOT	%I,%Q,%M,%S,%•:Xk
	S	SET	%I,%Q,%M,%S,%•:Xk,%Xi Only in the preliminary processing.
	R	RESET	%I,%Q,%M,%S,%•:Xk,%Xi Only in the preliminary processing.

Ladder diagram

Allen Bradley notation

Relays with *latch* and *unlatch*


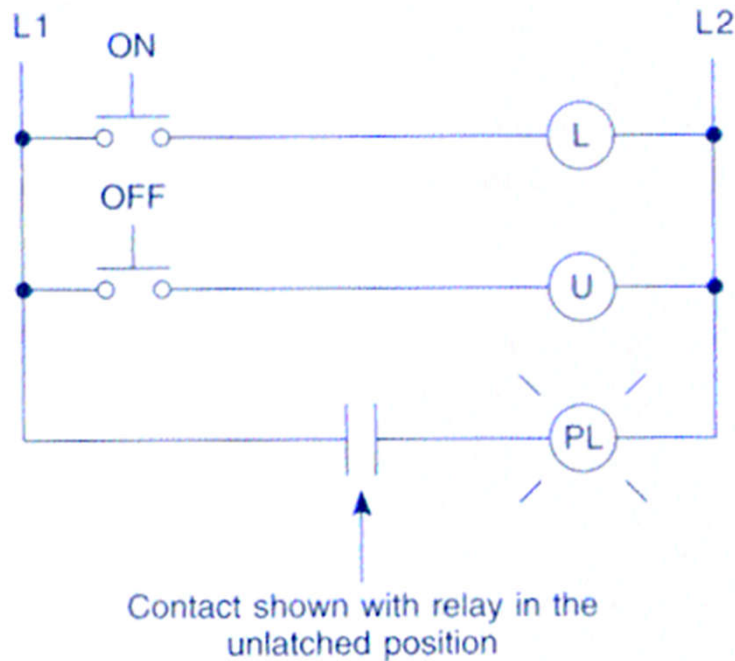



Fig. 6-50

Schematic of electromagnetic latching relay.

Instruction	Symbol	Mnemonic
Output latch	-(L)-	OTL
Output unlatch	-(U)-	OTU

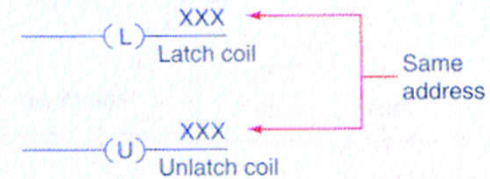

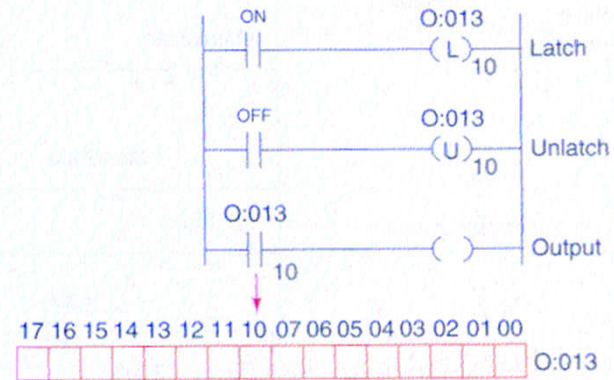(a) Latch and unlatch coils have the same address



(b) Control logic




Fig. 6-51

OUTPUT LATCH and OUTPUT UNLATCH instructions.

Ladder diagram


Relay-type instructions

Example:

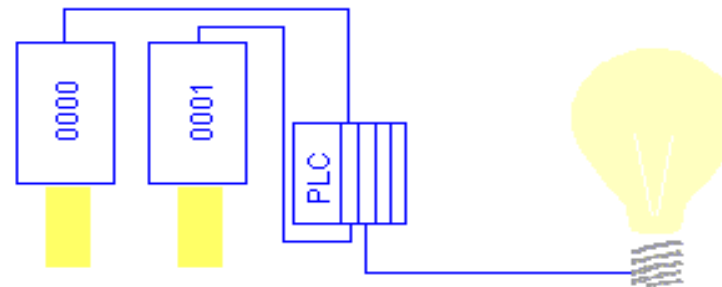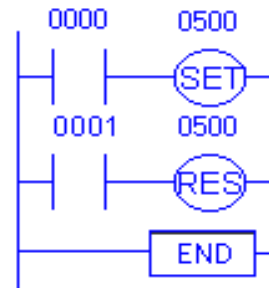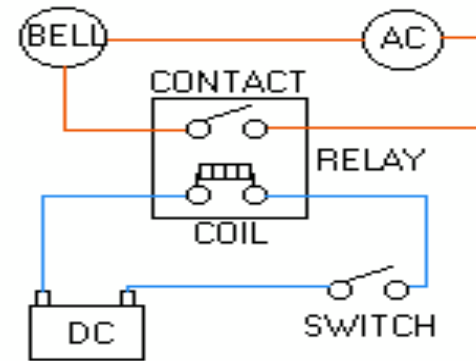

Ladder diagram

Basic Instructions

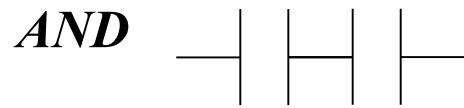


AND of the operand with the result of the previous logical operation.




AND of the inverted operand with the result of the previous logical operation.



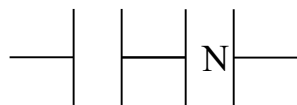AND of the rising edge with the result of the previous logical operation.



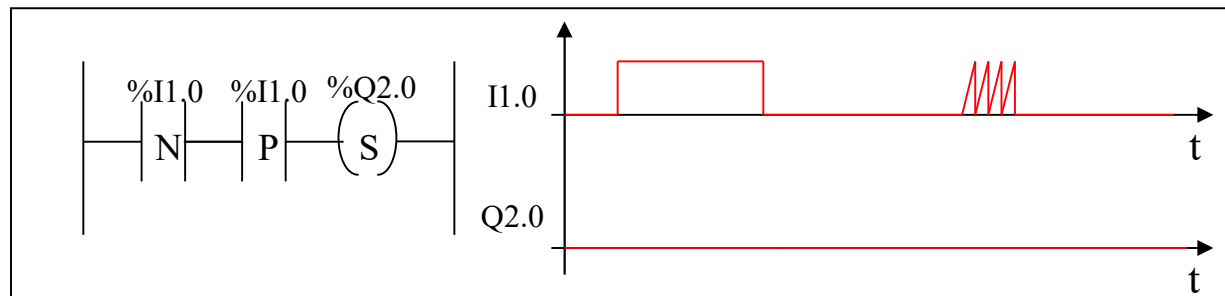
AND of the falling edge with the result of the previous logical operation.




Ladder diagram

Basic Instructions


OR

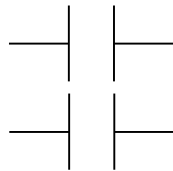

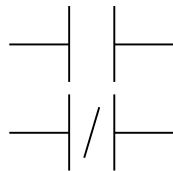
OR of the operand with the result of the previous logical operation.



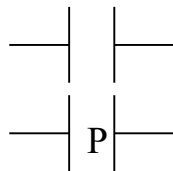OR of the inverted operand with the result of the previous logical operation.



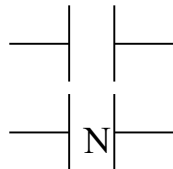OR of the rising edge with the result of the previous logical operation.




OR of the falling edge with the result of the previous logical operation.

Ladder diagram

Basic Instructions

XOR

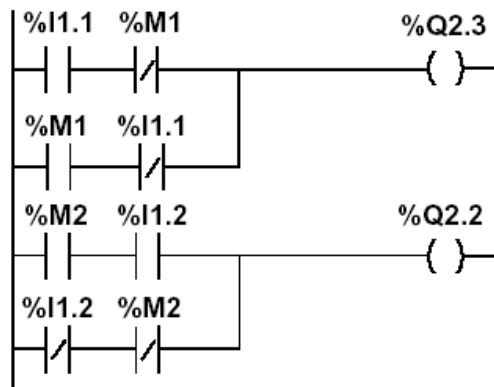


```

%Q2.3 := %I1.1 XOR %M1;
%Q2.2 := NOT(%M2 XOR %I1.2);
%Q2.2 := %M2 XOR NOT(%I1.2);
    
```

Instruction list	Structured text	Description	Timing diagram
XOR	XOR	OR Exclusive between the operand and the previous instruction's Boolean result	
XORN	XOR (NOT...)	OR Exclusive between the operand inverse and the previous instruction's Boolean result	
XORR	XOR (RE...)	OR Exclusive between the operand's rising edge and the previous instruction's Boolean result	
XORF	XOR (FE...)	OR Exclusive between the operand's falling edge and the previous instruction's Boolean result.	

Ladder diagram

Ladder assembling

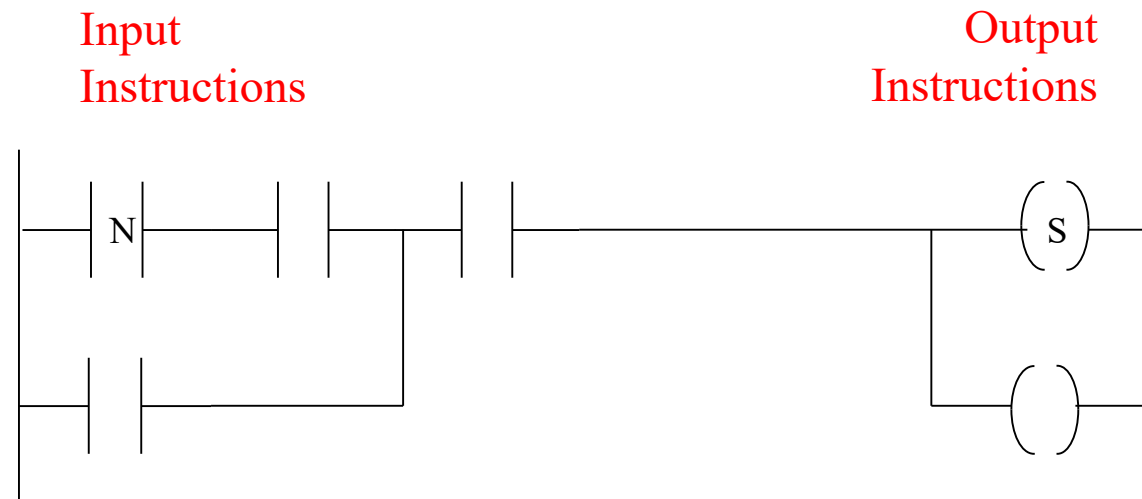


The **outputs** that have a **TRUE** logical value, evaluated from the left to right and from the top to the bottom, are **energized** .


[Schneider, Micro PLCs]

Ladder diagram

Example:
Latch / Sealing,
Feedback

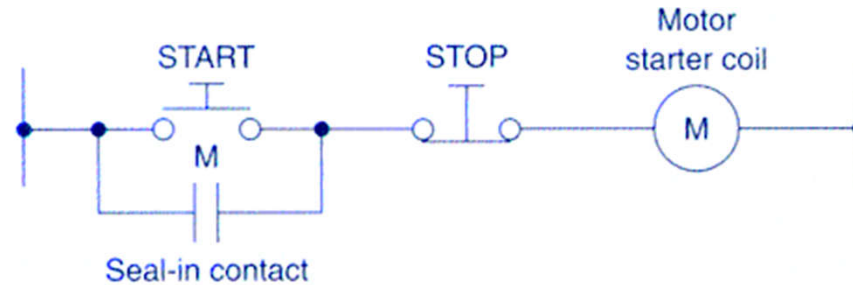

(a) Hard-wired circuit

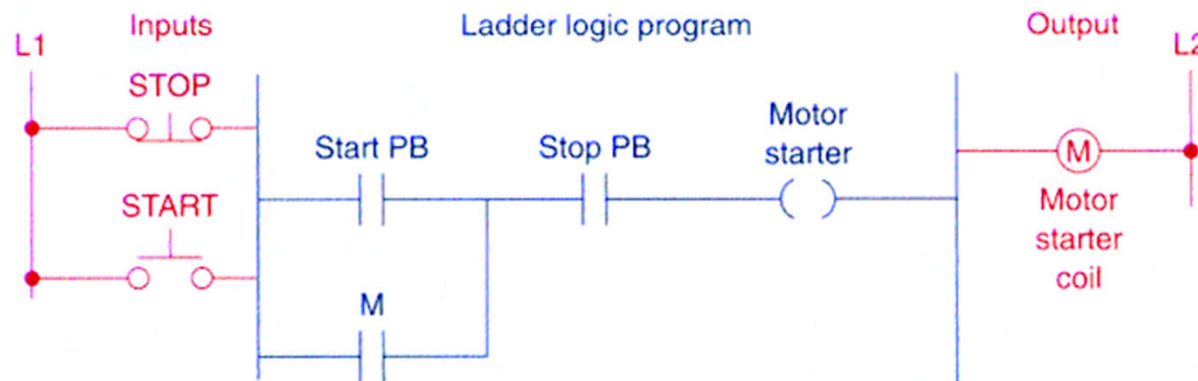

(b) Programmed circuit


Fig. 6-48

Seal-in circuit.

The **normally closed** push button **STOP** drives the normally open contact **Stop PB**

Ladder diagram


Example:
Latch / Sealing,
Feedback

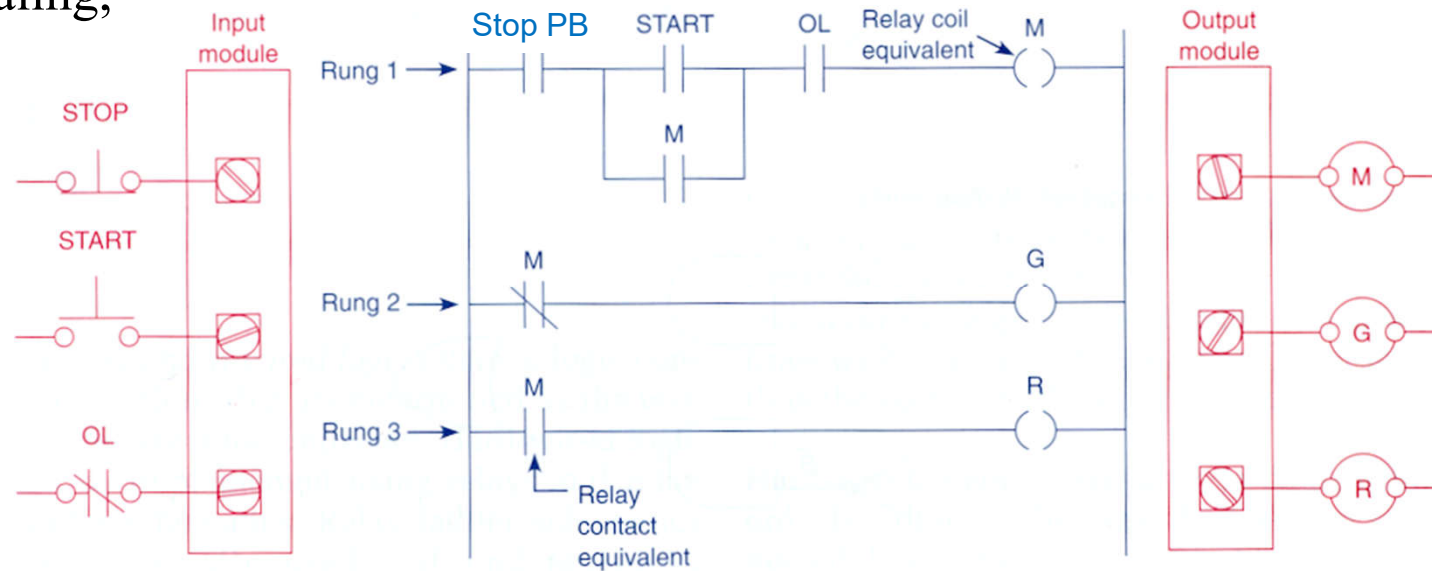

The **normally closed** push button **STOP** drives the normally open contact **Stop PB**

Ladder diagram

Example:
Latch / Sealing,
Feedback

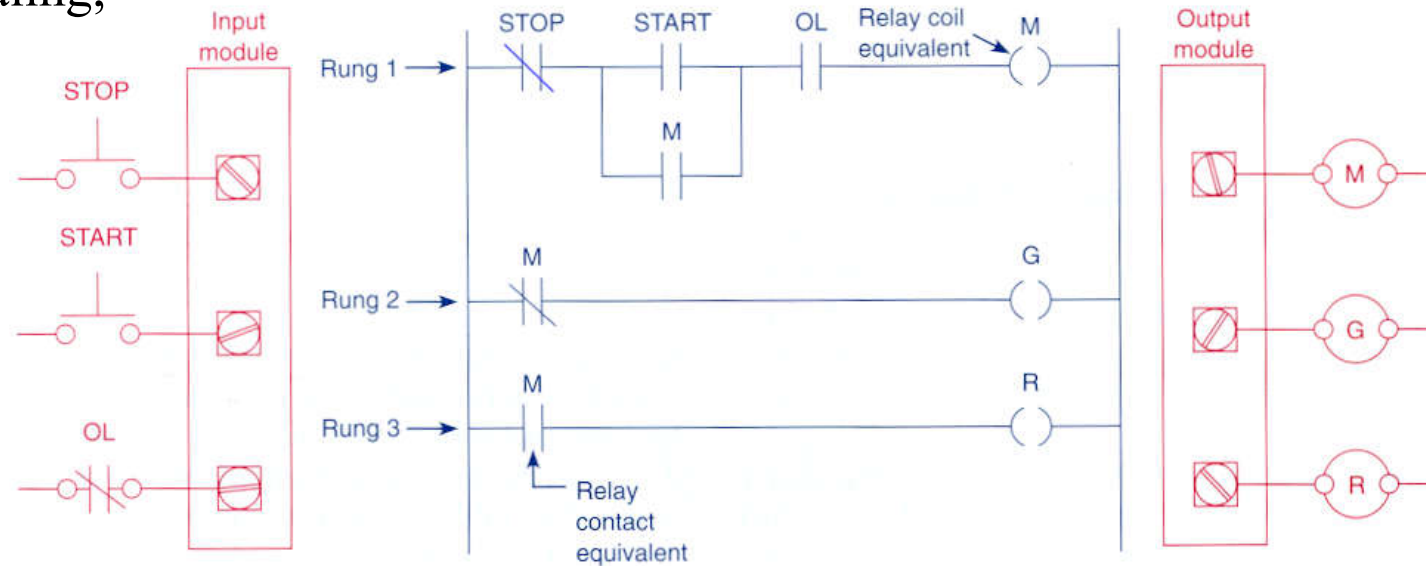

STOP button **normally open** implies **inverting that input** in the ladder diagram.

Ladder diagram


Example:
Latch / Sealing,
Feedback

Example 4-9


A motor control circuit with two stop buttons:

- When the start button is depressed, the motor runs.
- By sealing, it continues to run when the start button is released.
- The stop buttons stop the motor when they are depressed.


Relay Schematic

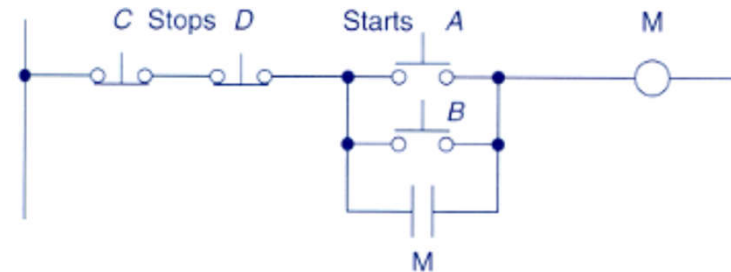

Ladder logic program

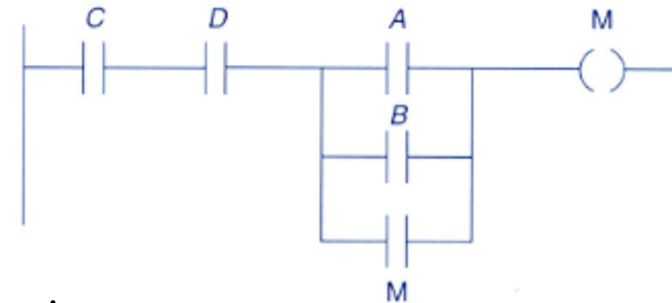

Gate logic

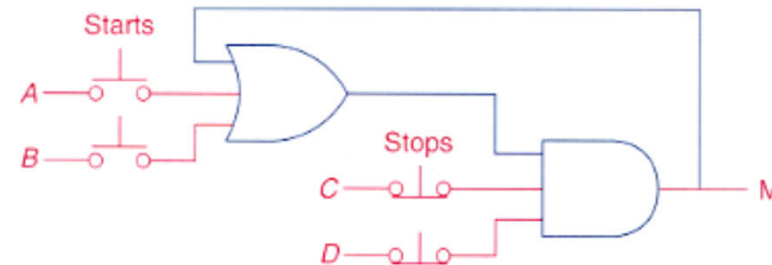

Ladder diagram

General case of Inputs and Outputs in **parallel**, with **derivations**

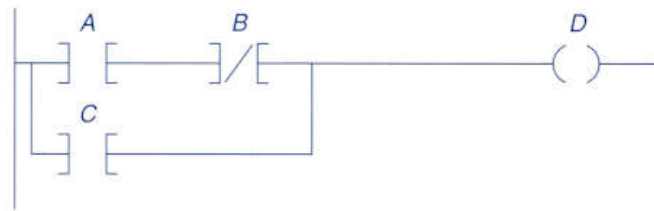


Fig. 5-21

Parallel input branching.

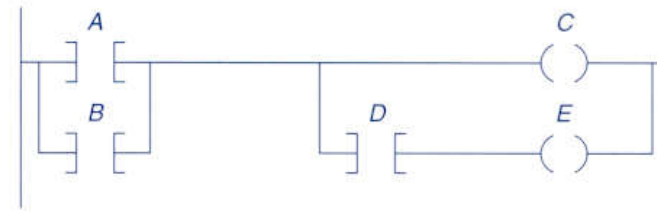


Fig. 5-23

Parallel output branching with conditions.



Fig. 5-22

Parallel output branching.

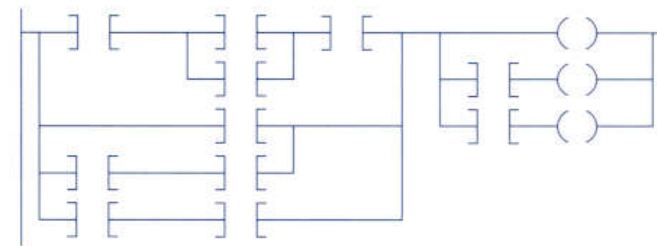


Fig. 5-24

Nested input and output branches.

Note: it is important to study the **constraints** and **potentialities** of the development tools.

Ladder diagram

Imbricated (nested) contacts and **alternative** solution

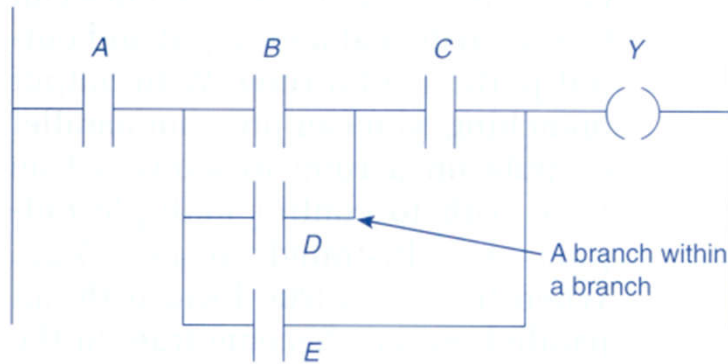


Fig. 5-25
Nested contact program.

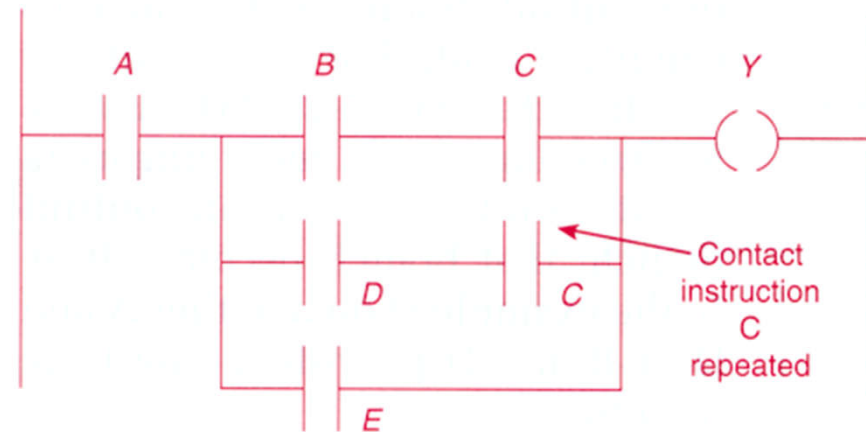


Fig. 5-26
Program required to eliminate nested contact.

Ladder diagram

Contacts in the **vertical** and **alternative** solution

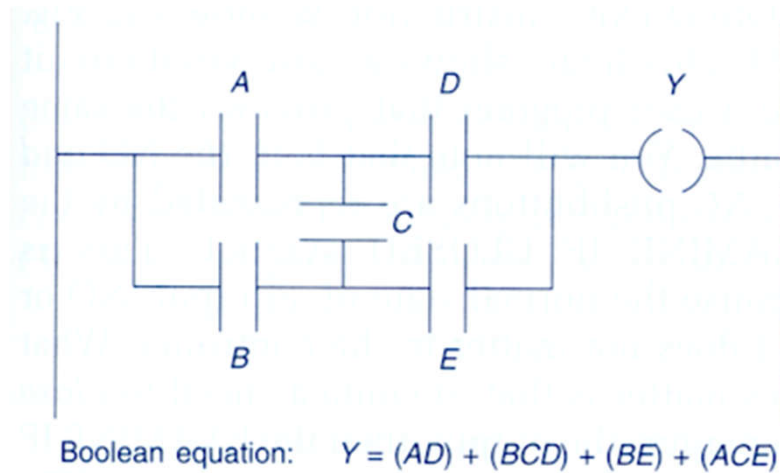


Fig. 5-28
Program with vertical contact


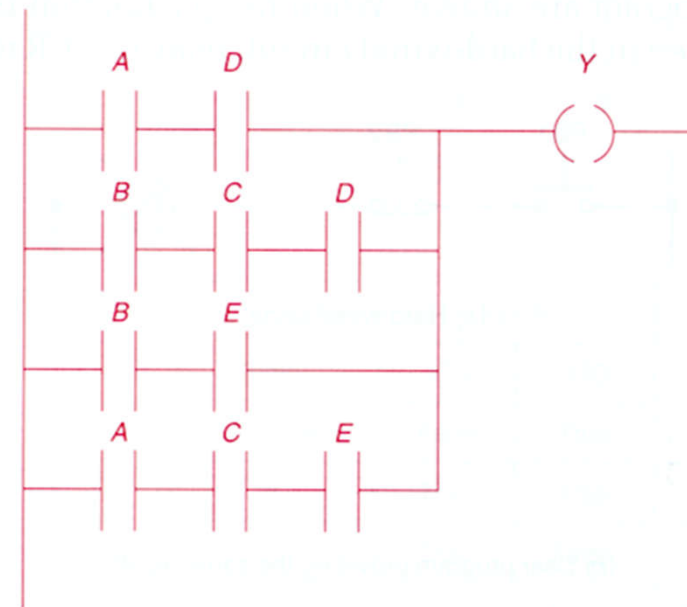


Fig. 5-29
Reprogrammed to eliminate vertical contact.

Ladder diagram

Contacts in the **vertical** and **alternative** solution

Another example:

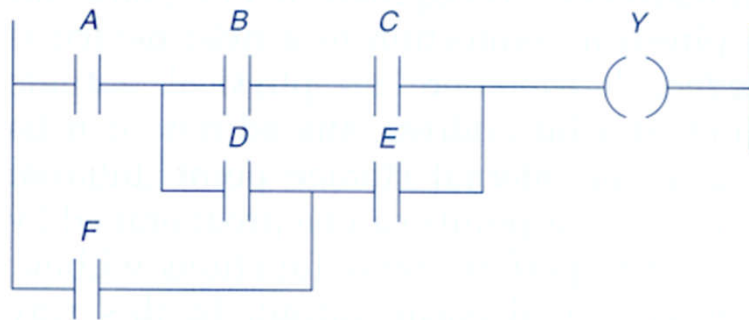

Boolean equation: $Y = (ABC) + (ADE) + (FE) + (FDBC)$

Fig. 5-30

Original circuit.

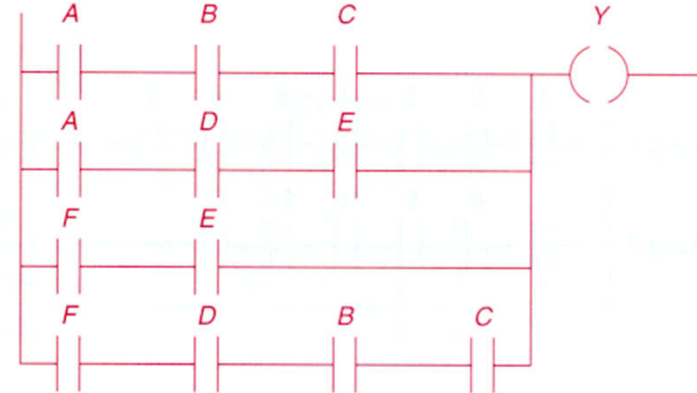


Fig. 5-31


Reprogrammed circuit.

Solves the problem of disallowed right to left scanning (FDBC in fig5.30).

Ladder diagram *Temporized Relays or Timers*



Solid-state timing relay

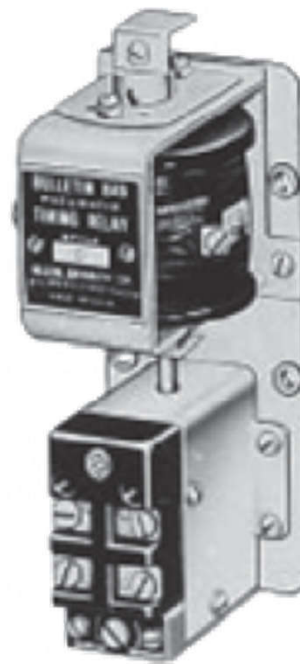


Pneumatic timing relay



Plug-in timing relay



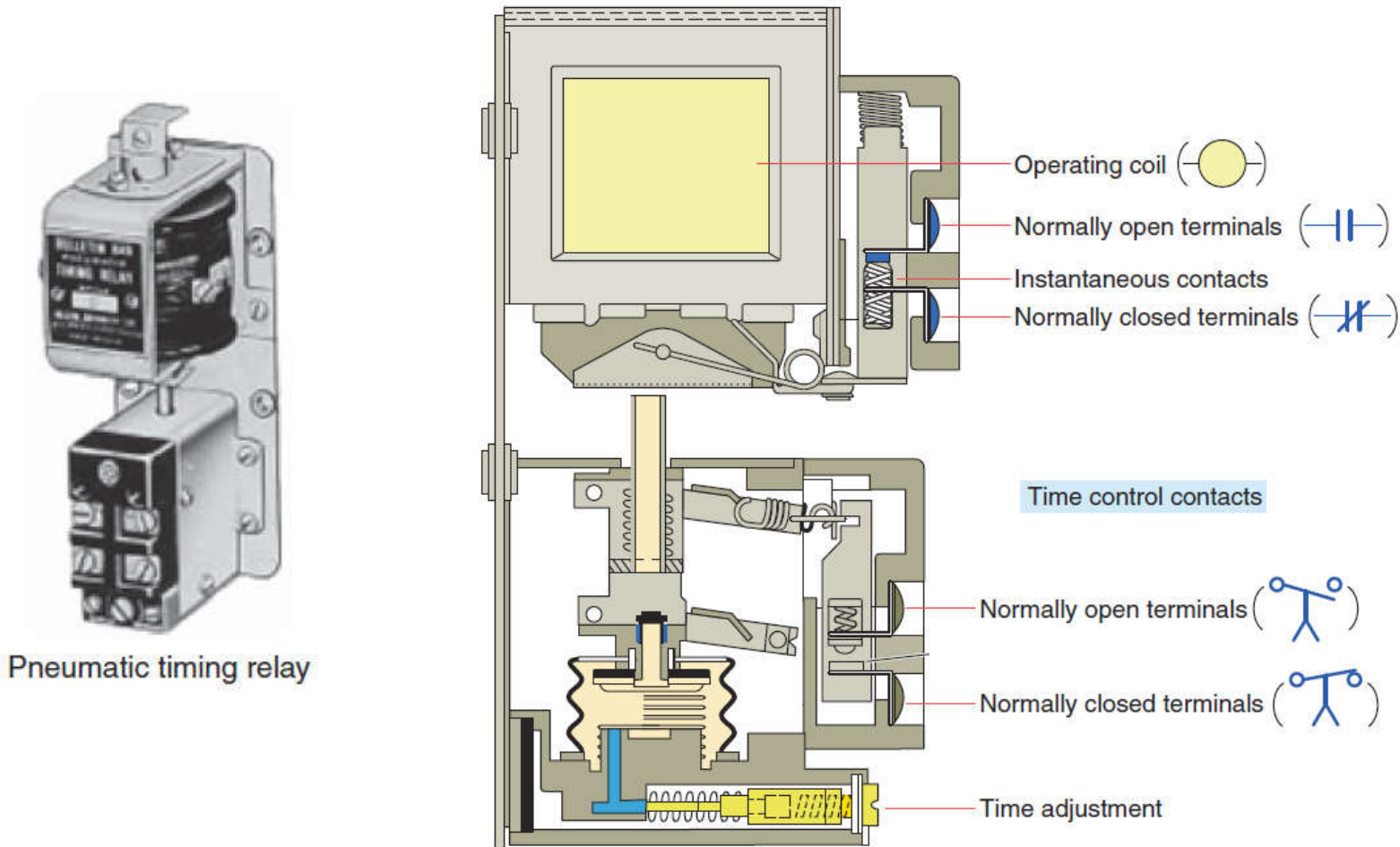

Ladder diagram *Temporized Relays or Timers (pneumatic)*



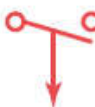

 

The **instantaneous** contacts change state as soon as the timer coil is powered.
 The **delayed** contacts change state at the end of the time delay.

Ladder diagram *Temporized Relays or Timers*

On-delay, provides time delay when the relay coil is energized.

On-delay symbols	
 or 	 or 
<p>Normally open, timed closed contact (NOTC).</p> <p>Contact is open when relay coil is de-energized.</p> <p>When relay is energized, there is a time delay in closing.</p>	<p>Normally closed, timed open contact (NCTO).</p> <p>Contact is closed when relay coil is de-energized.</p> <p>When relay is energized, there is a time delay in opening.</p>


Off-delay, provides time delay when the relay coil is de-energized.

Off-delay symbols	
 or 	 or 
<p>Normally open, timed open contact (NOTO).</p> <p>Contact is normally open when relay coil is de-energized.</p> <p>When relay coil is energized, contact closes instantly.</p> <p>When relay coil is de-energized, there is a time delay before the contact opens.</p>	<p>Normally closed, timed closed contact (NCTC).</p> <p>Contact is normally closed when relay coil is de-energized.</p> <p>When relay coil is energized, contact opens instantly.</p> <p>When relay coil is de-energized, there is a time delay before the contact closes.</p>

Tables: Relay *symbols* used for timed contacts.


Ladder diagram *Temporized Relays or Timers*

Timer On-delay (TON)

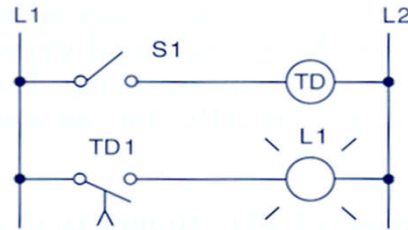

Sequence of operation:
 S1 open, TD de-energized, TD1 open, L1 off.
 S1 closes, TD energizes, timing period starts, TD1 is still open, L1 is still off.
 After 10 s, TD1 closes, L1 is switched on.
 S1 is opened, TD de-energizes, TD1 opens instantly, L1 is switched off.


(a)

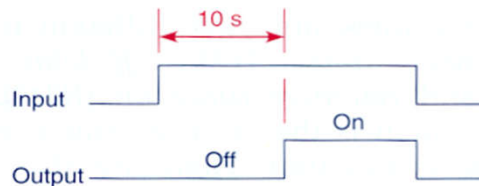

(b)


Fig. 7-3

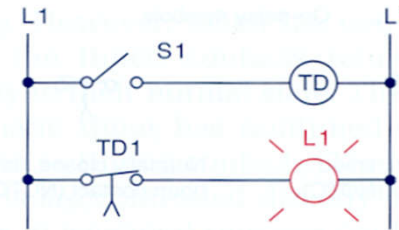On-delay timer circuit (NOTC contact). (a) Operation. (b) Timing diagram.



Sequence of operation:
 S1 open, TD de-energized, TD1 closed, L1 on.
 S1 closes, TD energizes, timing period starts, TD1 is still closed, L1 is still on.
 After 10 s, TD1 opens, L1 is switched off.
 S1 is opened, TD de-energizes, TD1 closes instantly, L1 is switched on.

(a)

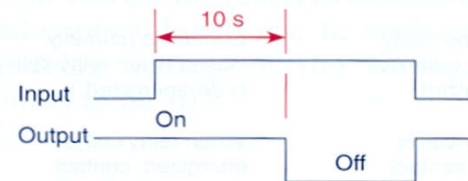


(b)

Fig. 7-4

On-delay timer circuit (NCTO contact). (a) Operation. (b) Timing diagram.


Ladder diagram *Temporized Relays or Timers*

**Timer
Off-delay
(TOF)**

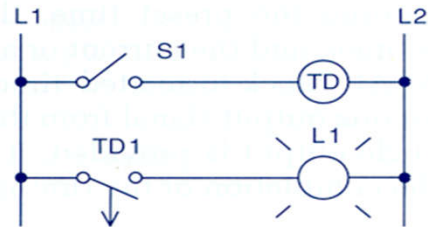

Sequence of operation:
 S1 open, TD de-energized, TD1 open, L1 off.
 S1 closes, TD energizes, TD1 closes instantly, L1 is switched on.
 S1 is opened, TD de-energizes, timing period starts, TD1 is still closed, L1 is still on.
 After 10 s, TD1 opens, L1 is switched off.


(a)

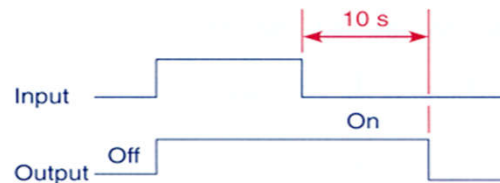

(b)


Fig. 7-5

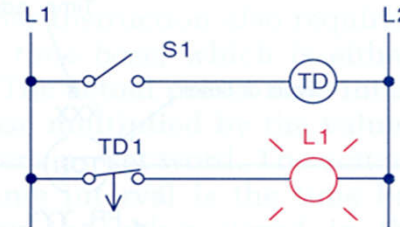Off-delay timer circuit (NOC contact). (a) Operation. (b) Timing diagram.



Sequence of operation:
 S1 open, TD de-energized, TD1 closed, L1 on.
 S1 closes, TD energizes, TD1 opens instantly, L1 is switched off.
 S1 is opened, TD de-energizes, timing period starts, TD1 is still open, L1 is still off.
 After 10 s, TD1 closes, L1 is switched on.

(a)

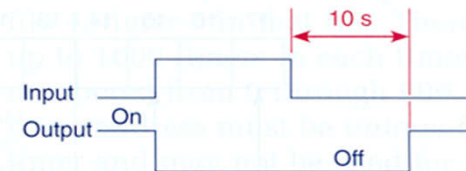

(b)


Fig. 7-6

Off-delay timer circuit (NCC contact). (a) Operation. (b) Timing diagram.

Ladder diagram

Temporized Relays

or Timers (PLC)

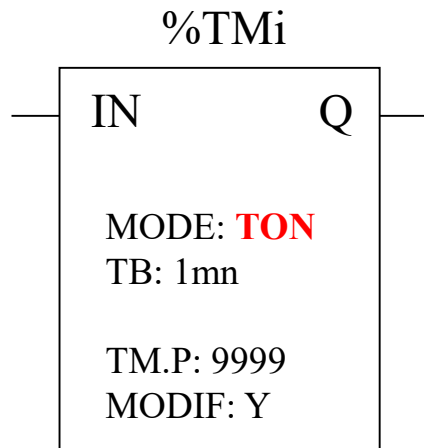

Characteristics:



Identifier:	%Tmi	0..63 in the TSX37
Input:	IN	to activate
Mode:	TON	Timer On delay
	TOF	Timer Off delay
	TP	Monostable
Time basis:	TB	1mn (def.), 1s, 100ms, 10ms
Programmed value:	%Tmi.P	0...9999 (def.) period=TB*Tmi.P
Actual value:	%Tmi.V	0...Tmi.P (can be read or tested)
Modifiable:	Y/N	can be modified from the console

Ladder diagram

Temporized Relays

or Timers (PLC)

TON mode

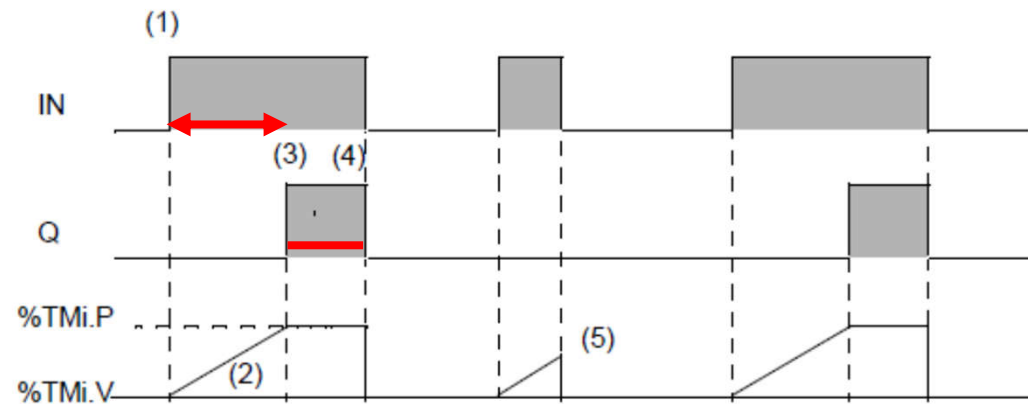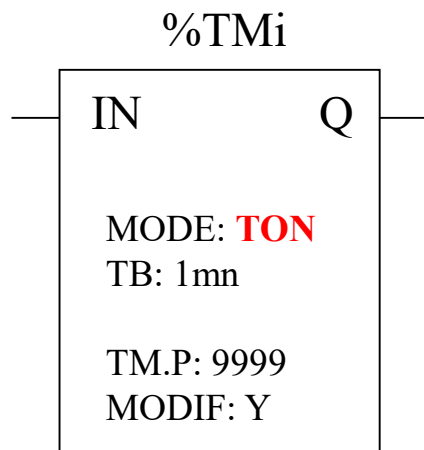

Phase	Description
1	The timer is started with a rising edge on the IN input
2	The current value %TMi.V of the timer increases from 0 to %TMi.P by one unit at each pulse of the time base TB
3	The %TMi.Q output bit moves to 1 when the current value has reached %TMi.P
4	The %TMi.Q output bit stays at 1 while the IN input is at 1.
5	When the IN input is at 0, the timer is stopped even if it is still running: %TMi.V takes the value 0.



App. example: start ringing the alarm if N sec after door open there is no disarm of the alarm.

Ladder diagram

Temporized Relays

or Timers (PLC)

TOF mode

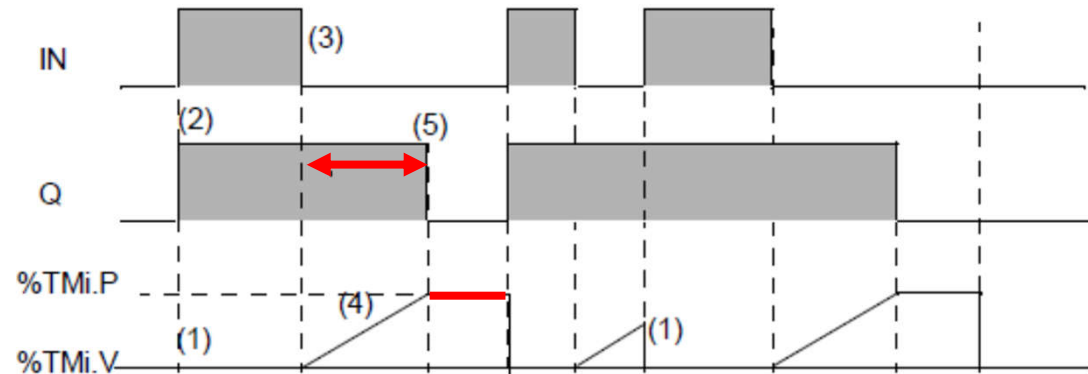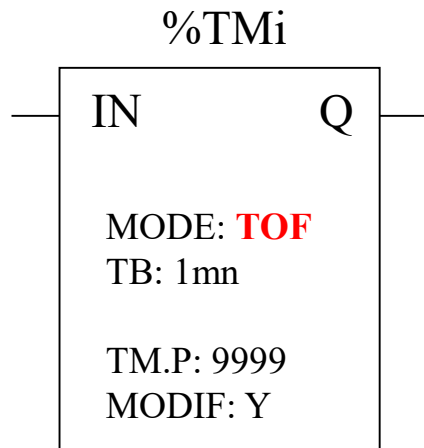

Phase	Description
1	The current value %Tmi.V takes 0, on a rising edge of the IN input (even if the timer is running)
2	The %Tmi.Q output bit moves to 1.
3	The timer is started with a falling edge on the IN input.
4	The current value %Tmi.P increases to %Tmi.P by one unit at each pulse of the time base TB.
5	The %Tmi.Q output bit returns to 0 when the current value has reached %Tmi.P

App. example: turn off stairways lights after N sec the lights' button has been released.



Ladder diagram

TP mode

Temporized Relays

or Timers (PLC)

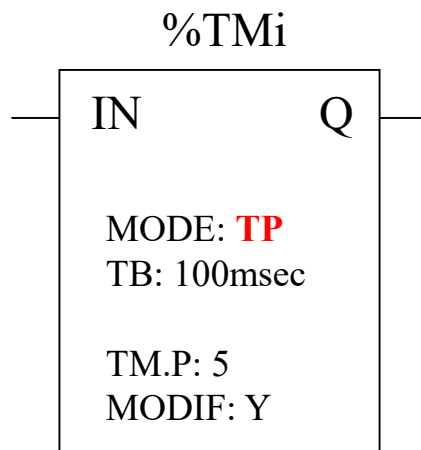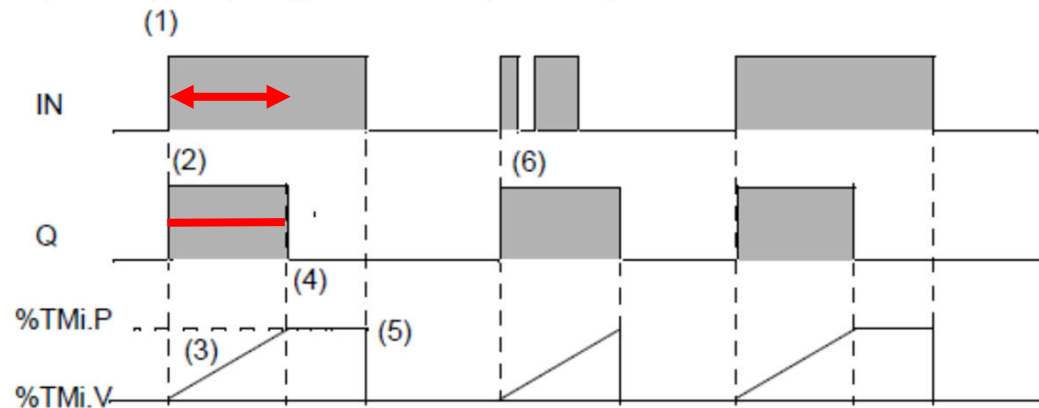Works as a monostable or as a pulse generator (with pre-programmed period)





Phase	Description
1	The timer is started with a rising edge on the IN input
2	The %Tmi.Q output bit moves to 1.
3	The current value %Tmi.V of the timer increases from 0 to %Tmi.P by one unit at each pulse of the time base TB
4	The %Tmi.Q output bit returns to 0 when the current value has reached %Tmi.P.
5	When the IN input and the %Tmi.Q output are at 0, %Tmi.V takes the value 0.
6	This monostable cannot be reactivated.

App. example: positive input edge give a controlled (fixed) duration pulse to start a motor.

Ladder diagram

Timers in PL7 vs Unity (Schneider)

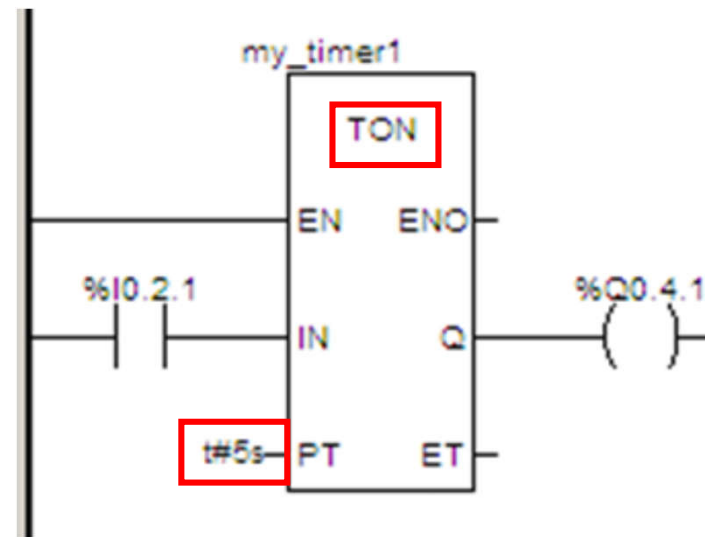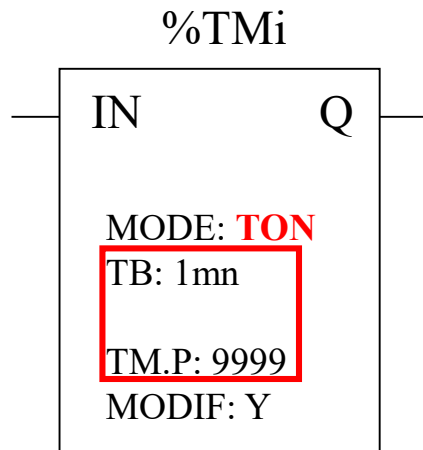

*Input EN and output ENO
are facultative*

Ladder diagram

Timers in the Allen-Bradley PLC-5

Two alternative representations


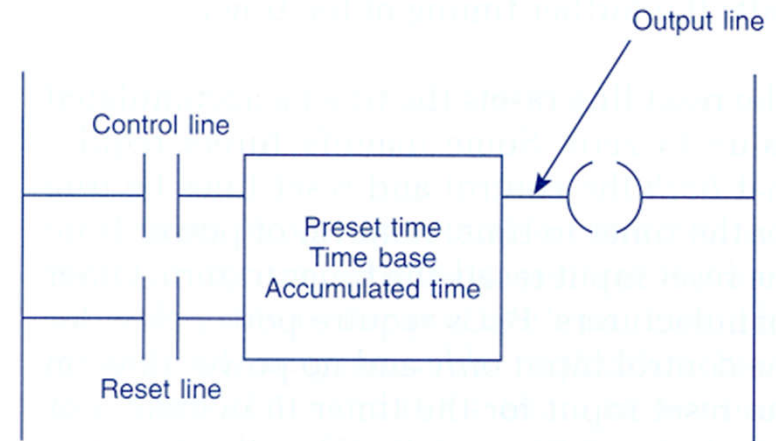
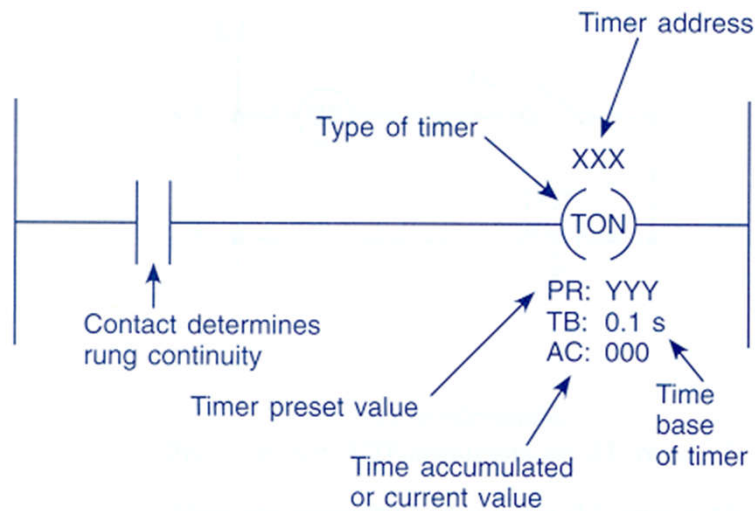


Fig. 7-8

Block-formatted timer instruction.

Ladder diagram

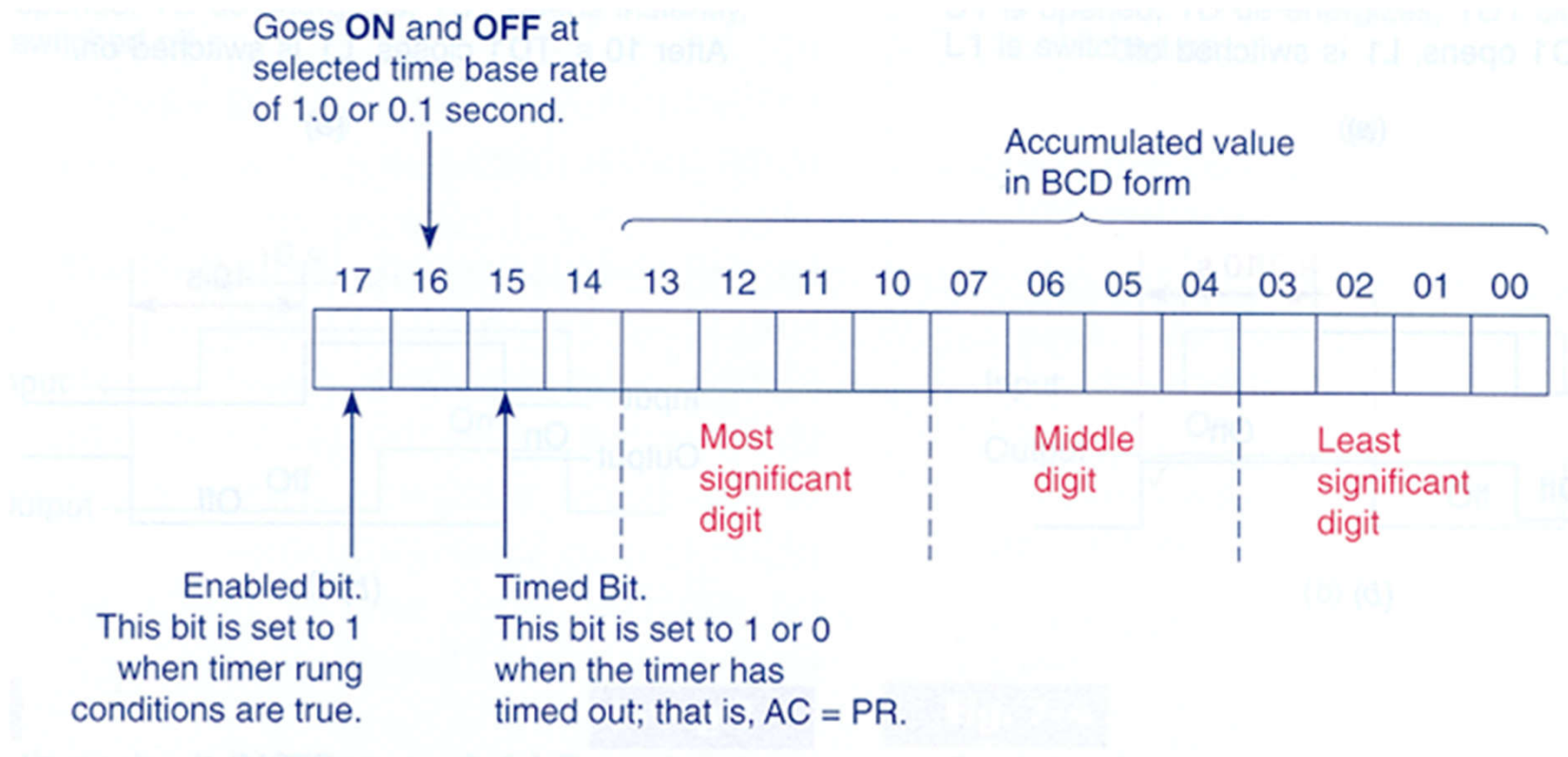Timers implementation in the Allen-Bradley PLC-5:



Ladder diagram

Timers operation in the Allen-Bradley PLC-5

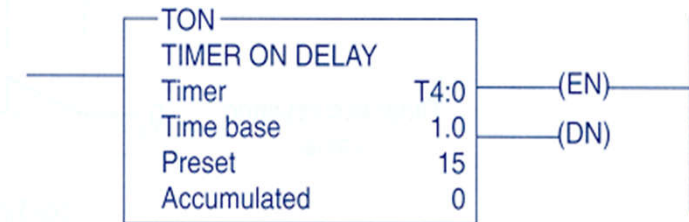
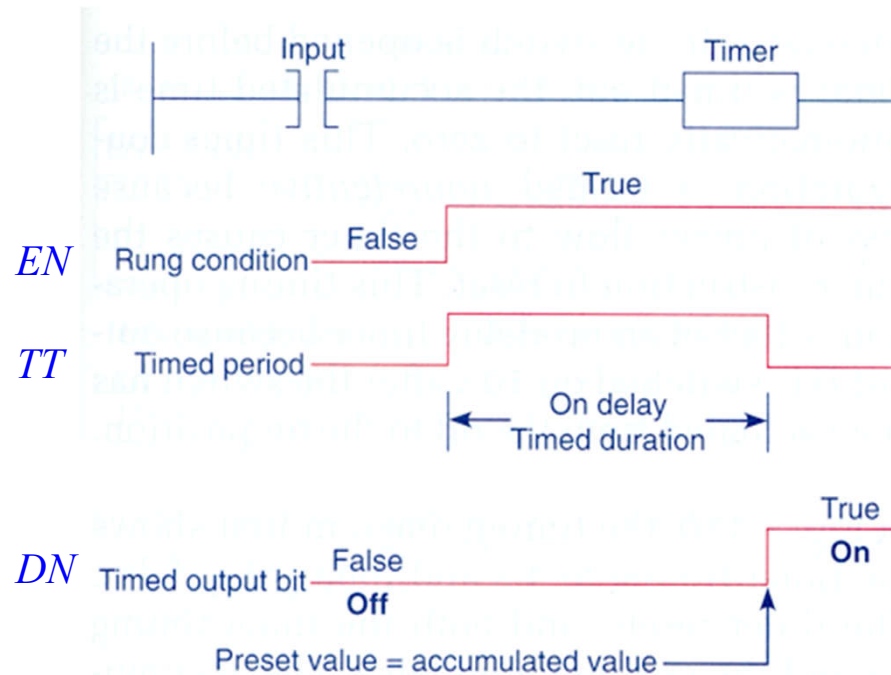


Fig. 7-10

On-delay timer instruction.

EN = Enable Bit TT = Timer-Timing Bit DN = Done Bit

Ladder diagram

Example of *timer on-delay*

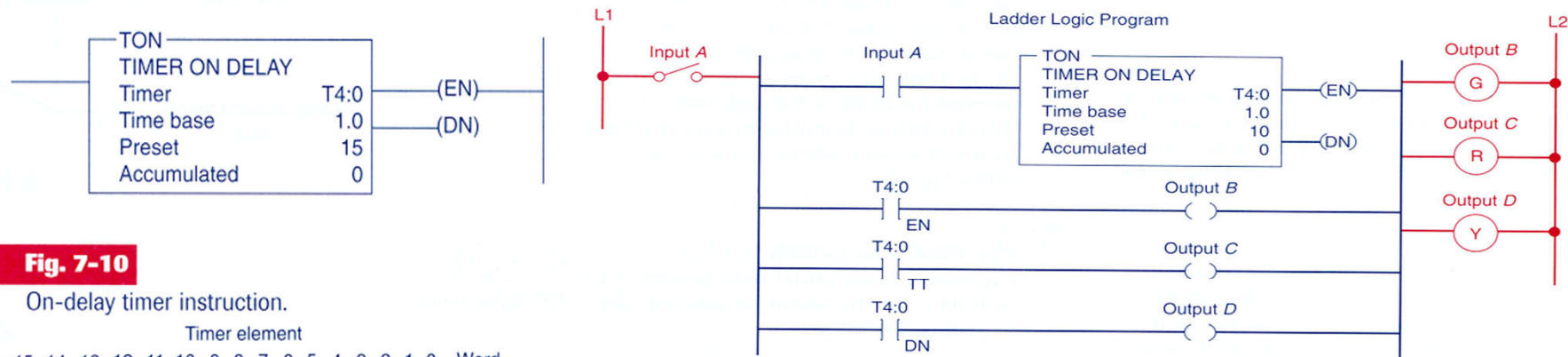


Fig. 7-10

On-delay timer instruction.

Timer element															Word	
15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	
EN	TT	DN													Internal use	0
Preset value PRE															1	
Accumulated value ACC															2	

Addressable bits **Addressable words**
 EN = Bit 15 enable PRE = Preset value
 TT = Bit 14 timer timing ACC = Accumulated value
 DN = Bit 13 done


(c) Timers are 3-word elements. Word 0 is the control word, word 1 stores the preset value, and word 2 stores the accumulated value (Allen-Bradley PLC-5 and SLC-500 format).

Fig. 7-11 (continued)

On-delay timer.

Fig. 7-11

On-delay timer.

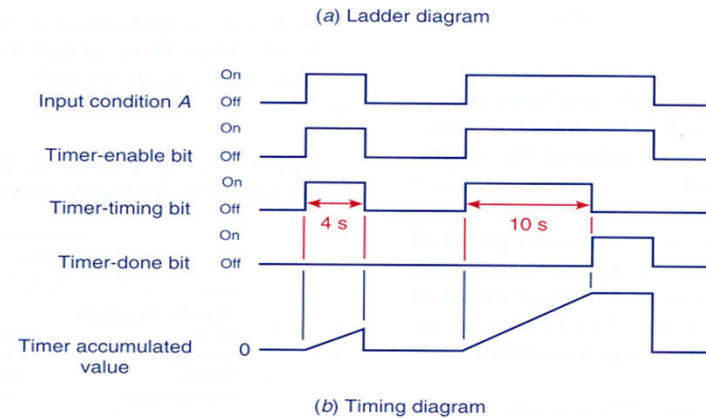

Ladder diagram

Example of a *timer on-delay* that sets an output after a count-down


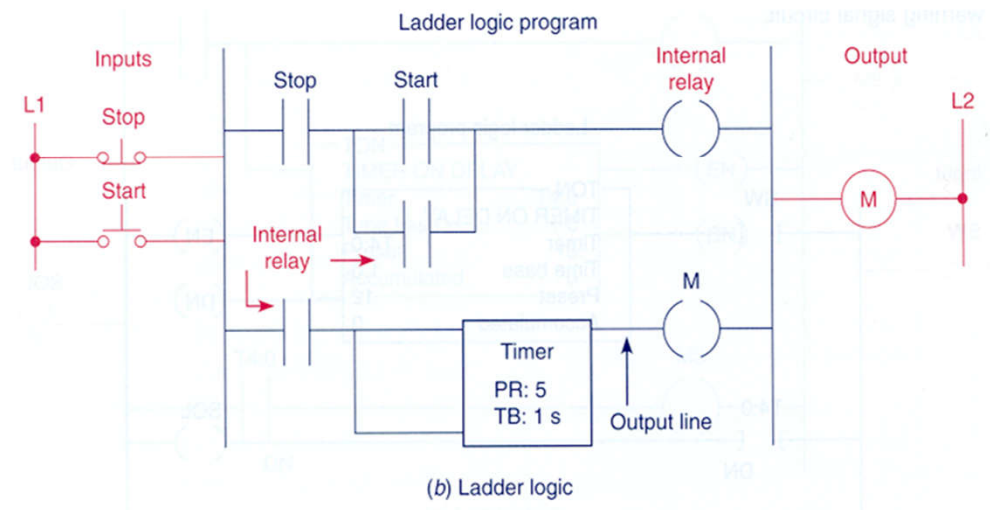
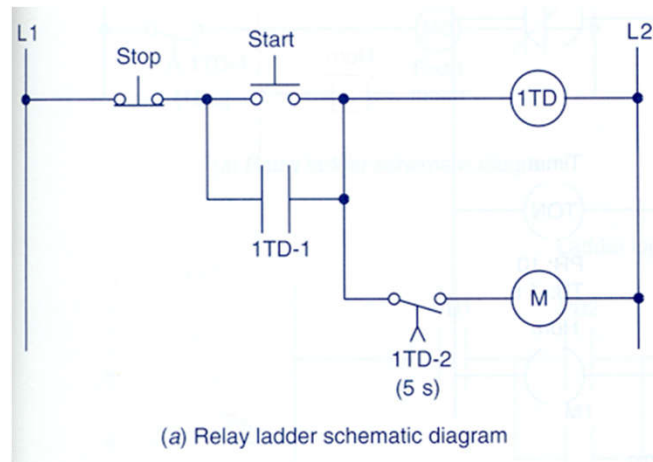



Fig. 7-12
On-delay timer with instantaneous output programming.

Ladder diagram

Example of *timer on-delay*

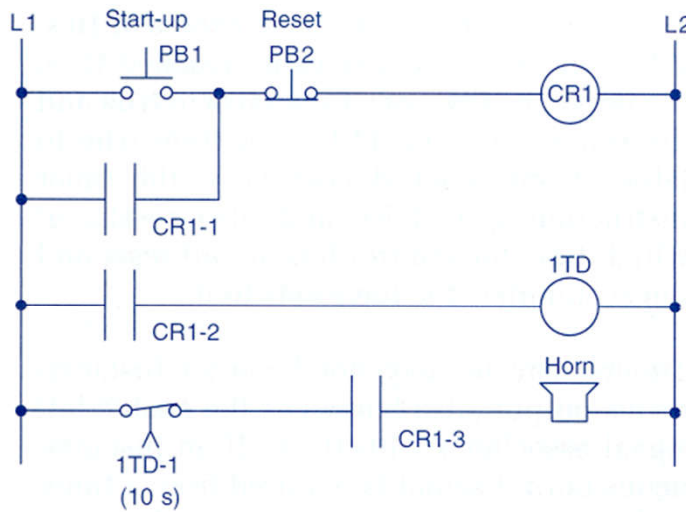

(a) Relay ladder schematic diagram

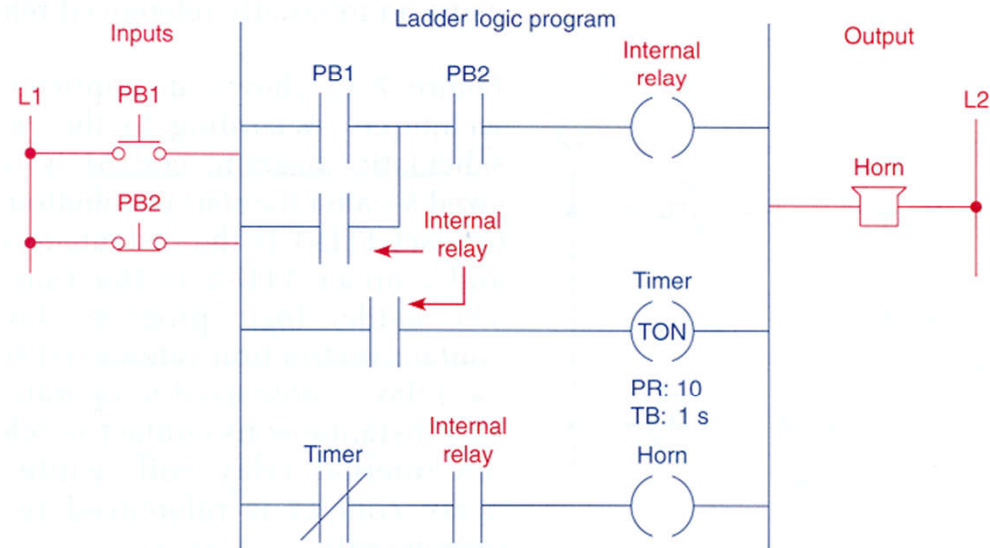

(b) Ladder logic

Fig. 7-13

Starting-up warning signal circuit.

Ladder diagram

Example of *timer on-delay*

Coil is energized if the switch remains closed for 12 seconds

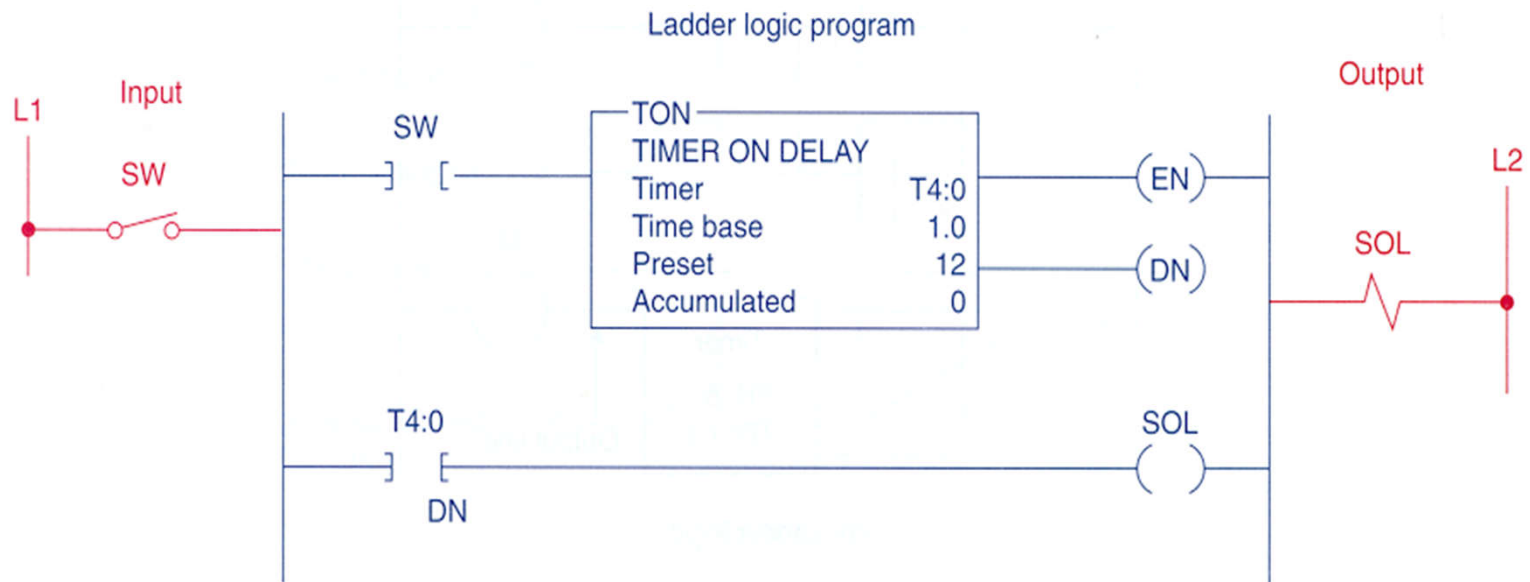



Fig. 7-14

Solenoid valve timed closed.


Ladder diagram

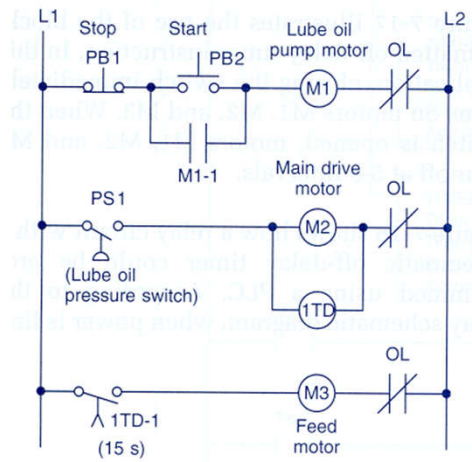Example of *timer on-delay*

- If PB2 is activated, powers on the oil pumping motor.
- When the pressure augments, PS1 detects the increase and activates the main motor.
- 15 seconds later the main drive motor starts.



(a) Relay ladder schematic diagram

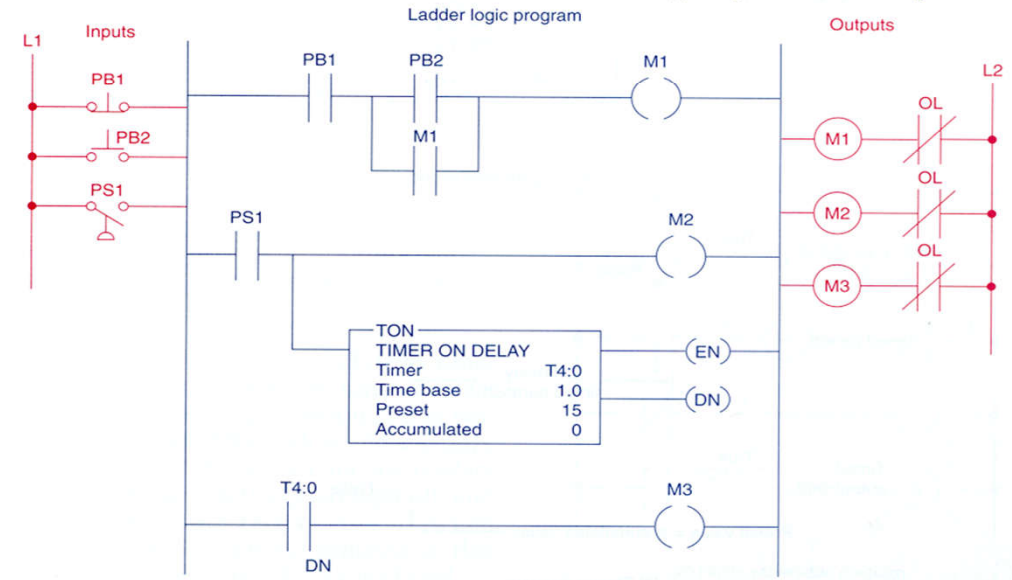

(b) Ladder logic

Fig. 7-15
Automatic sequential control system.

Ladder diagram

Example of *timer* programmed as *off-delay*

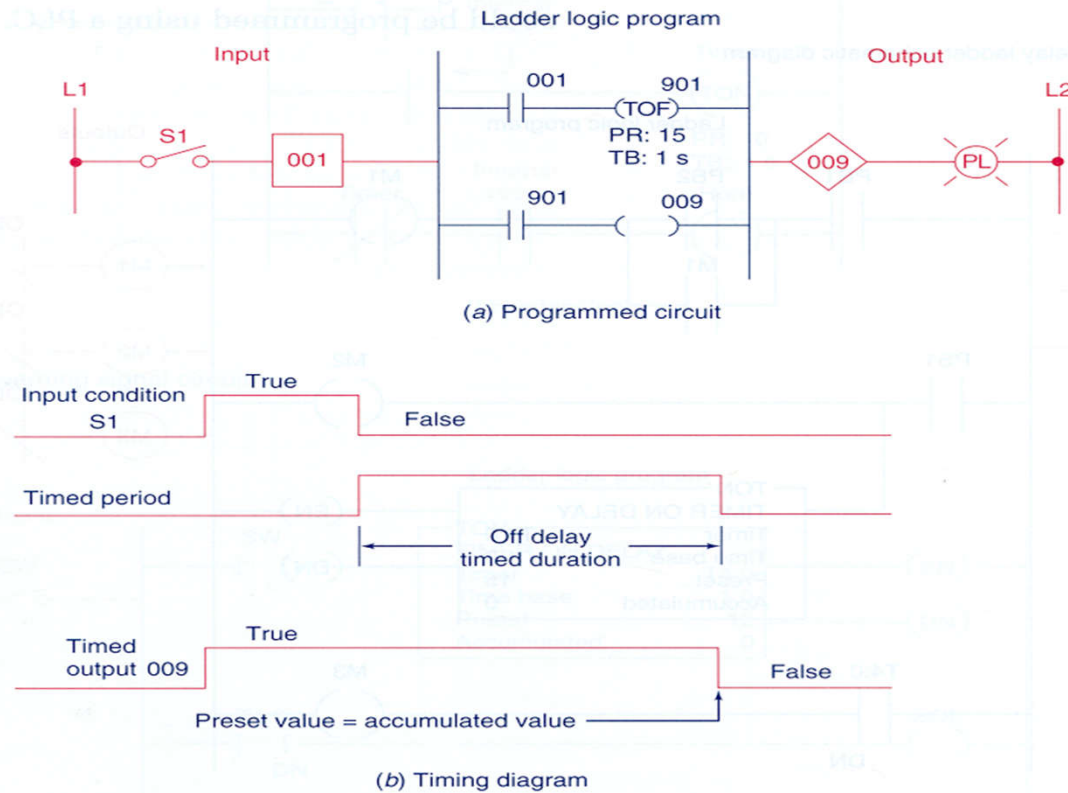


Fig. 7-16
Off-delay programmed timer.

Ladder diagram

Example of *timer* programmed as *off-delay*


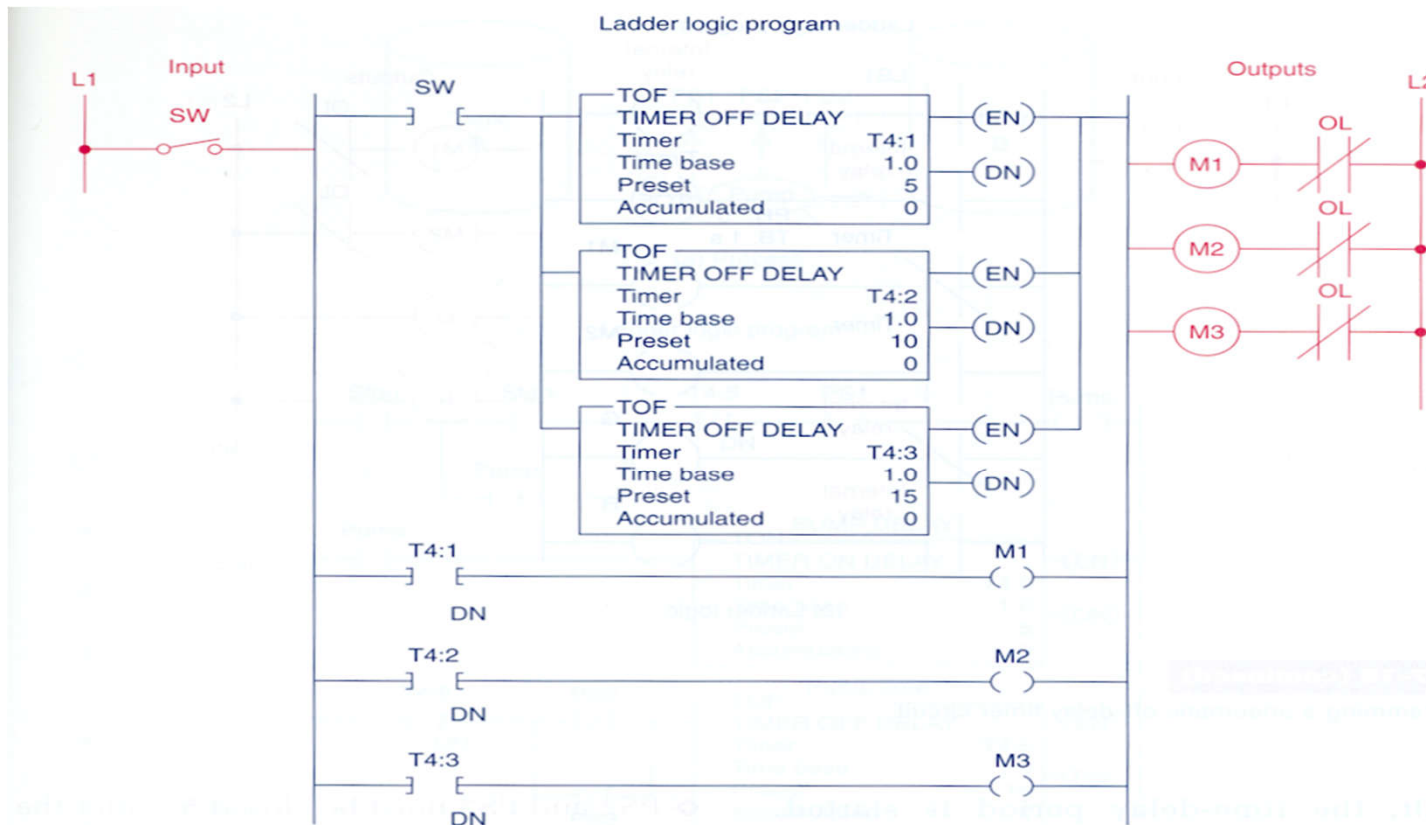


Fig. 7-17


Off-delay timer instructions programmed to switch motors off at 5-s intervals.

Ladder diagram

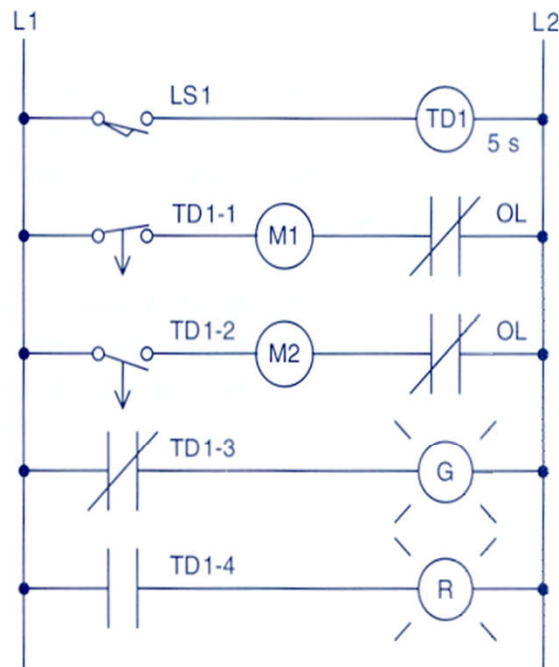Example of *timer* programmed as *off-delay*



(a) Relay schematic diagram

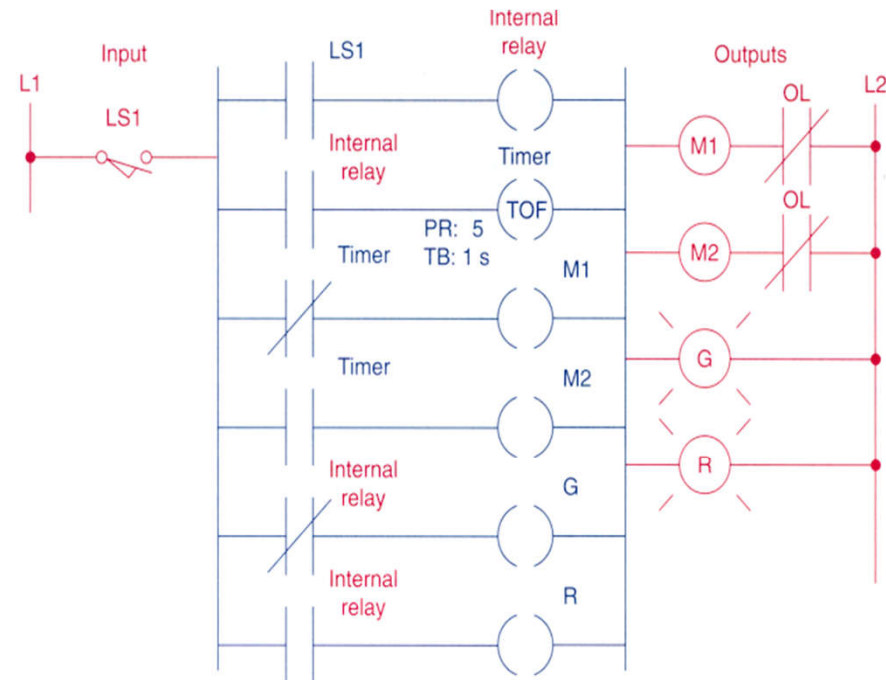

(b) Ladder logic

Fig. 7-18

Programming a pneumatic off-delay timer circuit.

Fig. 7-18 (continued)

Programming a pneumatic off-delay timer circuit.

Ladder diagram

Example of *timers* programmed as *off-delay* and *on-delay*


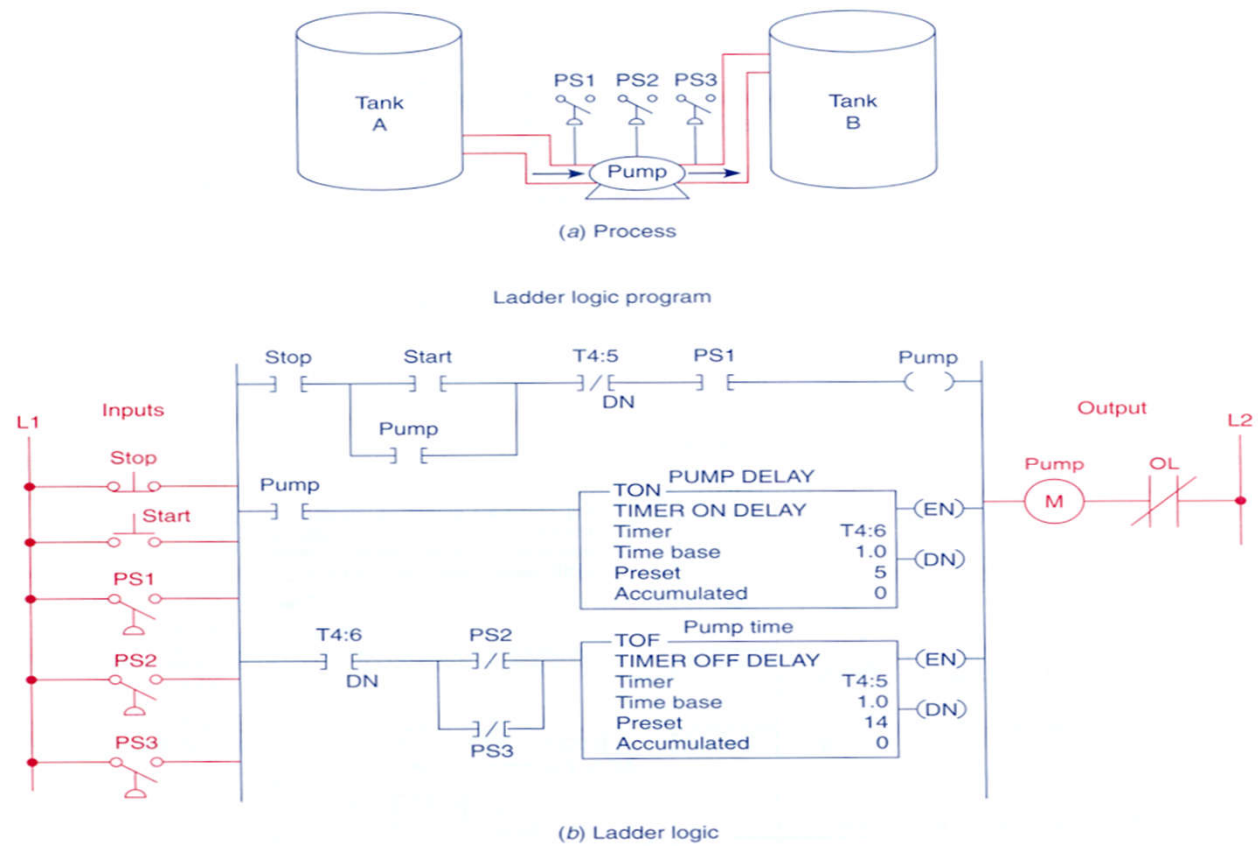


Fig. 7-19

Ladder diagram


Timers

Animated demonstration:

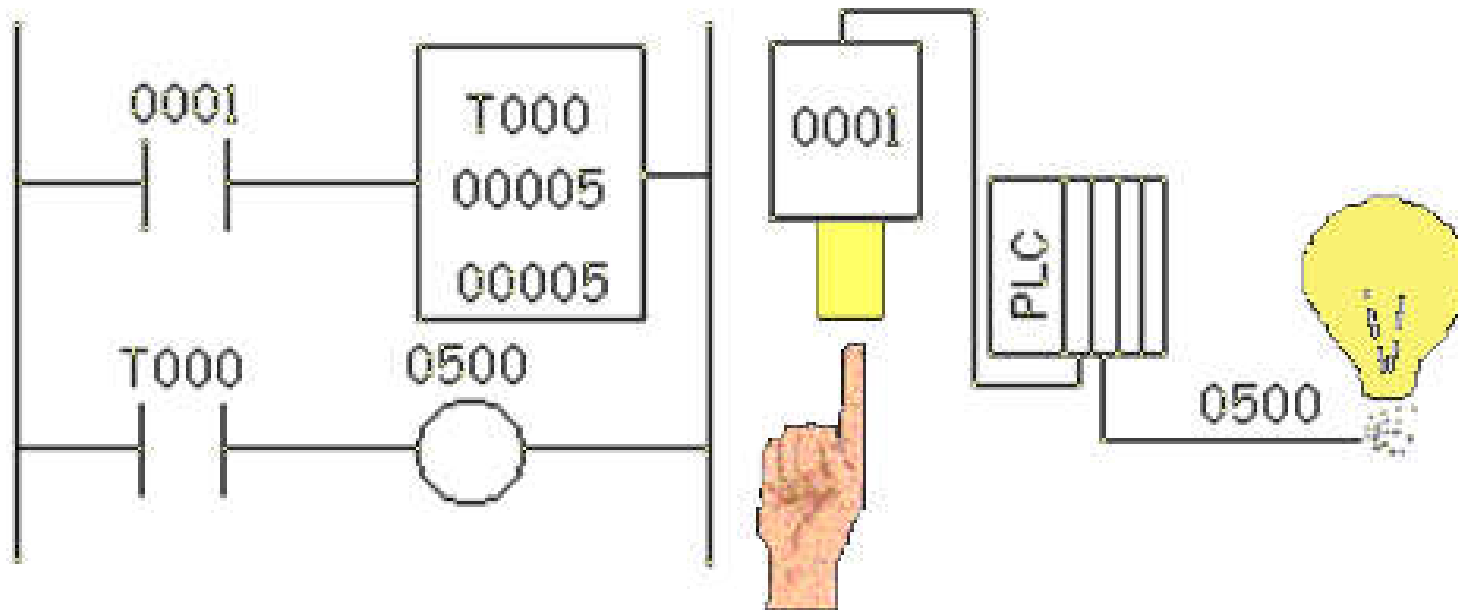

Ladder diagram


Retentive Timers

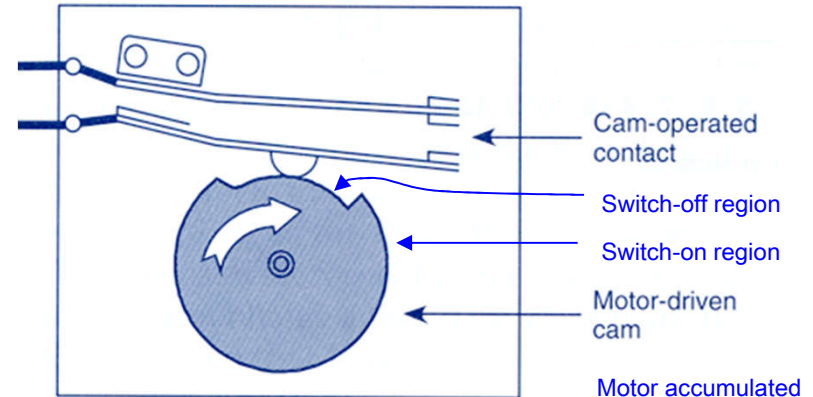


Motor accumulated motion (rotation) defines the on/off timing.

Fig. 7-20

Electromechanical retentive timer.

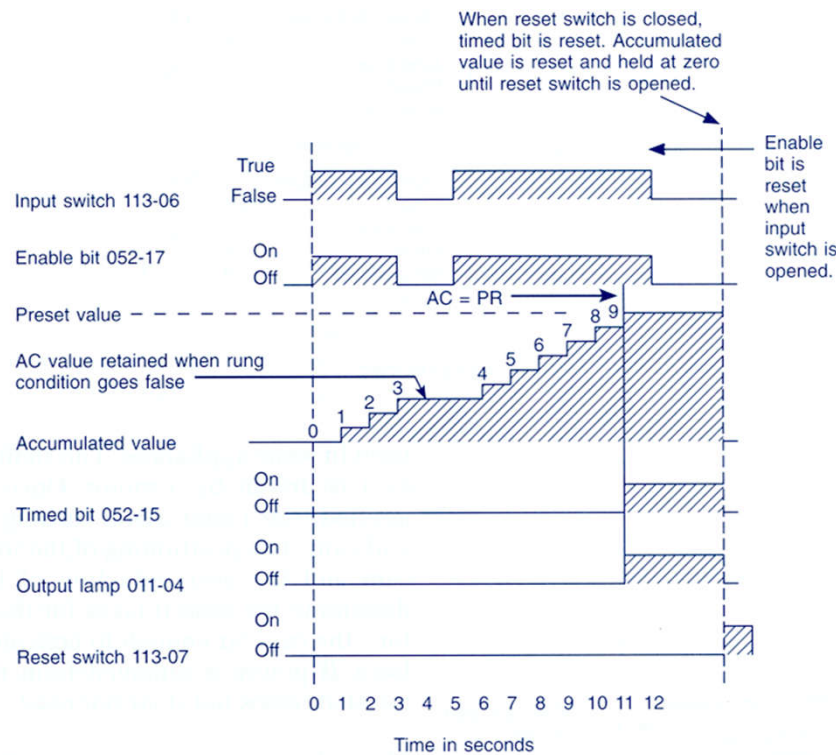

(b) Timing chart

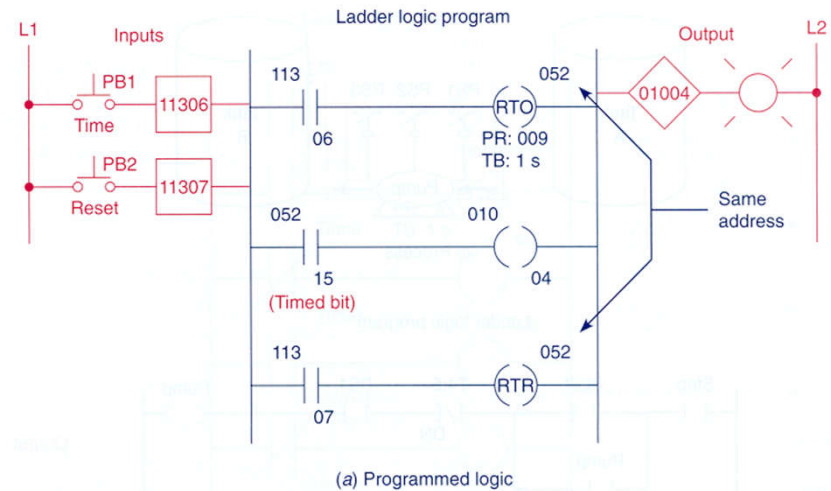

Ladder diagram

Example of *retentive timers*

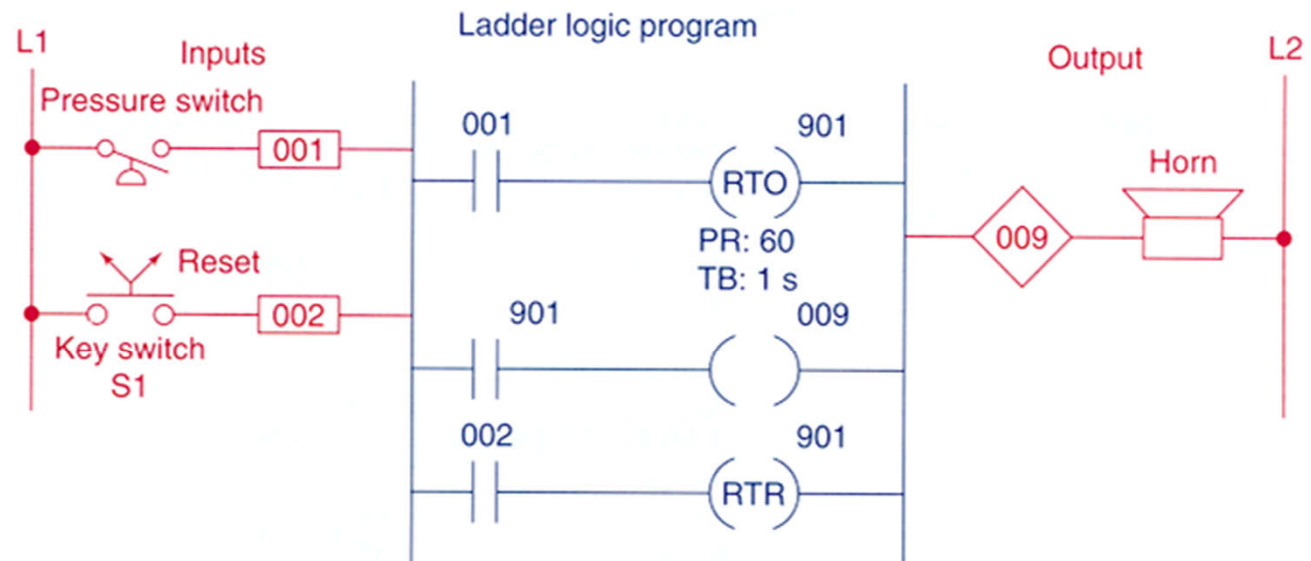



Fig. 7-22

Retentive on-delay alarm program.

~~adder~~ Timers

Animated demonstration:

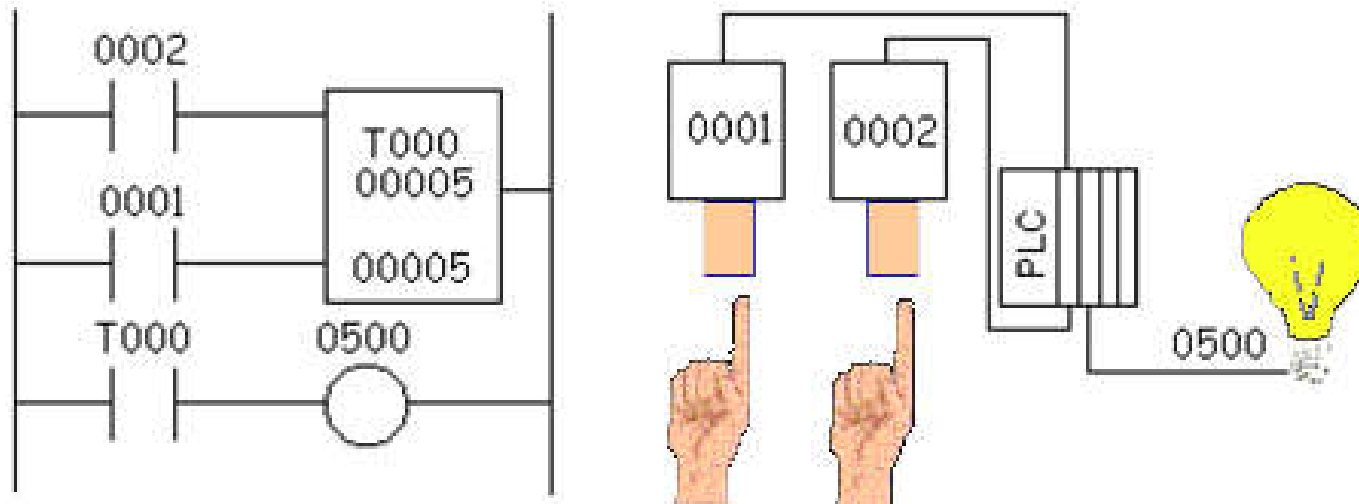(search this function on Schneider PLCs or discuss implementation)



T000 = retentive timer

0002 = push button (counted while ON)

0001 = reset push button

0500 = lamp output

Ladder diagram

Example:

- SW ON to start operation
- Before motor starts, lubricate 10 s with oil.
- SW OFF to stop. (lubricate 15 s more).
- After 3 hours of pump operation, stop motor and signal with pilot light.
- Reset available after servicing.

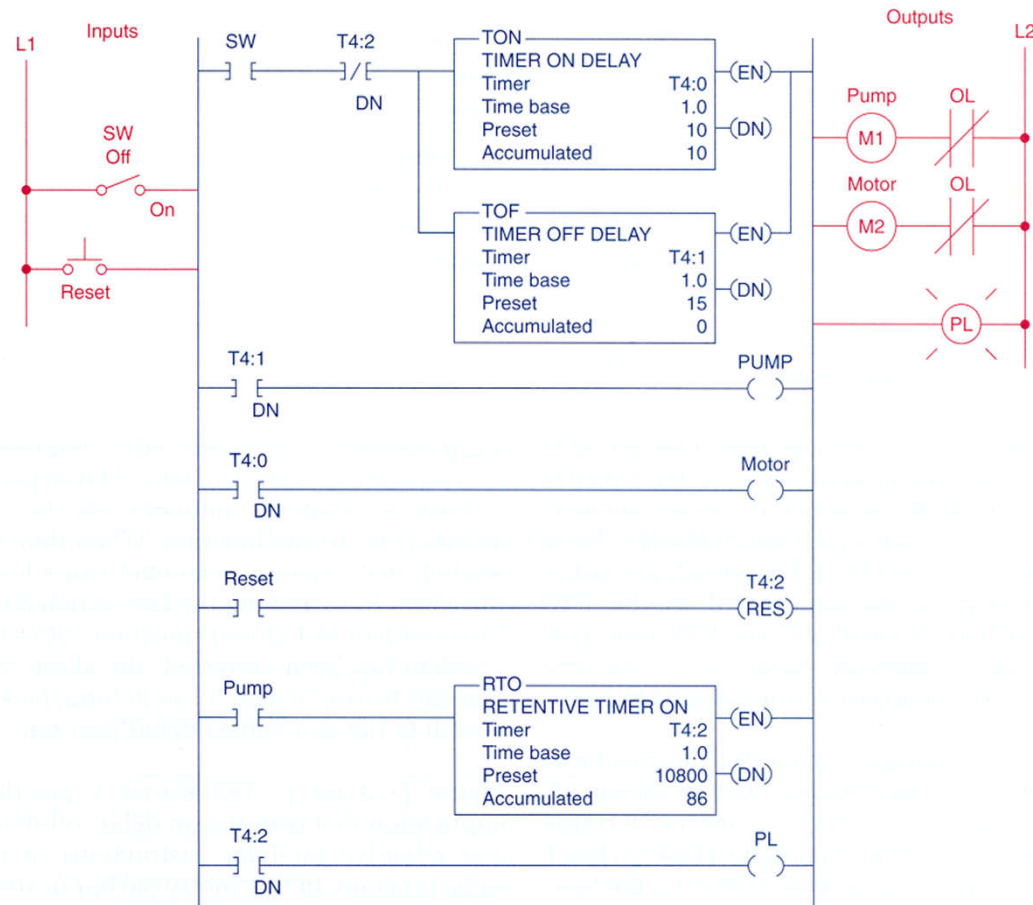


Fig. 7-23
Bearing lubrication program.

Ladder diagram

Cascaded Timers

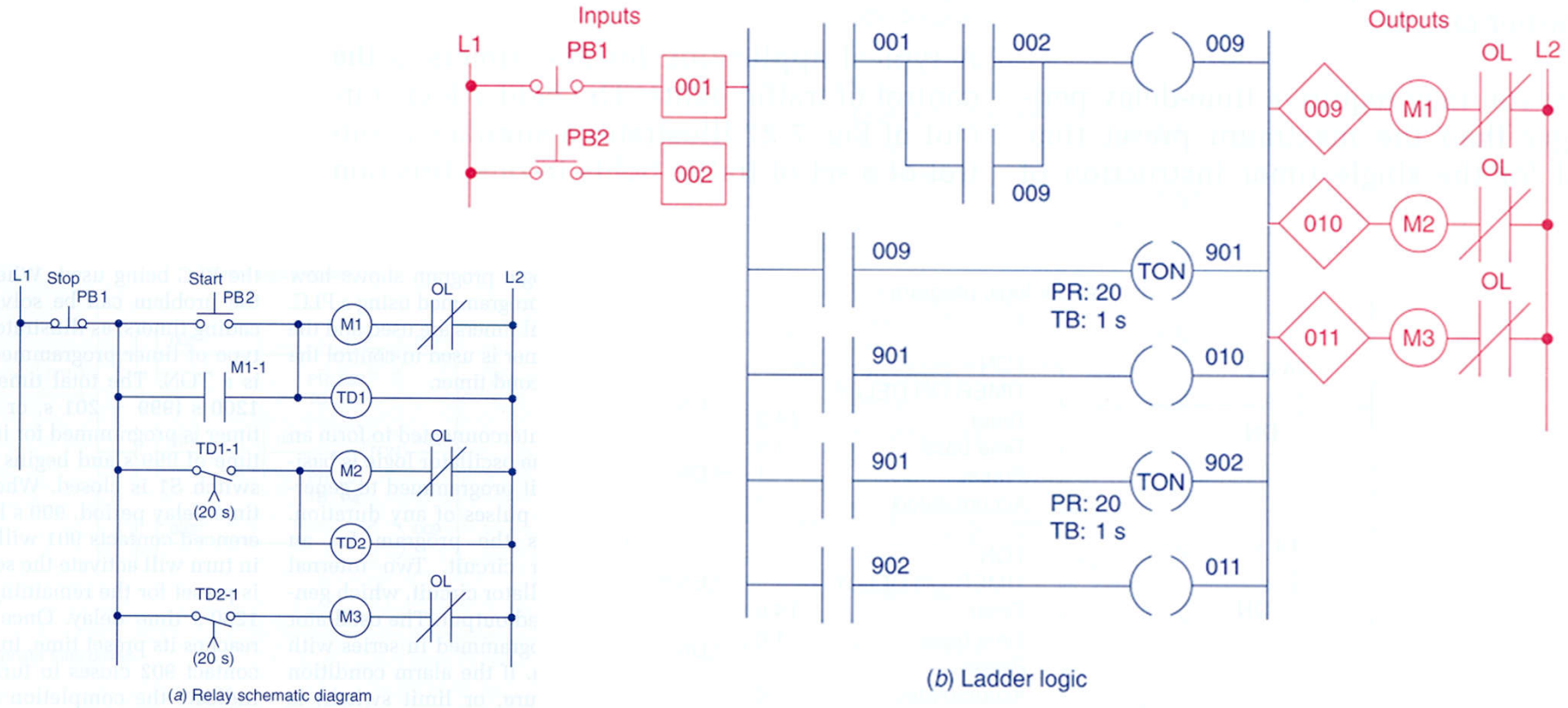


Fig. 7-24

Sequential time-delayed motor-starting circuit.

Start 3 motors

T=0, t=20, t=40sec

Ladder diagram

Cascaded Timers (bistable system)

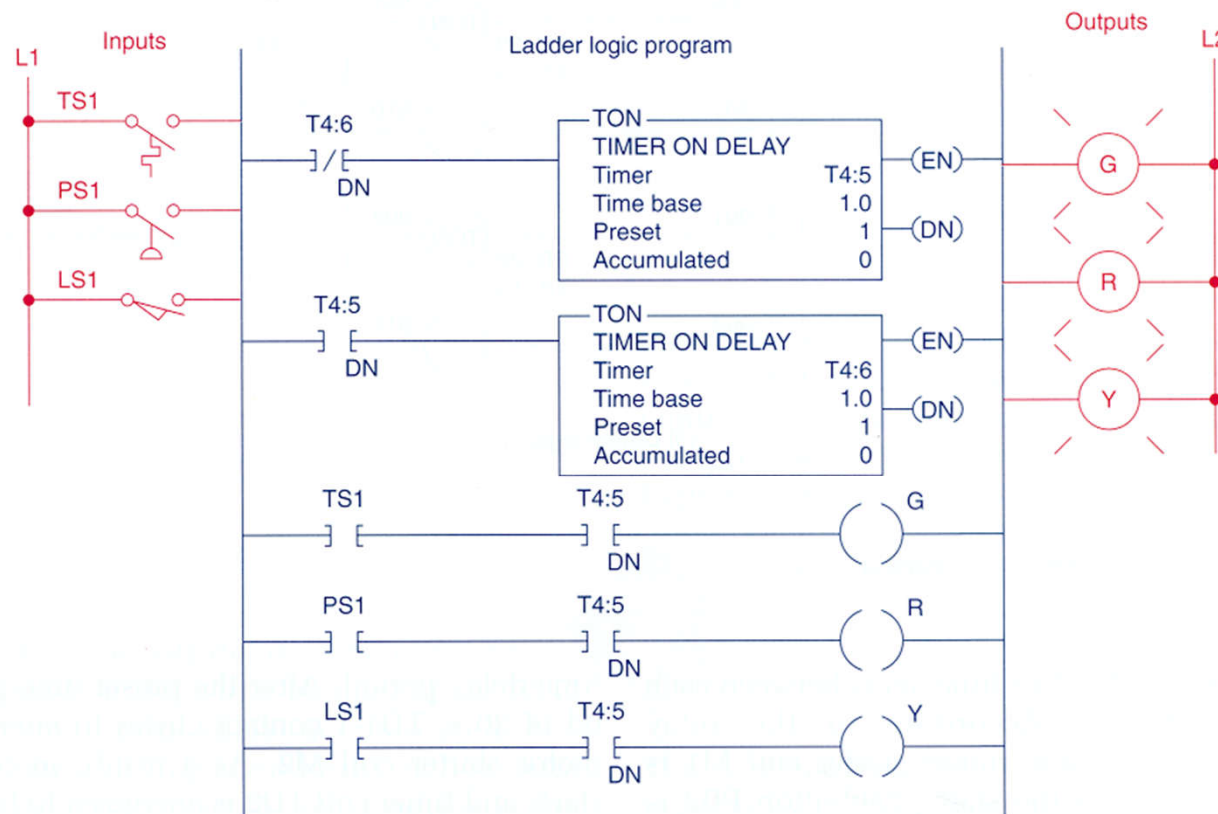


Fig. 7-25

Annunciator flasher program.

Ladder diagram

Timers for very long time intervals

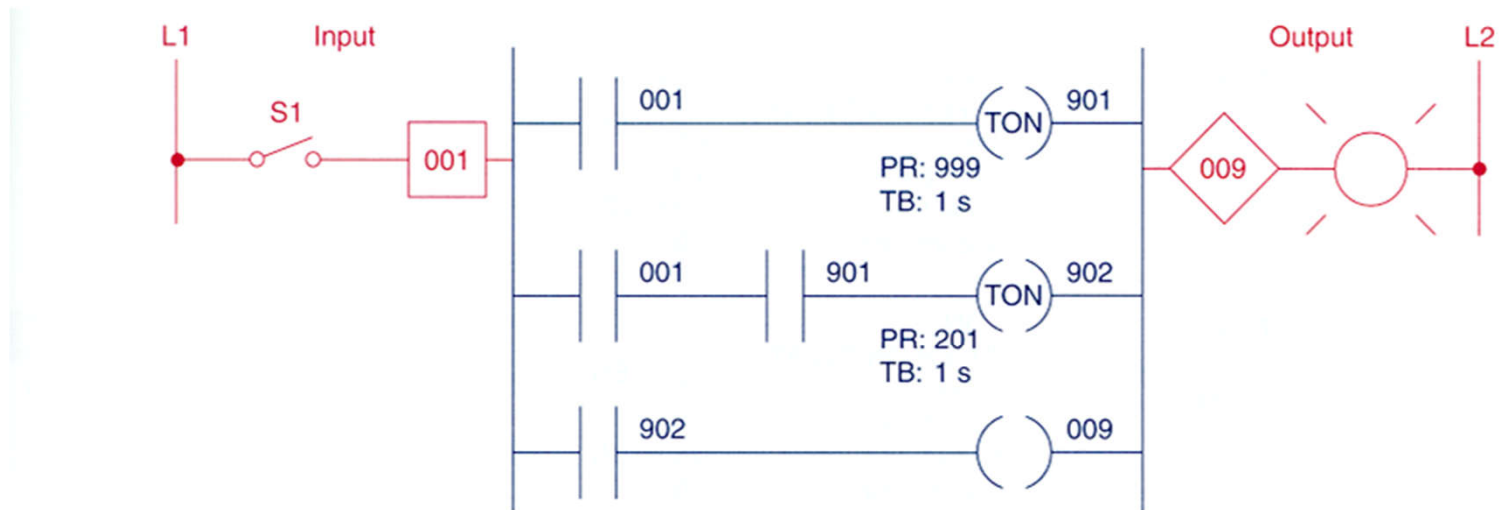


Fig. 7-26

Cascading of timers for longer time delays.

Ladder diagram

Example of a semaphore

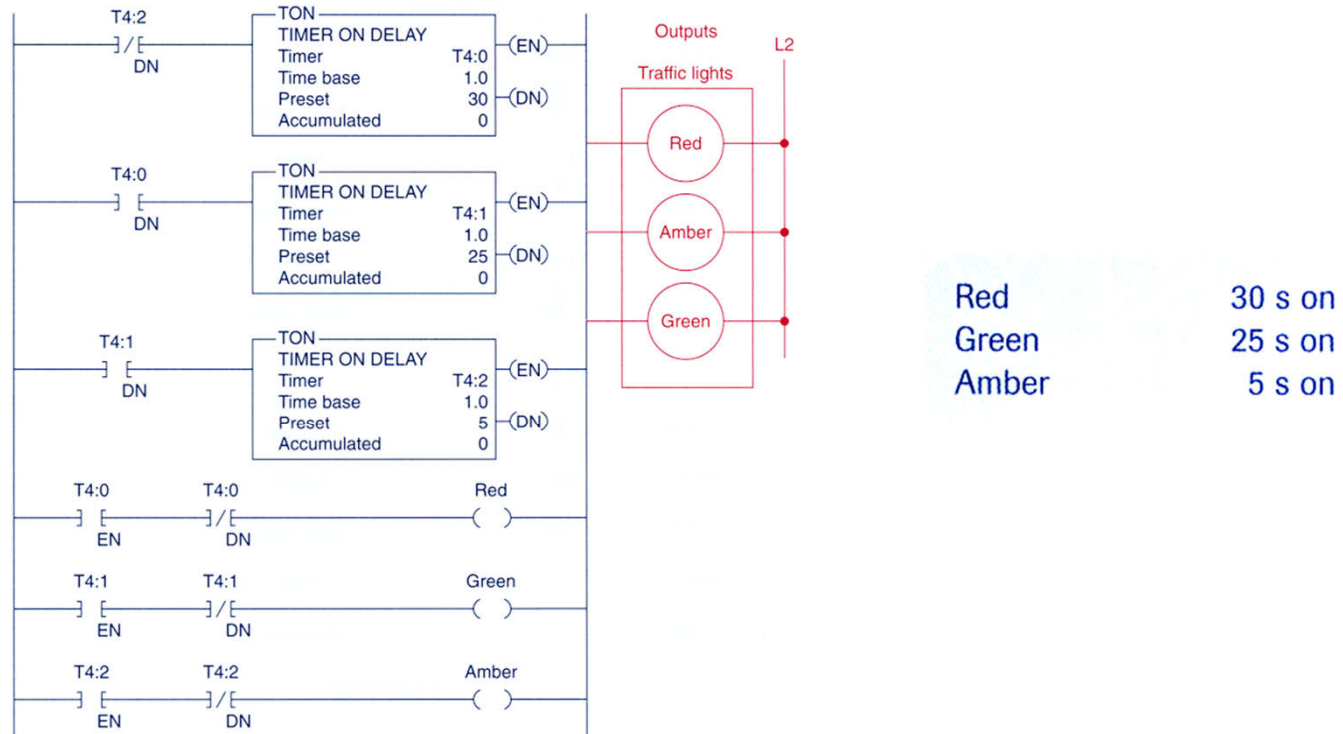


Fig. 7-27

Control of traffic lights in one direction.

Example of a semaphore in both directions

Red	30 s on
Green	25 s on
Amber	5 s on




(b) Timing chart

Fig. 7-28 (continued)

Control of traffic lights in two directions.

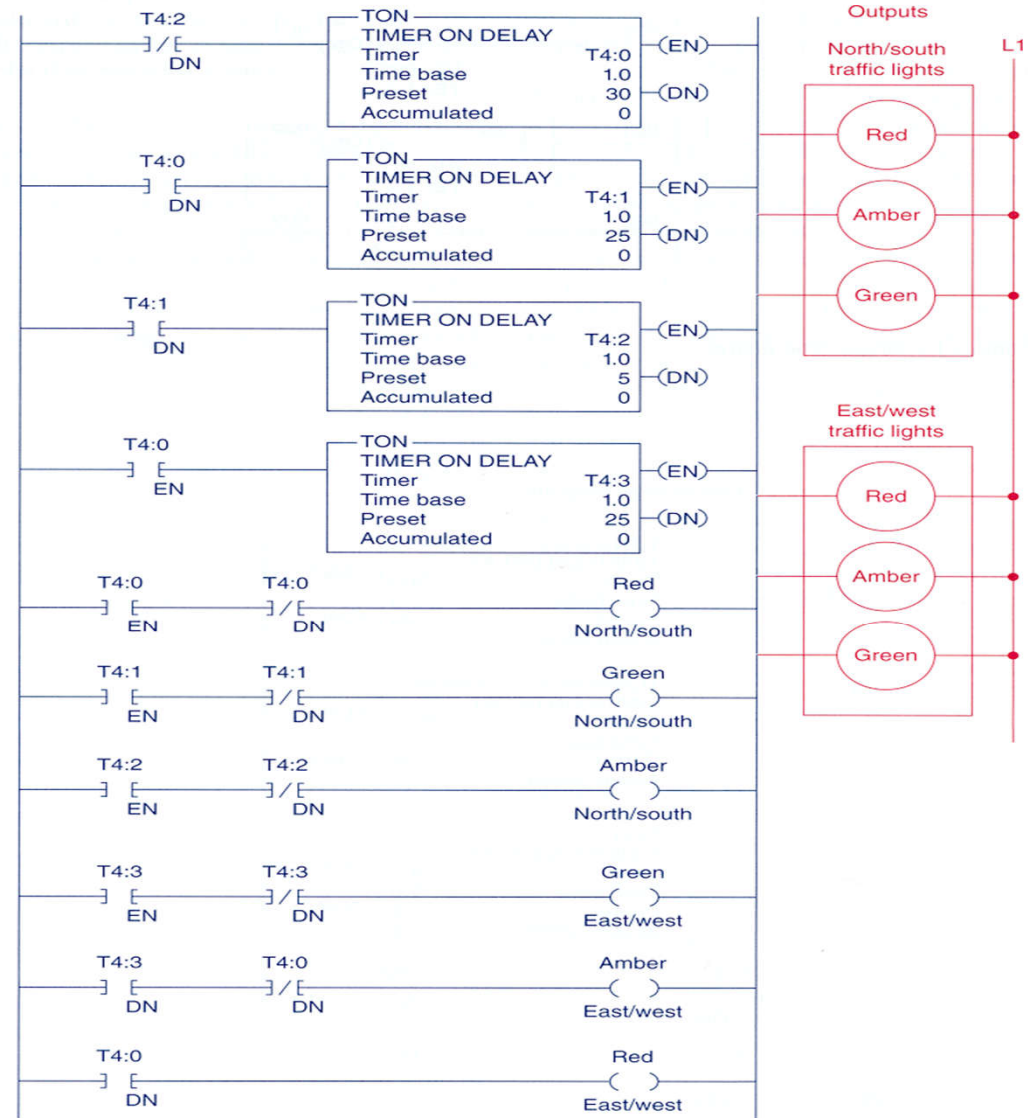Example of a semaphore in both directions



(a) Ladder logic

Fig. 7-28
Control of traffic lights in two directions.

Ladder diagram

Counters



Some applications...


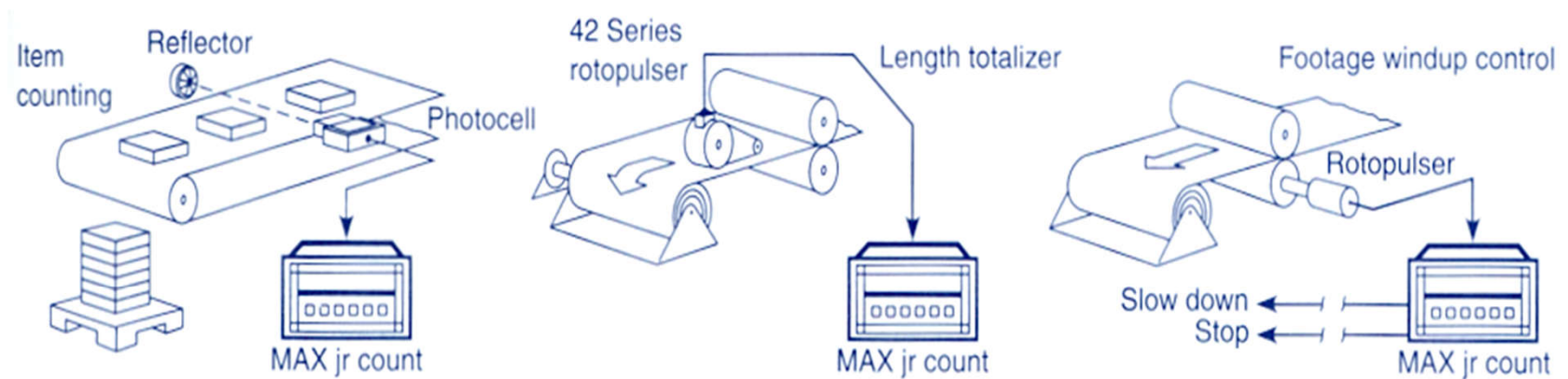


Fig. 8-3


Counter applications. (Courtesy of Dynapar Corporation, Gurnee, Illinois.)

Ladder diagram

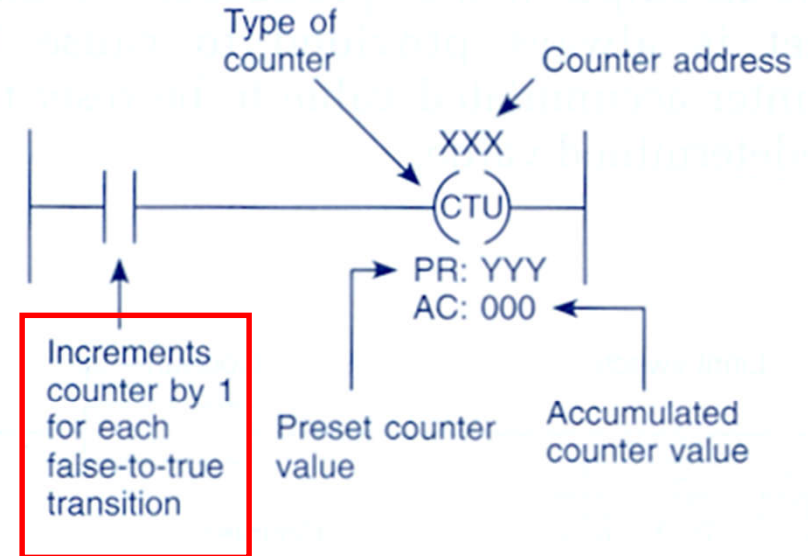Implementation of Counters in the PLC-5 of Allen-Bradley:



Internal structure representation

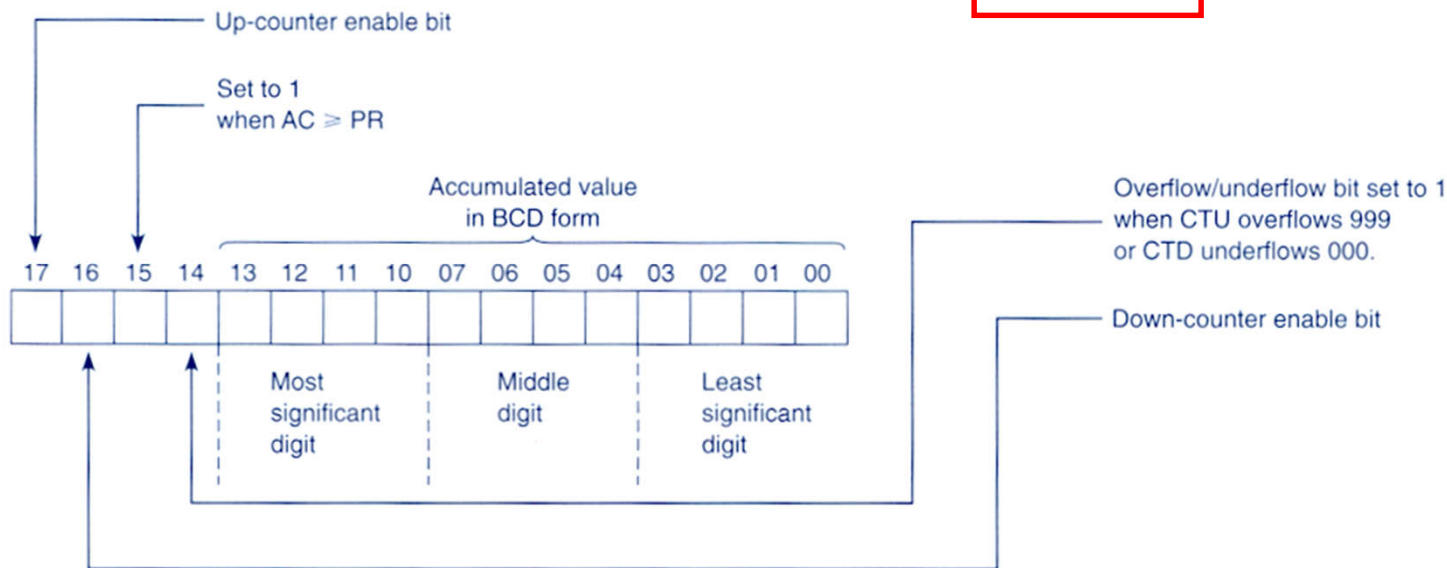


(b) Allen-Bradley PLC-2 timer accumulated value word (bit addressing is in octal)


Ladder diagram

Implementation of Counters in the PLC-5 of Allen-Bradley:

Two alternative representations:

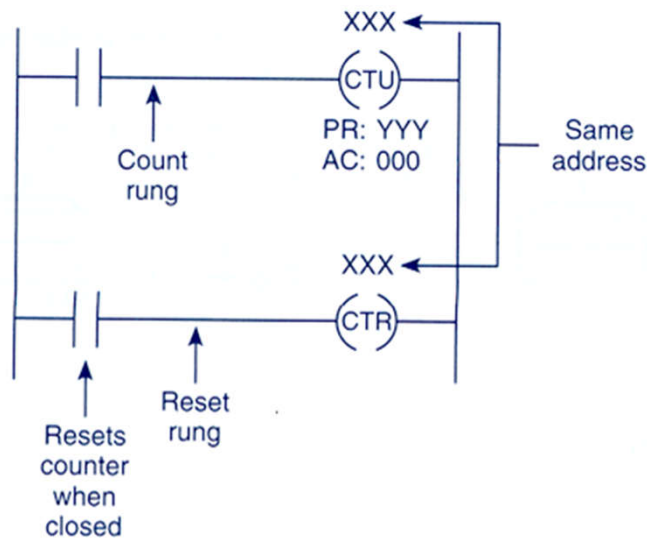


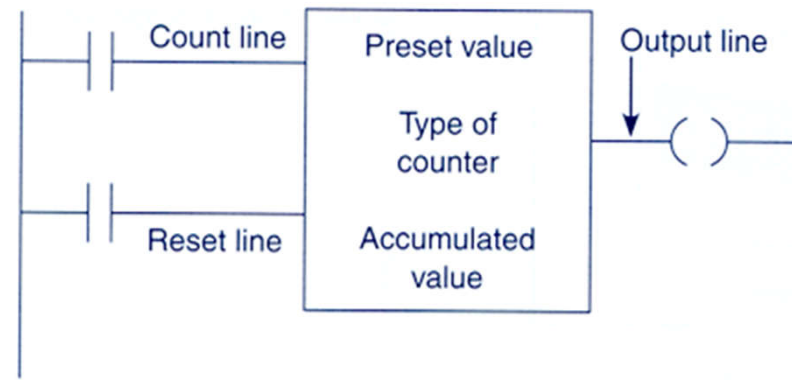
Coil-formatted counter and reset instructions



Block-formatted counter instruction

Ladder diagram

Up-counters

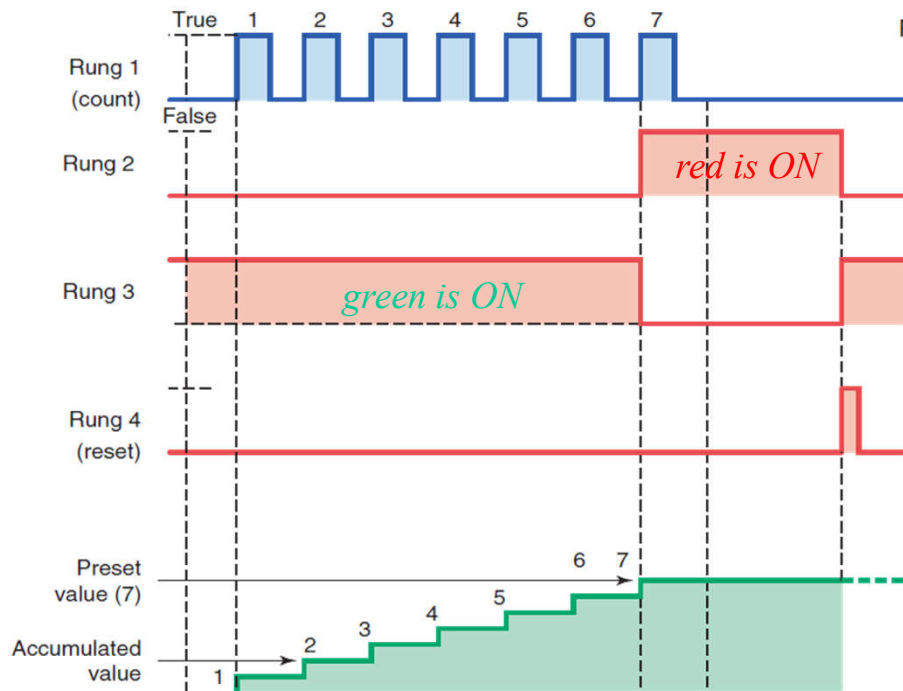
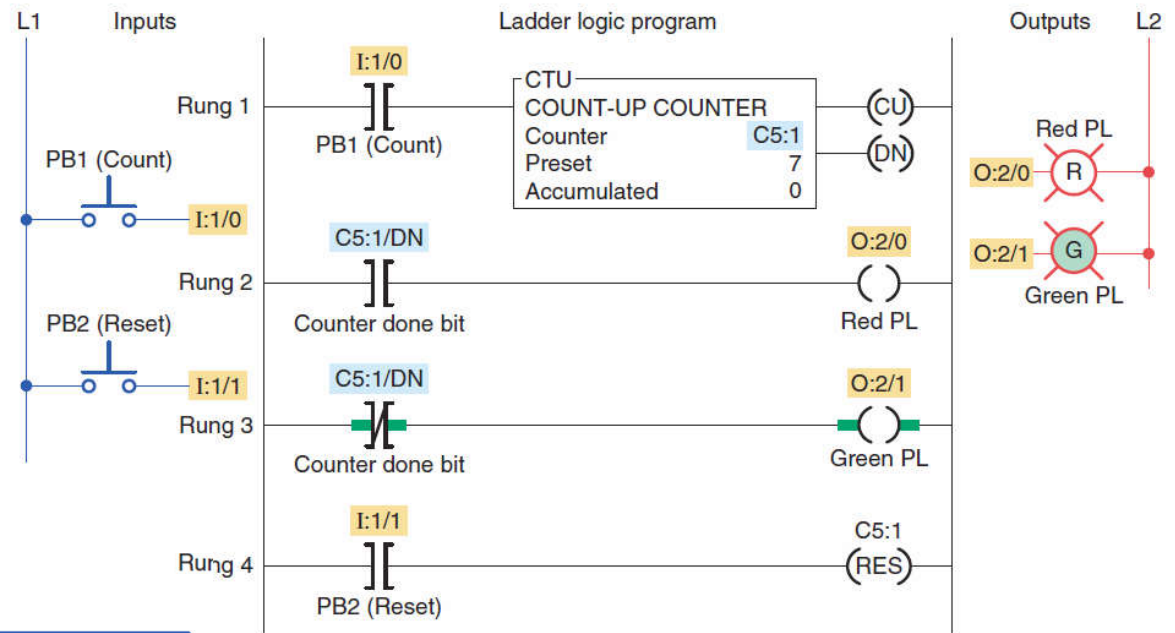


Usage of an **incremental up-counter** and the corresponding **temporal diagram:**

PB1 increments counting
PB2 resets the counting


Ladder diagram

Example:
Counting parts

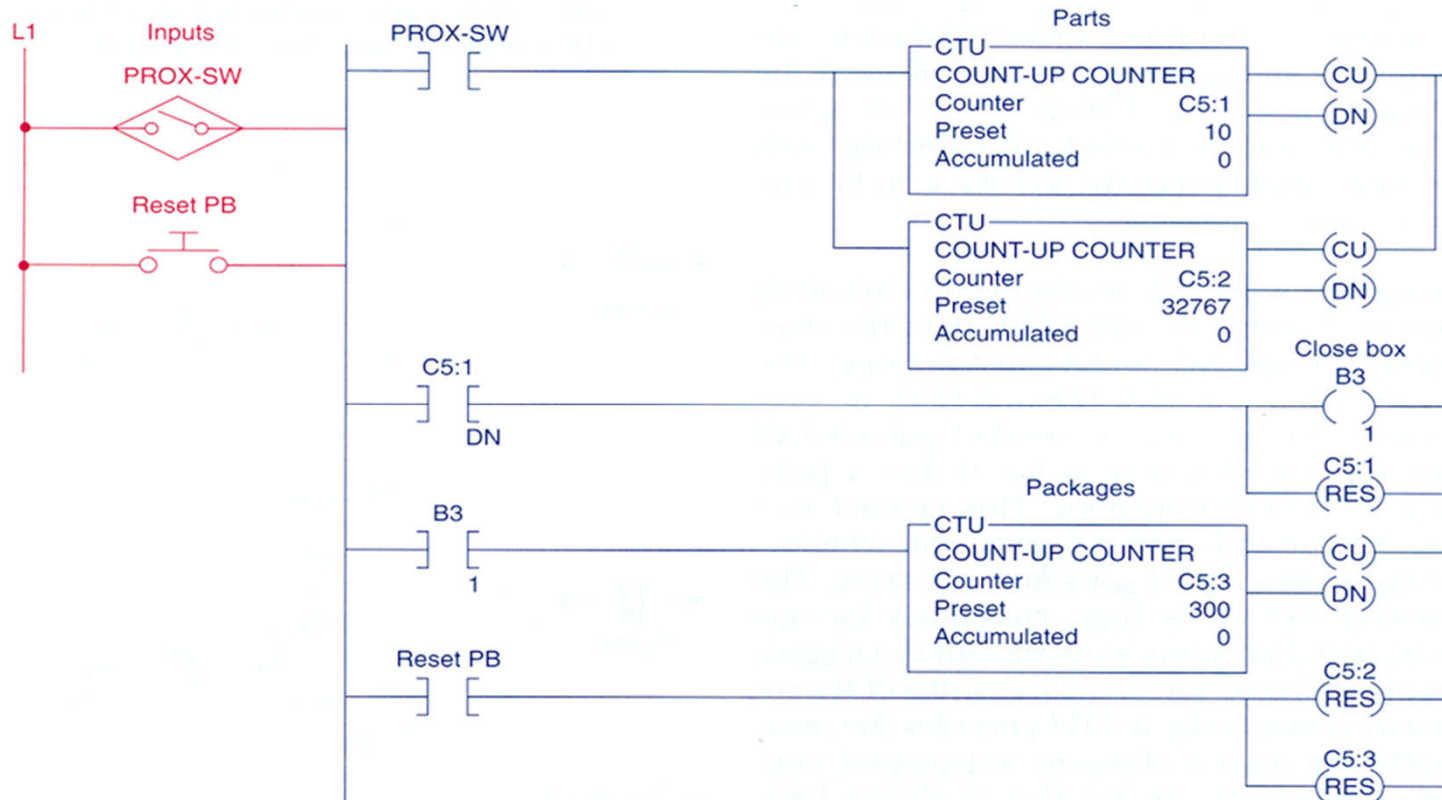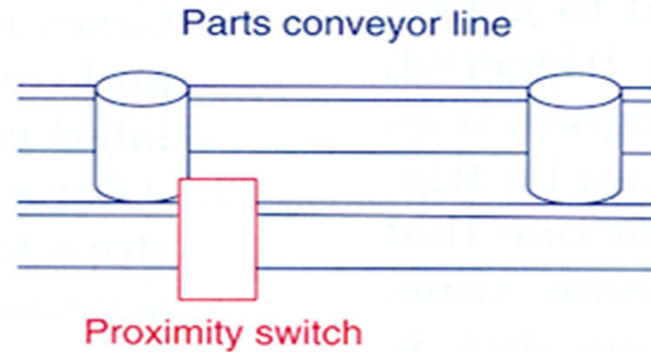


Ladder diagram

Example

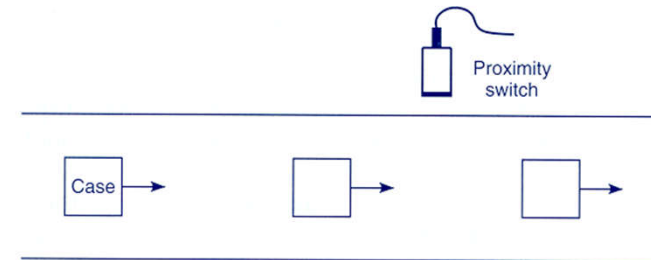

(a) Process flow diagram

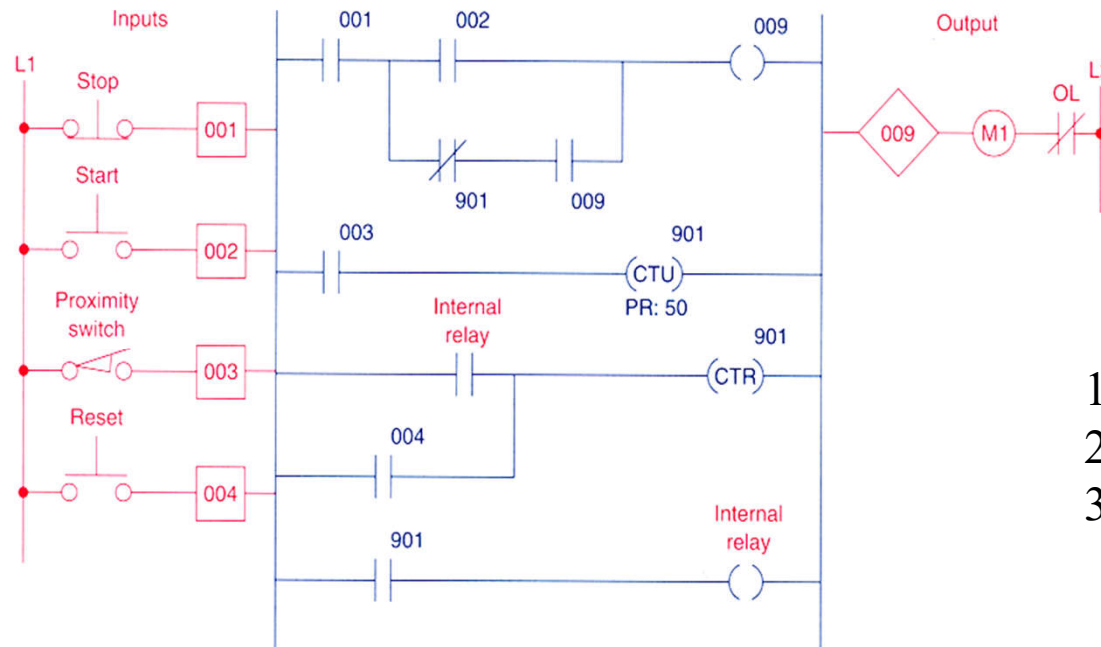

(b) Program


1. Start conveyor motor
2. Passing cases increment counter
3. After 50 cases, stop motor

Fig. 8-13

Conveyor motor program.

Ladder diagram

Up/down-counters

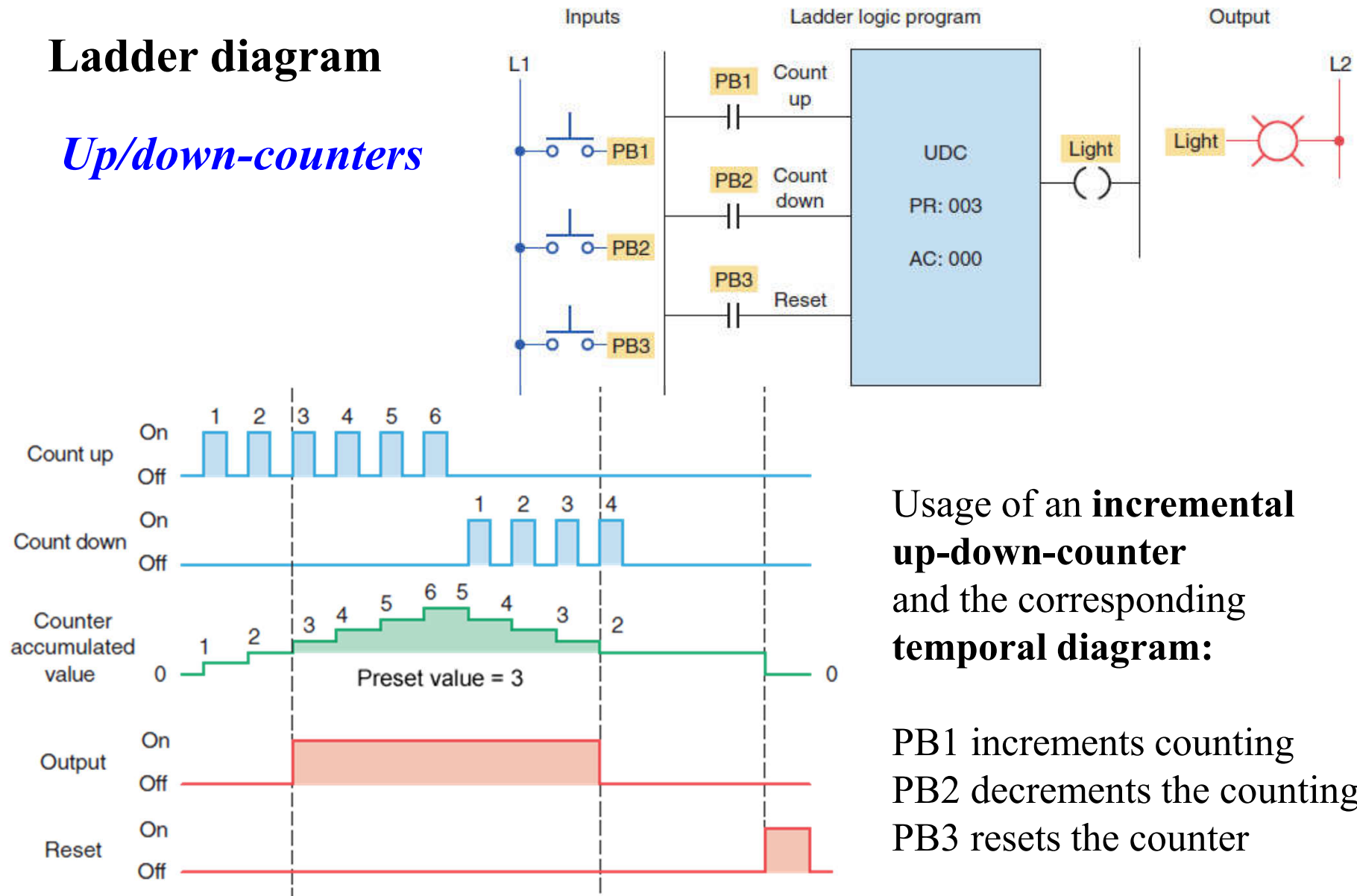

Usage of an **incremental up-down-counter** and the corresponding **temporal diagram**:

PB1 increments counting
 PB2 decrements the counting
 PB3 resets the counter

Ladder diagram

Up/down-counters

Example:

Finite parking garage

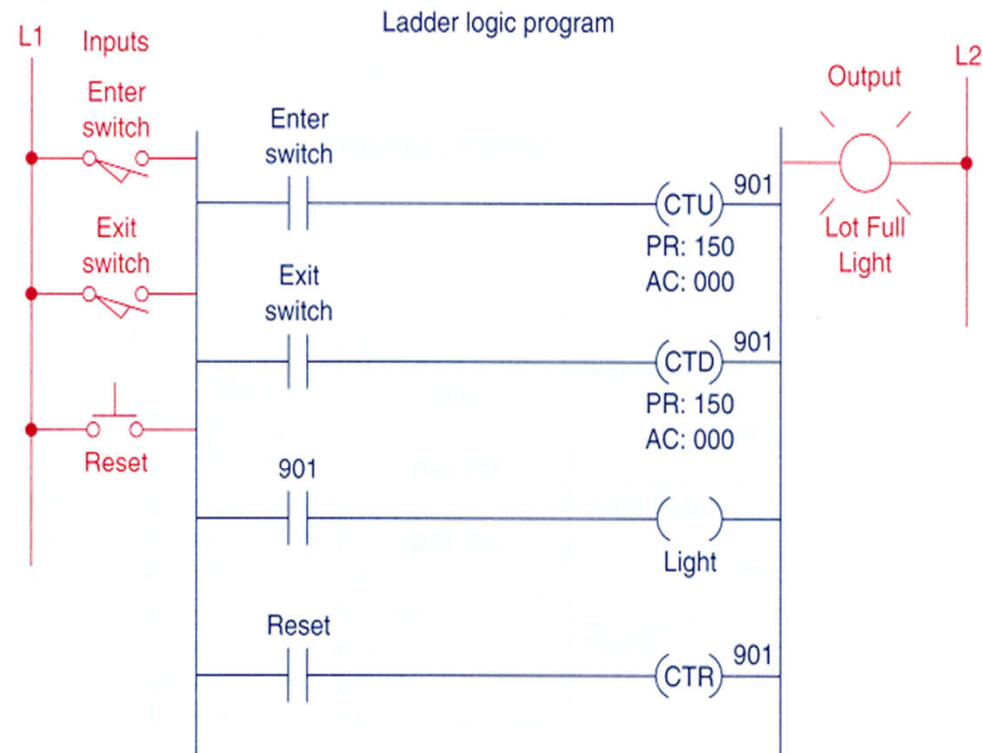


Fig. 8-17

Parking garage counter.

Ladder diagram

Cascaded Counters

Example:

24 hours clock

Note “auto-reset” of counters after “count-done”.

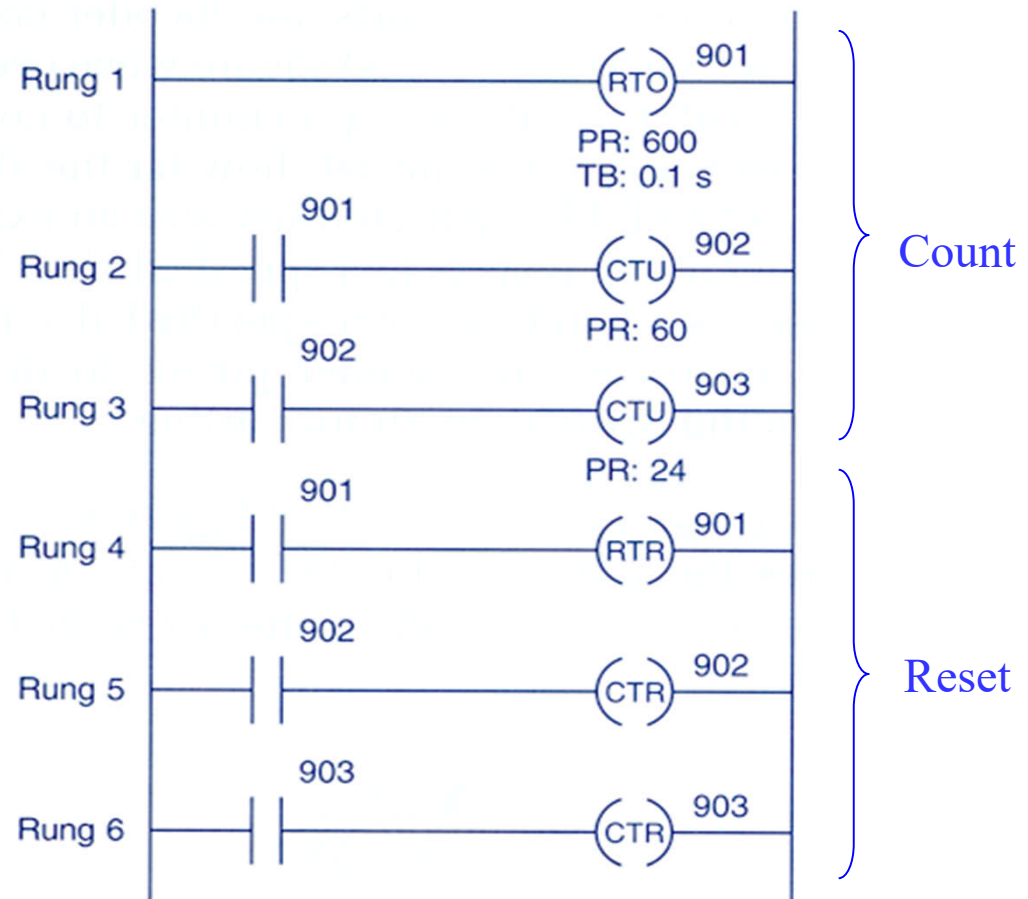


Fig. 8-23

A 24-h clock program.

Ladder diagram

Cascaded Counters

Example:

Memory time of event
Internal relay OFF stops clock

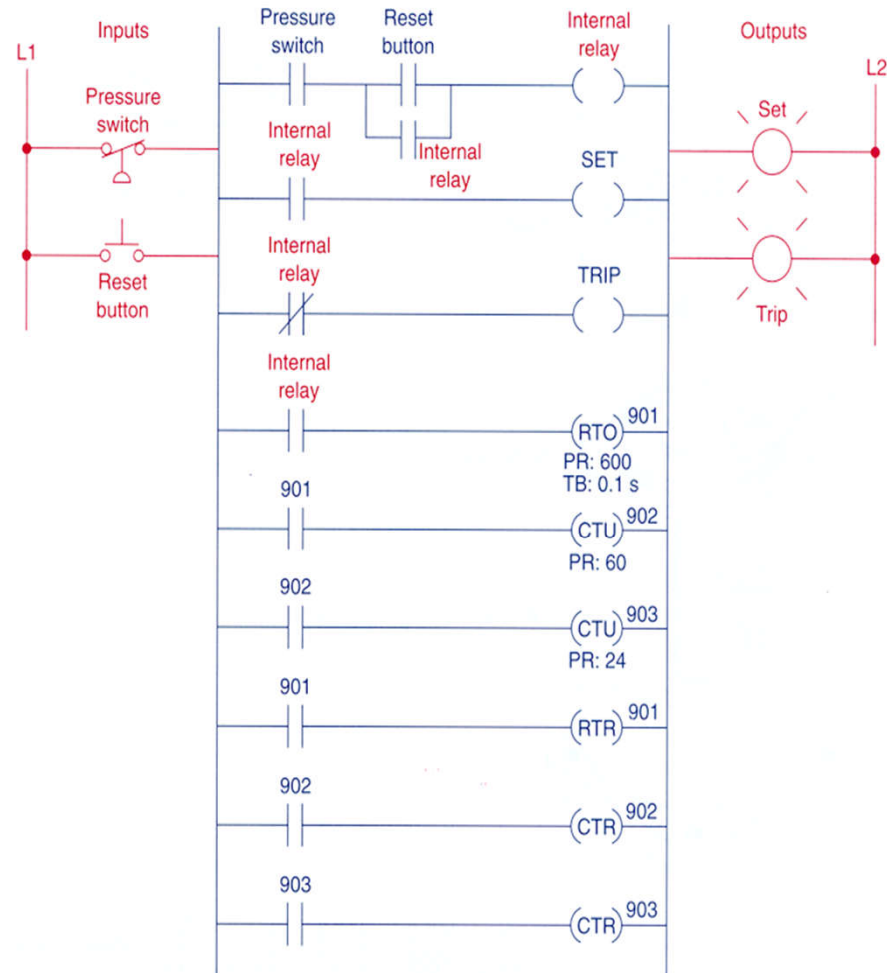


Fig. 8-24
 Program for monitoring the time of an event.

Ladder diagram

Incremental Encoder

counter measures **rotation angle** or **rotation speed** (if divided by time)

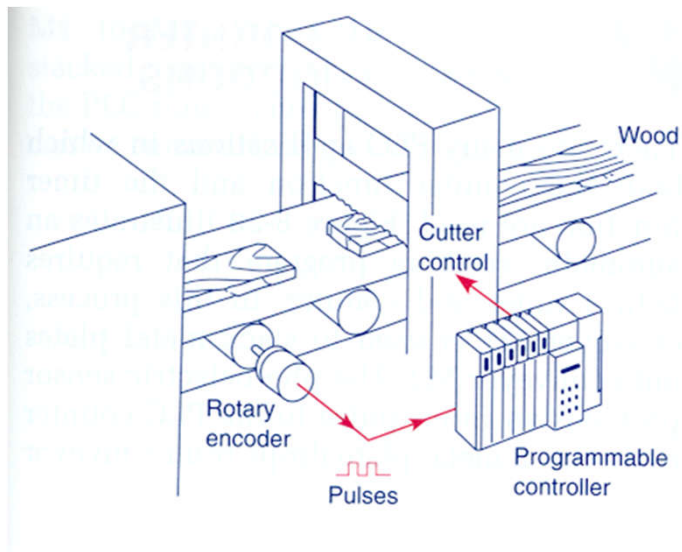


Fig. 8-26

Cutting objects to a specified size.

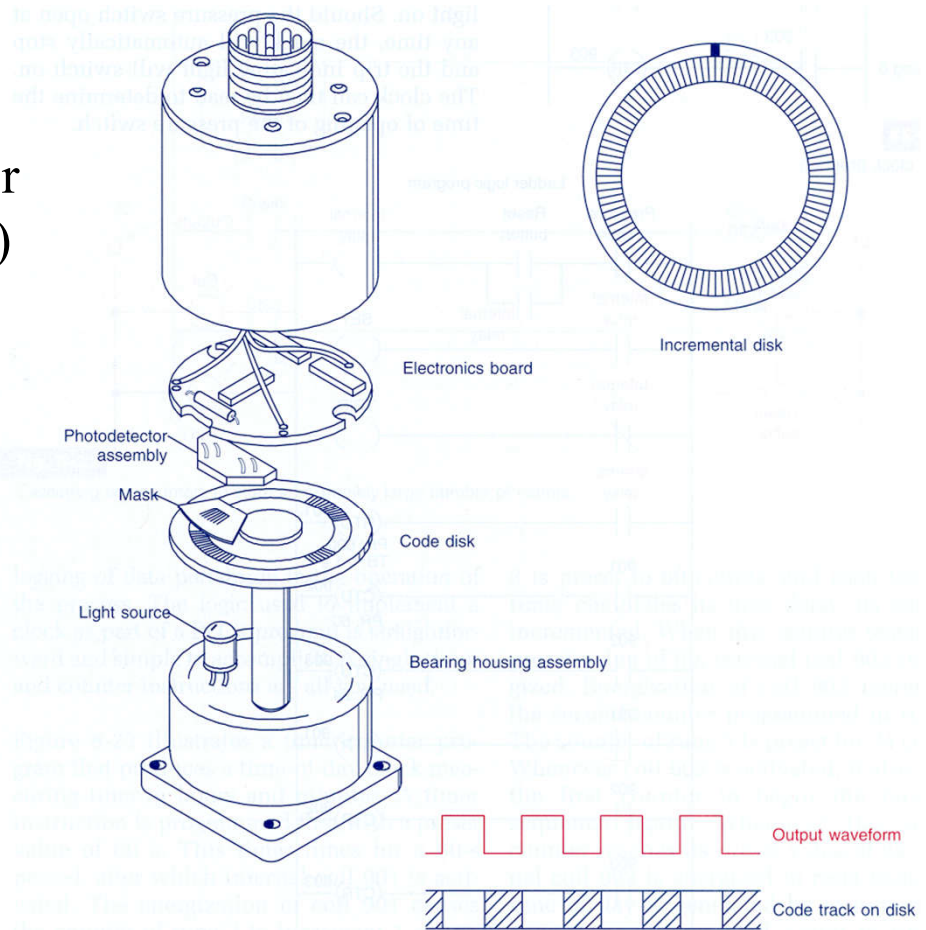



Fig. 8-25

Incremental encoder. (Courtesy of BEI Motion Systems Company.)


Ladder diagram

Incremental *Encoder*

Example:
counter as a "length sensor"

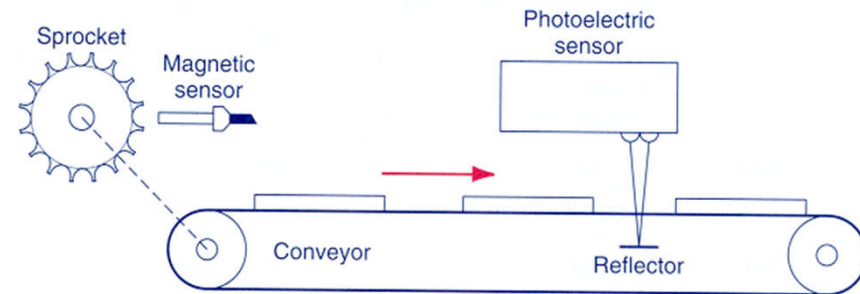

(a) Process

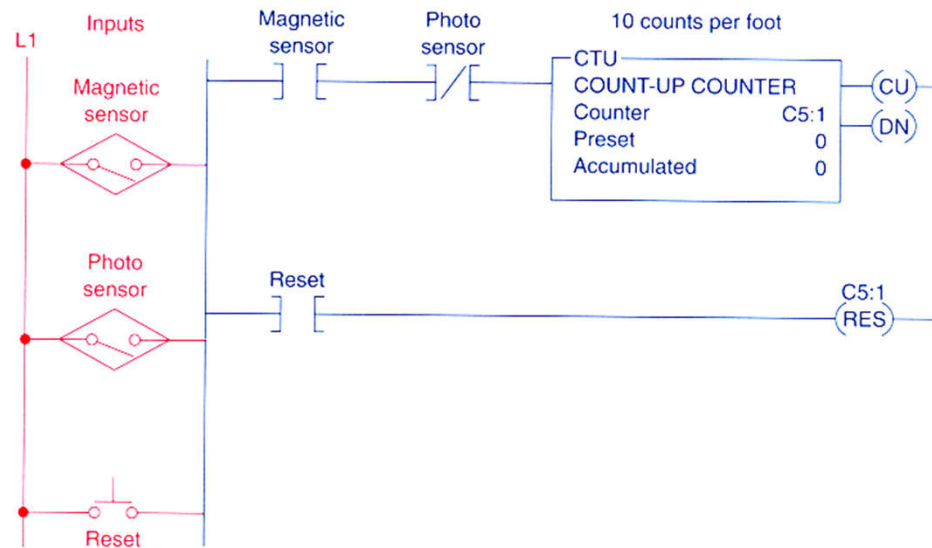

(b) Program

Fig. 8-27


Counter used for length measurement.

Ladder diagram

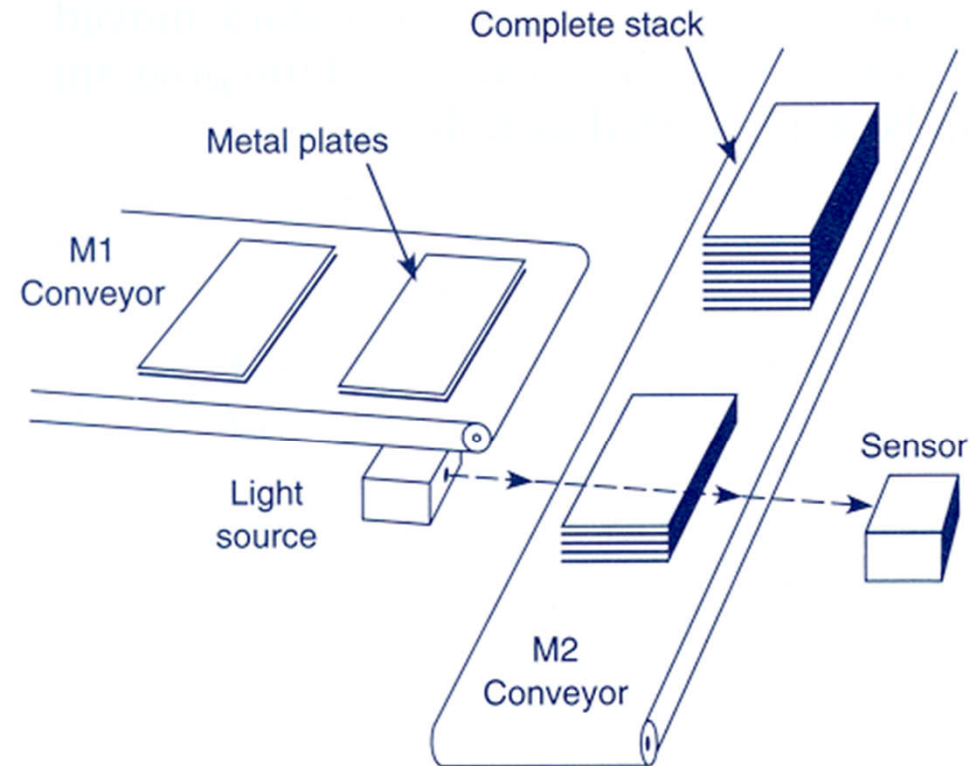Example with counters and timers (cont.):

Specs:

- Starts M1 conveyor upon pushing button .
- After 15 plates stops M1 and starts conveyor M2 .
- M2 operates for 5 seconds and then stops.
- Restart sequence.



(a) Process

Ladder diagram

Example with counters and timers (cont.):

Specs:

- Starts M1 conveyor upon pushing button .
- After 15 plates stops M1 and starts conveyor M2 .
- M2 operates for 5 seconds and then stops.
- Restart sequence.

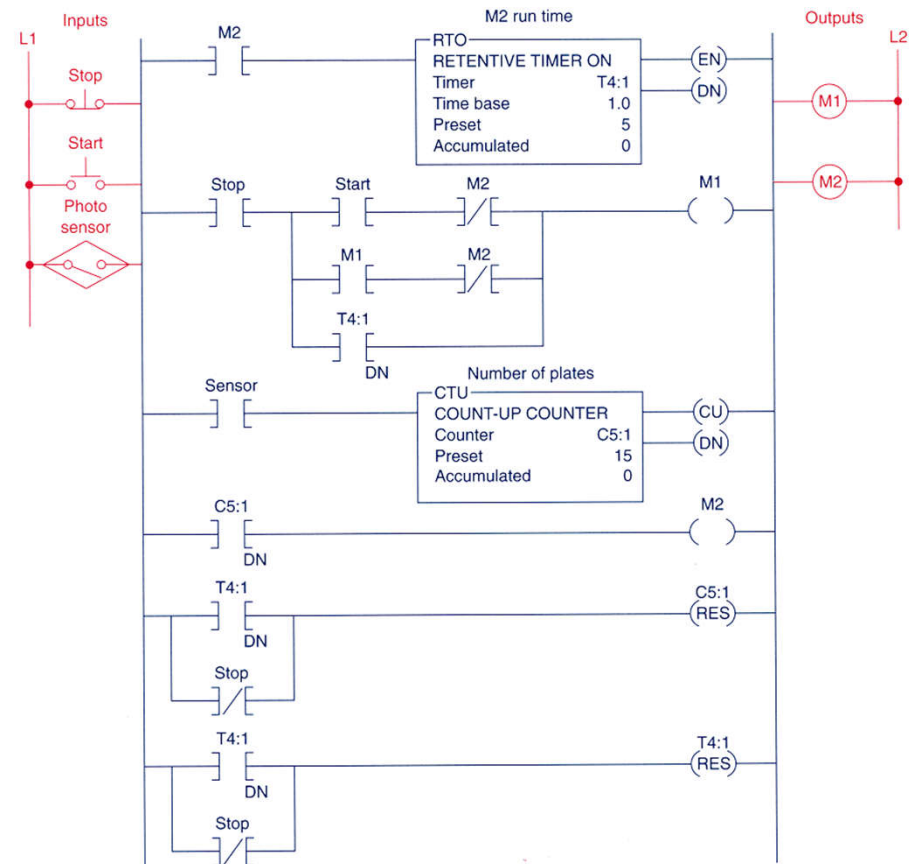


Fig. 8-28

Automatic stacking program.

(b) Program

Ladder diagram

Example with counters and timers (cont.):

Specs:

- Starts M1 conveyor upon pushing button .
- After 15 plates stops M1 and starts conveyor M2 .
- M2 operates for 5 seconds and then stops.
- Restart sequence.

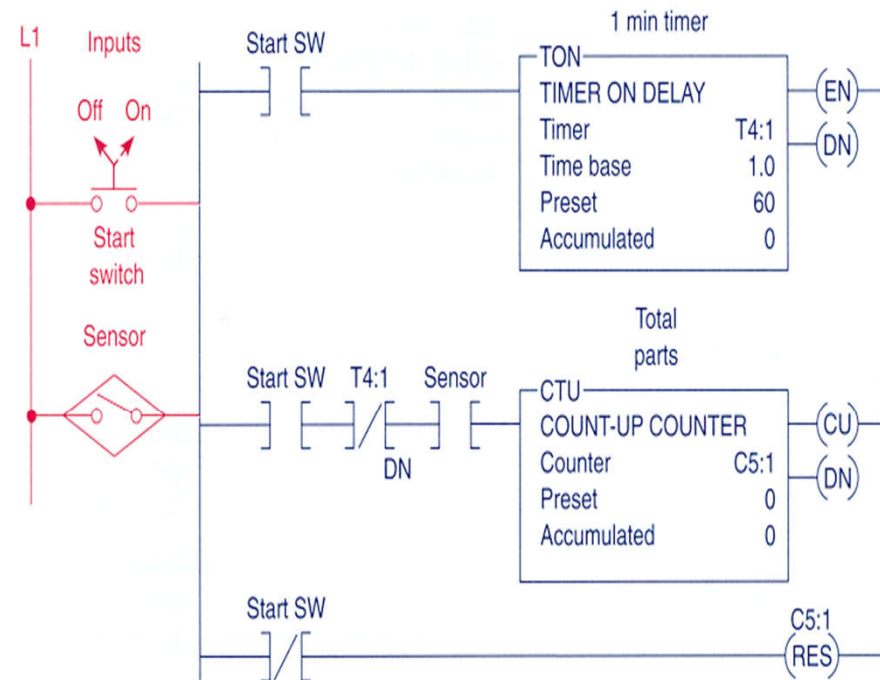


Fig. 8-30

Product flow rate program.

Ladder diagram

Example with counters and timers (cont.):

To use a timer to command a counter, to implement large periods of time.

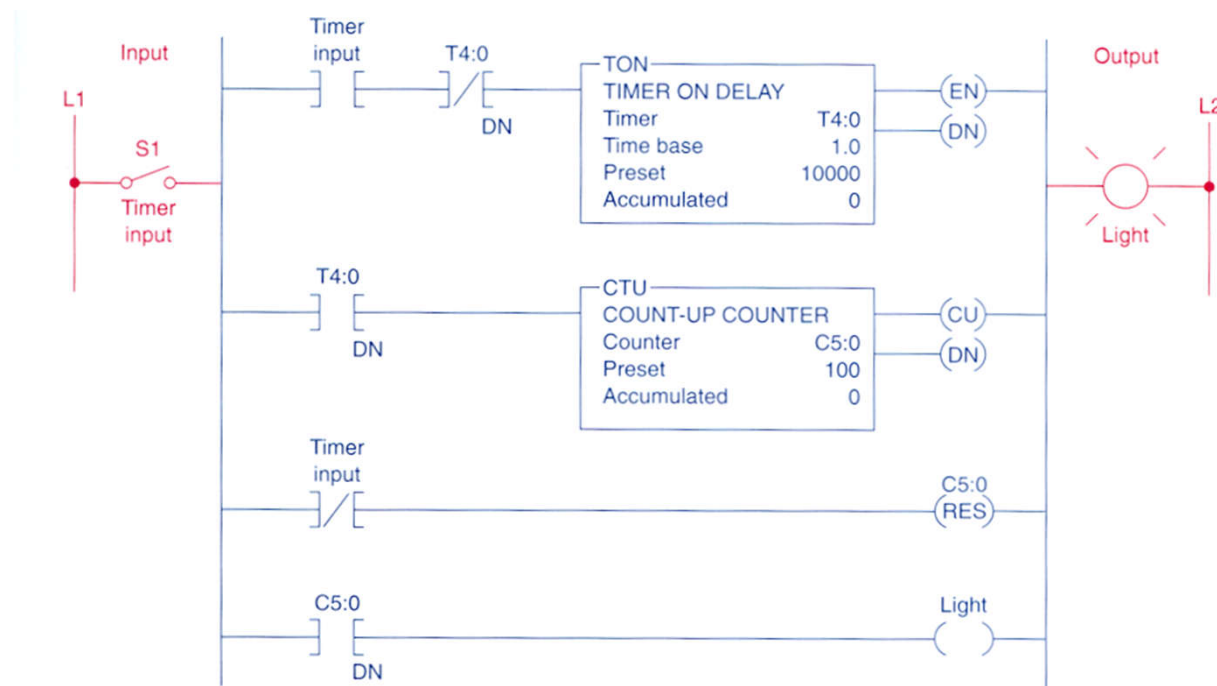



Fig. 8-31

Timer driving a counter to produce an extremely long time-delay period.

Ladder diagram


Counters

Example:

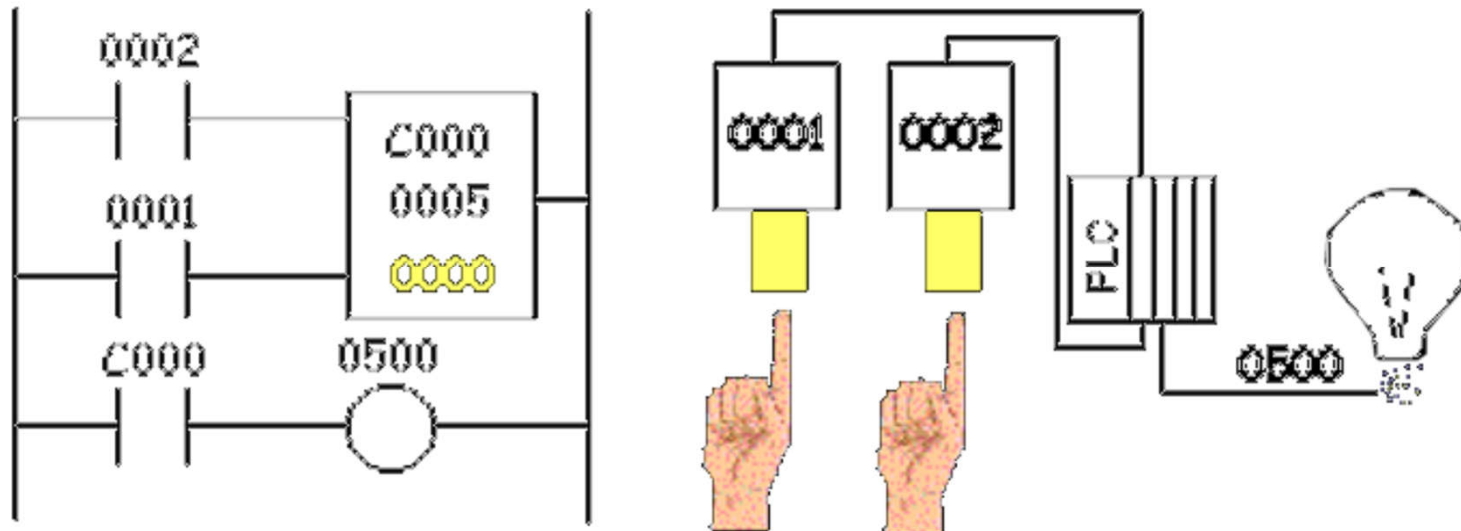

Ladder diagram

Counters in PL7

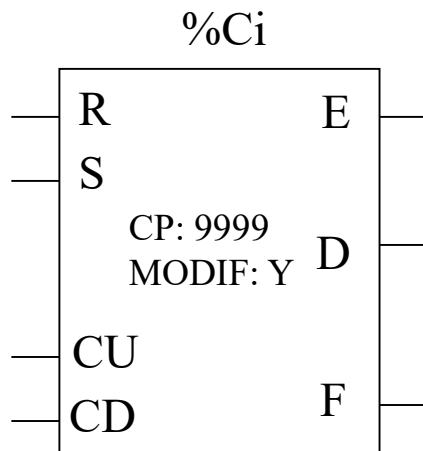


Characteristics:

Identifier: %Ci	0..31 in the TSX37
Value progr.:	%Ci.P 0...9999 (def.)
Value Actual:	%Ci.V 0...Ci.P (only to be read)
Modifiable:	Y/N can be modified from the console
Inputs:	R Reset Ci.V=0 S Preset Ci.V=Ci.P CU <i>Count Up</i> CD <i>Count Down</i>
Outputs:	E Overrun %Ci.E=1 %Ci.V=0->9999 D Done %Ci.D=1 %Ci.V=Ci.P F Full %Ci.F=1 %Ci.V=9999->0

Ladder diagram


Counters in Unity Pro

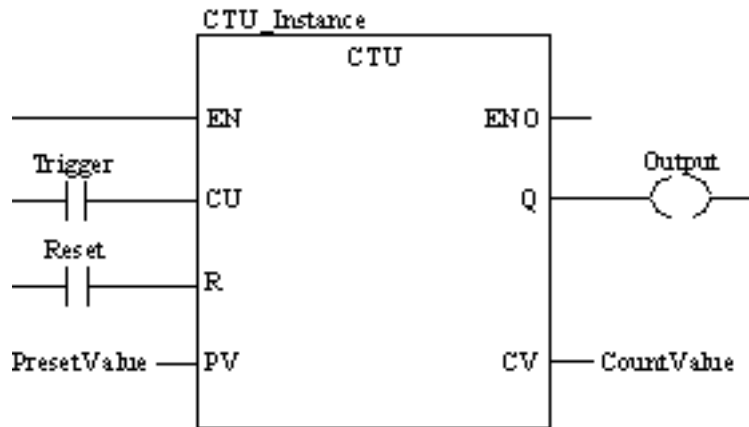

CU "0" to "1" => CV is incremented by 1

CV ≥ PV => Q:=1

R=1 => CV:=0

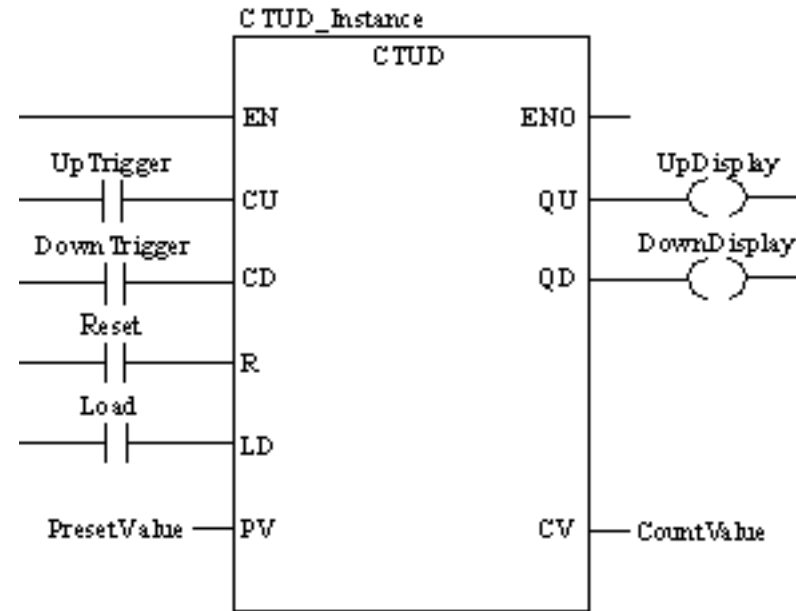

CU "0" to "1" => CV is incremented by 1

CD "0" to "1" => CV is decremented by 1

CV ≥ PV => QU:=1

CV ≤ 0 => QD:=1

R=1 => CV:=0 **LD=1** => CV:=PV

R has precedence over LD

NOTE: counters are saturated such that no overflow occurs

Ladder diagram

Numerical Processing


Algebraic / Arithmetic and Logic Functions

Note:

- %M memory
- %K constant
- %S system

Compare block →

Operate block →

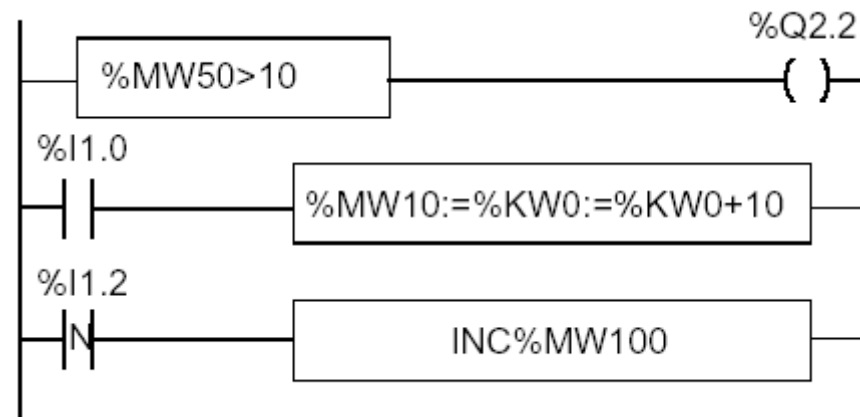

Ladder diagram

Numerical Processing

Arithmetic Functions

+	addition of two operands	SQRT	square root of an operand
-	subtraction of two operands	INC	incrementation of an operand
*	multiplication of two operands	DEC	decrementation of an operand
/	division of two operands	ABS	absolute value of an operand
REM	remainder from the division of 2 operands		

Operands


Type	Operand 1 (Op1)	Operand 2 (Op2)
Indexable words	%MW	%MW,%KW,%Xi.T
Non-indexable words	%QW,%SW,%NW,%BLK	Imm.Val.,%IW,%QW,%SW,%NW,%BLK, Num.expr.
Indexable double words	%MD	%MD,%KD
Non-indexable double words	%QD,%SD	Imm.Val.,%ID,%QD,%SD, Numeric expr.

Ladder diagram

Numerical Processing

Example:

Arithmetic functions

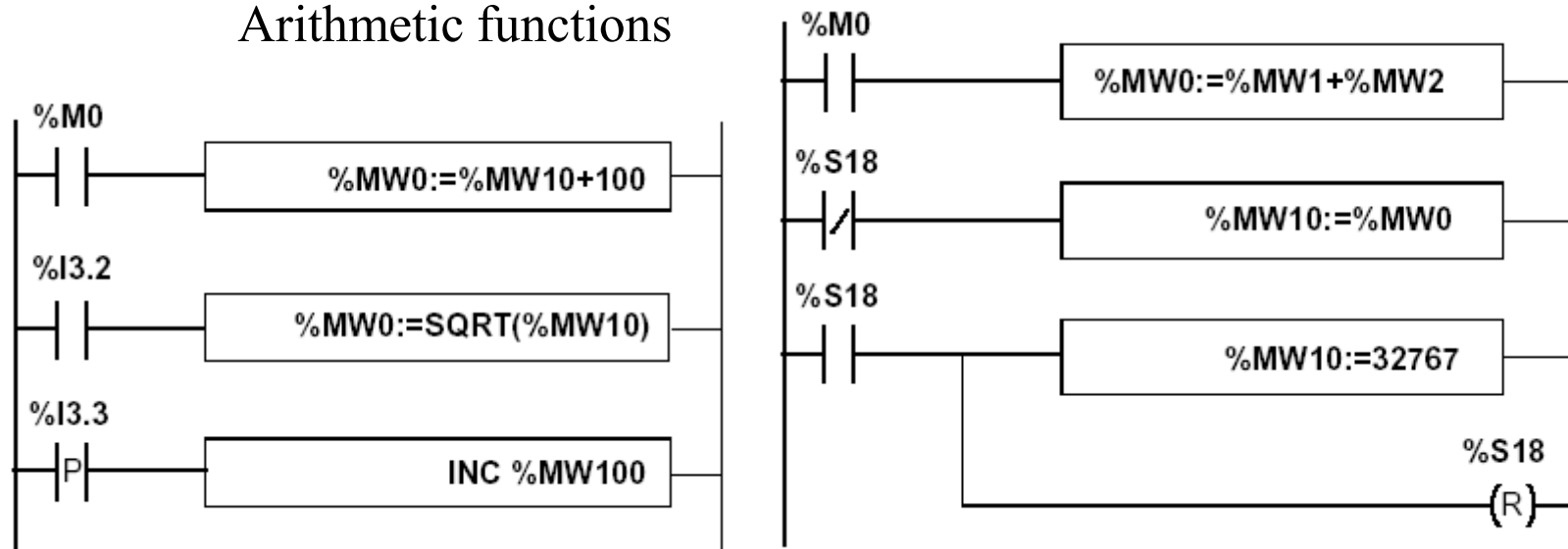

Use of a system variable:

`%S18` – flag de overflow

Ladder diagram

Numerical Processing

Logic Functions

AND	AND (bit by bit) between two operands
OR	logical OR (bit by bit) between two operands
XOR	exclusive OR (bit by bit) between two operands
NOT	logical complement (bit by bit) of an operand

Comparison instructions are used to compare two operands.

- >: tests whether operand 1 is greater than operand 2,
- >=: tests whether operand 1 is greater than or equal to operand 2,
- <: tests whether operand 1 is less than operand 2,
- <=: tests whether operand 1 is less than or equal to operand 2,
- =: tests whether operand 1 is different from operand 2.

Operands


Type	Operands 1 and 2 (Op1 and Op2)
Indexable words	%MW, %KW, %Xi.T
Non-indexable words	Imm.val., %IW, %QW, %SW, %NW, %BLK, Numeric Expr.
Indexable double words	%MD, %KD
Non-indexable double words	Imm.val., %ID, %QD, %SD, Numeric expr.

Ladder diagram

Numerical Processing

Example:

Logic functions

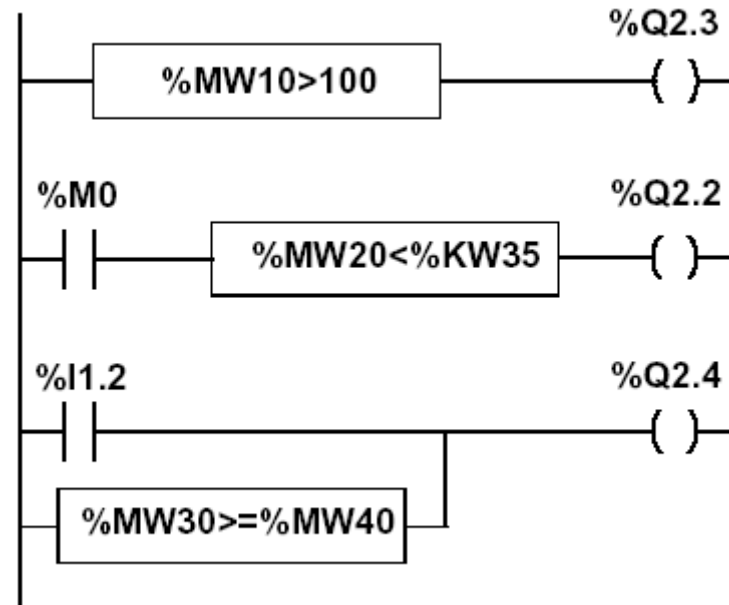

Ladder diagram

Numerical Processing

Priorities on the execution of the operations

Rank	Instruction
1	Instruction to an operand
2	*,/,REM
3	+,-
4	<,>,<=,>=
5	=,<>
6	AND
7	XOR
8	OR

Ladder diagram

Structures for Control of Flux

JUMP instructions:

Conditional and unconditional

Jump instructions are used to go to a programming line with an %Li label address:

- **JMP**: unconditional program jump
 - **JMPC**: program jump if the instruction's Boolean result from the previous test is set at 1
 - **JMPCN**: program jump if the instruction's Boolean result from the previous test is set at 0. %Li is the label of the line to which the jump has been made (address i from 1 to 999 with maximum 256 labels)
-

Ladder diagram


Structures for Control of Flux

Example:

Use of jump instructions

Attention to:

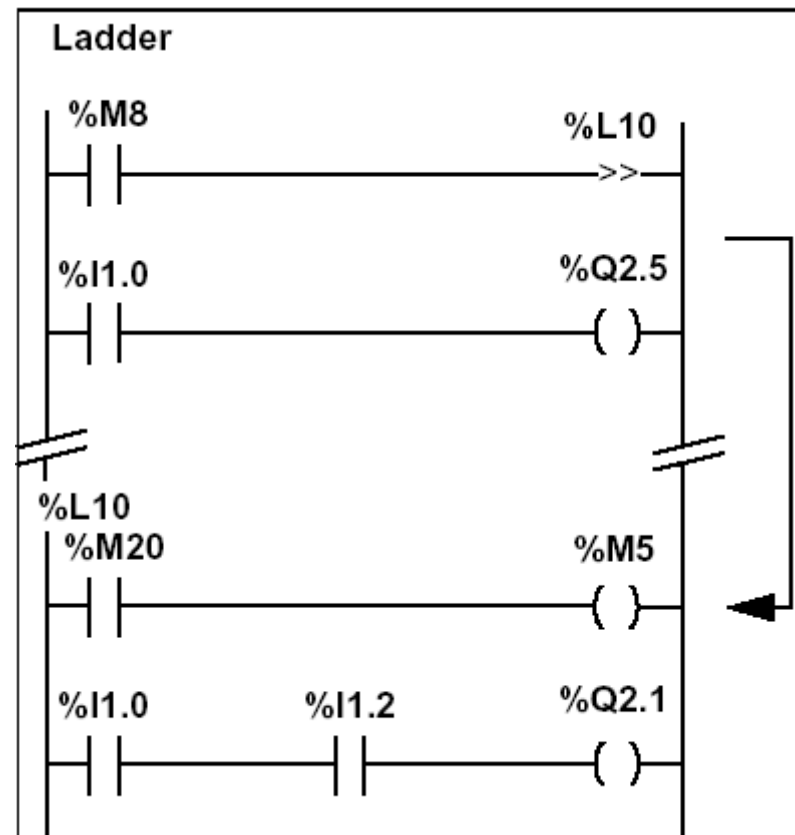- **INFINITE LOOPS ...**
- **It is not a good style of programming!...**
- **Does not improve the legibility of the proposed solution.**




Ladder diagram


Structures for Control of Flux

Subroutines



Call and Return

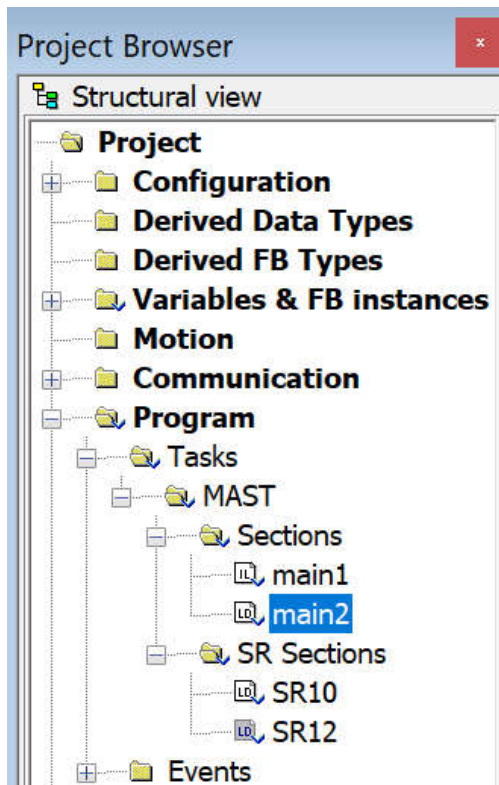

main2

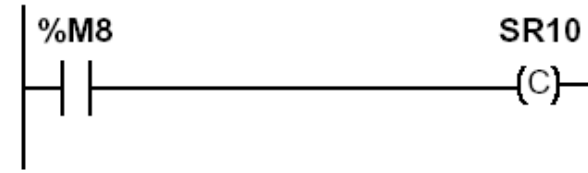


SR10

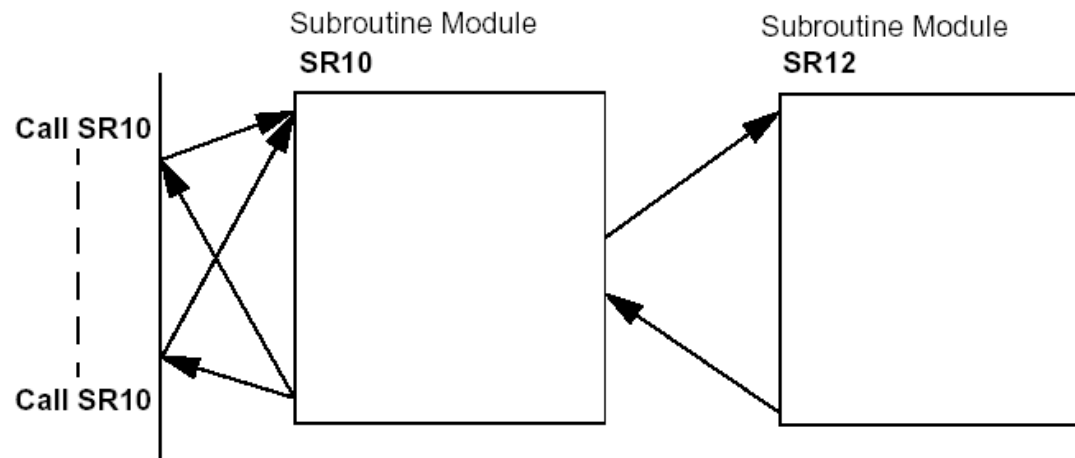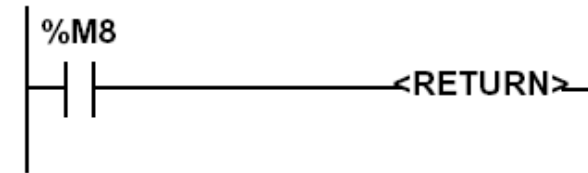

Ladder diagram


Structures for Control of Flux

Halt

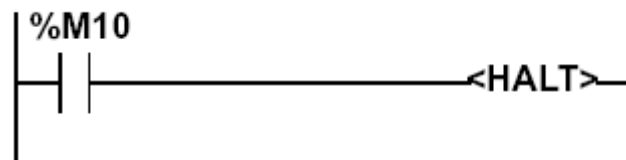

Stops all processes!

Events masking

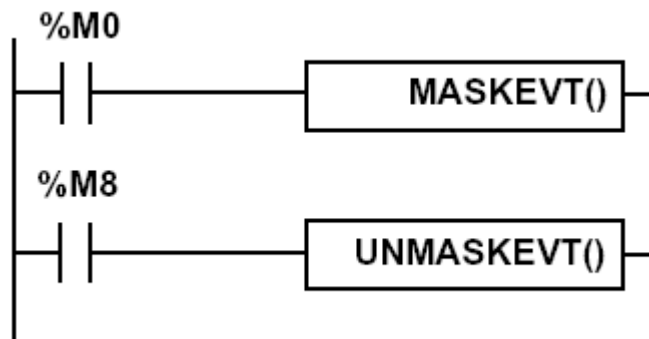

Ladder diagram


There are other advanced instructions (see manual)

- **Monostable**
- **Registers of 256 words (LIFO ou FIFO)**
- ***DRUMs***
- **Comparators**
- ***Shift-registers***
- **...**
- **Functions to manipulate *floats***
- **Functions to convert bases and types**


Ladder diagram

Numerical Tables

Type	Format	Maximum address	Size	Write access
Internal words	Simple length	%MWi:L	i+L<=Nmax (1)	Yes
	Double length	%MWDi:L	i+L<=Nmax-1 (1)	Yes
	Floating point	%MFi:L	i+L<=Nmax-1 (1)	Yes
Constant words	Single length	%KWi:L	i+L<=Nmax (1)	No
	Double length	%KWDi:L	i+L<=Nmax-1 (1)	No
	Floating point	%KFi:L	i+L<=Nmax-1 (1)	No
System word	Single length	%SW50:4 (2)	-	Yes

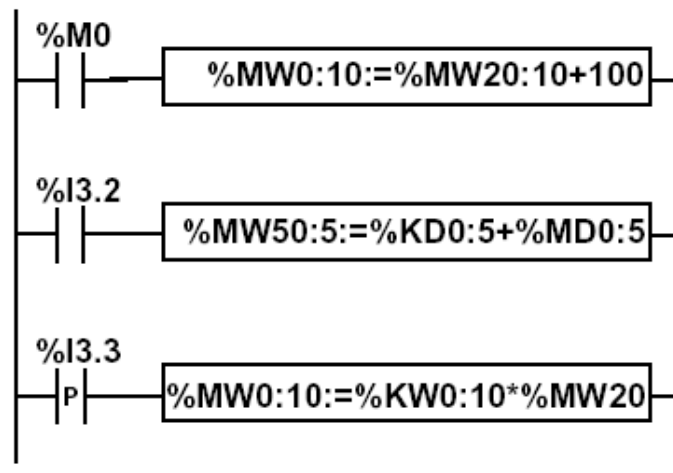

Ladder diagram [Schneider Micro PLC, system information: system bits](#)

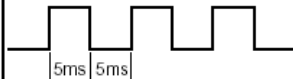Bit	Function	Description	Initial state	TSX37	TSX57
%S0	Cold start	Normally on 0, this bit is set on 1 by: <ul style="list-style-type: none"> ● loss of data on power restart (battery fault), ● the user program, ● the terminal, ● cartridge uploading, ● pressing on the RESET button. This bit goes to 1 during the first complete cycle. It is reset to 0 before the following cycle. (Operation)	0	YES	YES
%S1	Warm restart	Normally on 0, this bit is set on 1 by: <ul style="list-style-type: none"> ● power restart with data save, ● the user program, ● the terminal. It is reset to 0 by the system at the end of the first complete cycle and before output is updated. (Operation)	0	YES	YES
%S4	Time base 10ms	An internal timer regulates the change in status of this bit. It is asynchronous in relation to the PLC cycle. Graph : 	-	YES	YES
%S5	Time base 100 ms	Idem %S4	-	YES	YES
%S6	Time base 1 s	Idem %S4	-	YES	YES
%S7	Time base 1 mn	Idem %S4	-	YES	YES

**See manual
for the remaining
100 bits generated...**

Ladder diagram [Schneider Micro PLC, System information: system words](#)

Words	Function	Description	Management
%SW0	Master task scanning period	The user program or the terminal modify the duration of the master task defined in configuration. The duration is expressed in ms (1.255 ms) %SW0=0 in cyclic operation. On a cold restart: it takes on the value defined by the configuration.	User
%SW1	Fast task scanning period	The user program or the terminal modify the duration of the fast task as defined in configuration. The duration is expressed in ms (1.255 ms) On a cold restart: it takes on the value defined by the configuration.	User
%SW8	Acquisition of task input monitoring	Normally on 0, this bit can be set on 1 or 0 by the program or the terminal. It inhibits the input acquisition phase of each task. <ul style="list-style-type: none"> ● %SW8:X0 =1 assigned to MAST task: outputs linked to this task are no longer guided. ● %SW8:X1 =1 assigned to FAST task: outputs linked to this task are no longer guided. 	User
%SW9	Monitoring of task output update	Normally on 0, this bit can be set on 1 or 0 by the program or the terminal. Inhibits the output updating phase of each task. <ul style="list-style-type: none"> ● %SW9:X0 =1 assigned to MAST task: outputs linked to this task are no longer guided. ● %SW9:X1 =1 assigned to FAST task: outputs linked to this task are no longer guided. 	User
%SW10	First cycle after cold start	If the bit for the current task is on 0, this indicates that the first cycle is being carried out after a cold start. <ul style="list-style-type: none"> ● %SW10:X0: is assigned to the MAST Master task ● %SW10:X1: is assigned to the FAST fast task 	System
%SW11	Watchdog duration	Reads the duration of the watchdog as set in configuration. It is expressed in ms (10...500 ms).	System

**See manual
for the remaining
140 words generated...**

Schneider Premium System information: system *bits*, system *words*

Operating Modes

Hide Locate Back Forward Print

Contents Index Search

- Welcome to the Unity Pro On-line Help
- How to Use the On-line Help
- Addendum
- General Safety Instructions
- Compatibility Rules
- Cyber Security
- Unity Pro Software
 - Languages Reference
 - Operating Modes
 - Unity Pro System Bits and Words
 - Safety Information
 - About the Book
 - System Bits**
 - System Bits Introduction
 - Description of System Bits %S0 to %S7
 - Description of System Bits %S9 to %S13
 - Description of System Bits %S15 to %S21
 - Description of System Bits %S30 to %S59
 - Description of System Bits %S62 to %S79
 - Description of System Bits %S80 to %S97
 - Description of System Bits %S100 to **%S124**
 - System Words

Operating Modes

Hide Locate Back Forward Print

Contents Index Search

- Welcome to the Unity Pro On-line Help
- How to Use the On-line Help
- Addendum
- General Safety Instructions
- Compatibility Rules
- Cyber Security
- Unity Pro Software
 - Languages Reference
 - Operating Modes
 - Unity Pro System Bits and Words
 - Safety Information
 - About the Book
 - System Bits
 - System Words
 - System Words %SW0 to %SW127**
 - Description of System Words %SW0 to %SW11
 - Description of System Words %SW12 to %SW29
 - Description of System Words %SW30 to %SW47
 - Description of System Words %SW48 to %SW69
 - Description of Hot Standby Quantum System Words %SW60 to %SW69
 - Description of Hot Standby Premium System Words %SW60 to %SW65
 - Description of System Words %SW70 to %SW99
 - Description of System Words %SW100 to %SW116
 - Description of System Words %SW124 to %SW127
 - Premium/Atrium-specific System Words
 - Description of Premium/Atrium-specific System Words %SW128 to %SW143
 - Description of Premium/Atrium-specific System Words %SW144 to %SW146
 - Description of Premium/Atrium-specific System Words %SW147 to %SW152
 - Description of Premium/Atrium-specific System Word %SW153
 - Description of Premium/Atrium-specific System Word %SW154
 - Description of Premium/Atrium-specific System Words %SW155 to **%SW167**
 - Quantum-specific System Words


IST / DEEC / API

%S0 COLDSTART	Function	Cold start		
	Initial State	1 (1 cycle)		
	Platforms	M340: Yes M580: Yes	Quantum: Yes Momentum Unity: Yes	Premium: Yes Atrium: Yes
	Normally on 0, this bit is set on 1 by: <ul style="list-style-type: none"> power restoral with loss of data (battery fault found) the user program the terminal a change of cartridge (PCMCIA on Premium and Quantum) This bit is set to 1 during the first complete restored cycle of the PLC either in RUN or in STOP mode. It is reset to 0 by the system at the end of the first complete cycle and before the outputs are updated.			
%S1 WARMSTART	Function	Warm restart		
	Initial State	0		
	Platforms	M340: Yes M580: Yes	Quantum: Yes ⁽¹⁾ Momentum Unity: Yes	Premium: Yes Atrium: Yes
	(1) except for safety PLCs			
Normally at 0, this bit is set to 1 by: <ul style="list-style-type: none"> power is restored with data save, the user program, the terminal, It is reset to 0 by the system at the end of the first complete cycle and before the outputs are updated.				
This bit is not available on Quantum Safety PLCs.				
%S1 is not always set in the first scan of the PLC. If a signal set for every start of the PLC is needed, %S21 should be used instead.				

IST / DEEC / API

%SW0 MASTPERIOD <div style="border: 1px solid blue; padding: 5px; display: inline-block; color: blue;"> <i>Not the cyclic period</i> </div>	Function	Master task scanning period		
	Initial State	0		
	Platforms	M340: Yes M580: Yes	Quantum: Yes ⁽¹⁾ Momentum Unity: Yes	Premium: Yes Atrium: Yes
	(1) except for safety PLCs			
<p>This word is used to modify the period of the master task via the user program or via the terminal.</p> <p>The period is expressed in ms (1...255 ms)</p> <p>%SW0=0 in cyclic operation.</p> <p>On a cold restart: it takes the value defined by the configuration.</p>				
%SW1 FASTPERIOD	Function	FAST task scanning period		
	Initial State	0		
	Platforms	M340: Yes M580: Yes	Quantum: Yes ⁽¹⁾ Momentum Unity: No	Premium: Yes Atrium: Yes
	(1) except for safety PLCs			
<p>This word is used to modify the period of the FAST task via the user program or via the terminal.</p> <p>The period is expressed in milliseconds (1...255 ms).</p> <p>On a cold restart, it takes the value defined by the configuration.</p> <p>NOTE: This word is not available on Quantum safety PLCs.</p>				

Ladder diagram Software Organization

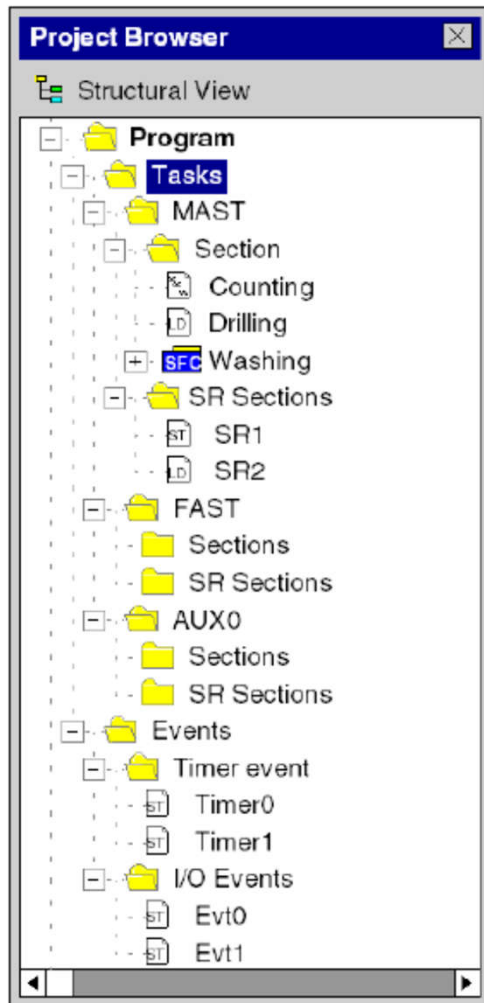

A program can be built from:

Tasks, that are executed cyclically or periodically.

Tasks **MAST** / **FAST** / **AUX** are built from:

Sections

Subroutines

Event processing, that is carried out before all other tasks.

Event processing is built from:

Sections for processing time controlled events



Sections for processing hardware controlled events

Unity - Project Browser

Ladder diagram Software Organization

MAST – Master Task Program

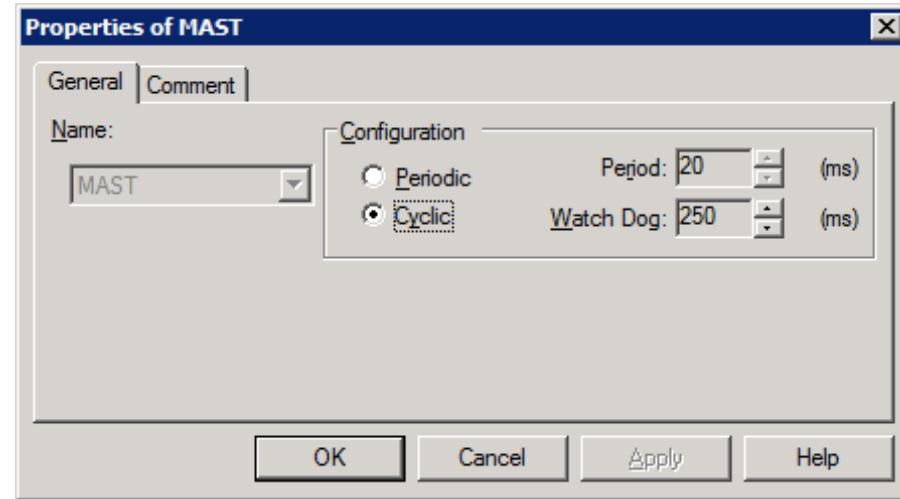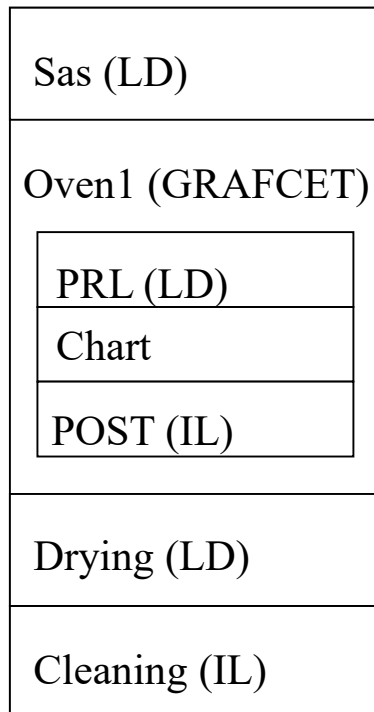- Composed by **sections**
- Execution **Cyclic** or **Periodic**




Cyclical execution consists of stringing cycles together one after the other with no waiting time between the cycles.

In **Periodic** mode, you determine a specific time (period) in which the master task must be executed. If it is executed under this time, a waiting time is generated before the next cycle. If it is executed over this time, a control system indicates the overrun. If the overrun is too high, the PLC is stopped.

Ladder diagram Software Organization

FAST – Fast Task Program

Priority greater than MAST

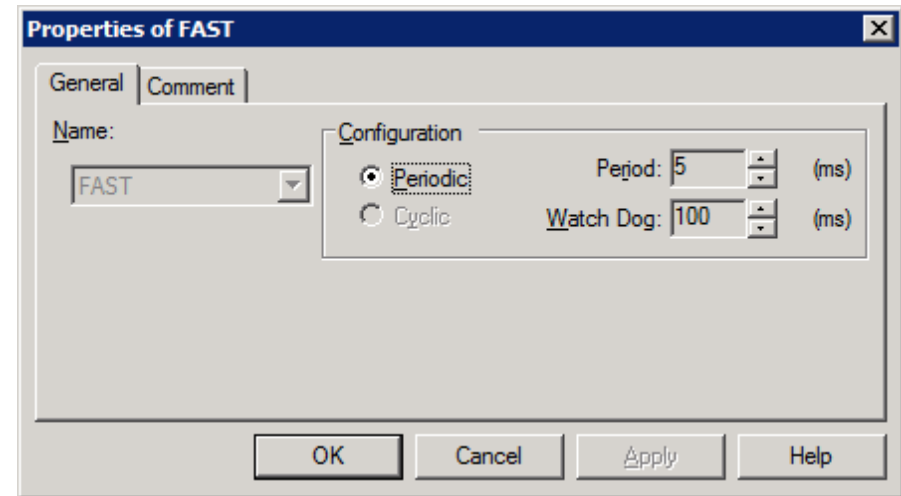

- Executed Periodically (1-255ms)
- Verified by a *Watchdog*, impacts on %S11
- %S31 *Enables* or *disables* a FAST
- %S33 gives the execution time for FAST

Ladder diagram **Software Organization**

Event Processes – Processes that can react to external changes
(16 in the Micro 3722 EV0 to EV15)

Priority greater than MAST and FAST!

Event Generators

- Inputs 0 to 3 in module 1, given transitions
- Counters
- Upon telegrams reception
- %S38 *Enables* or *disables* event processes

(also with MASKEVT() or UNMASKEVT())

Ladder diagram Development tools

Each PLC has limitations in terms of connections

Example:


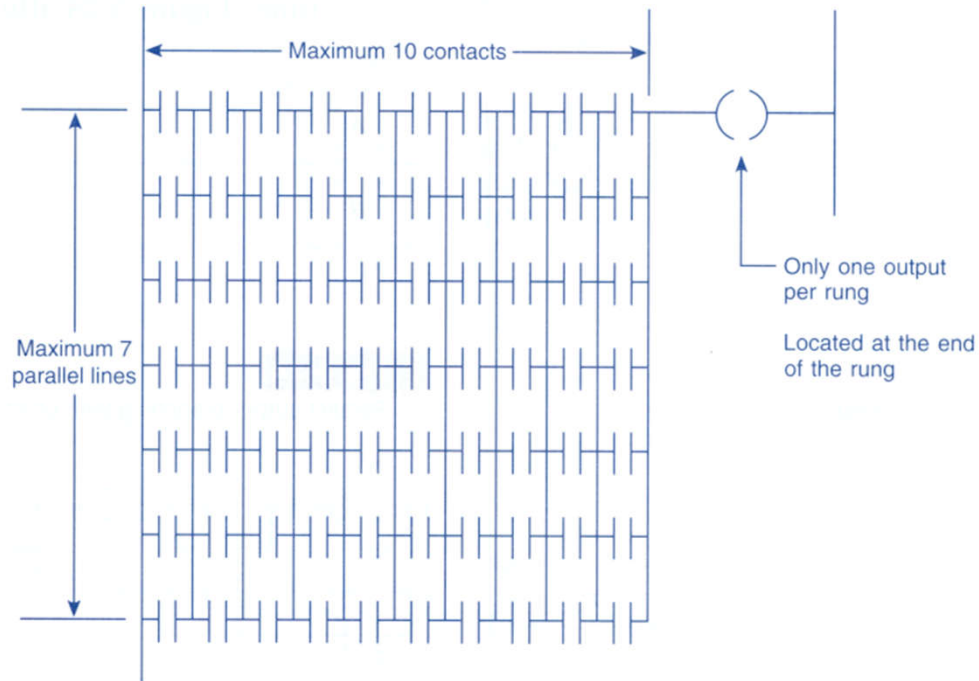


Fig. 5-27

Typical PLC matrix limitation diagram. The exact limitations are dependent on the particular type of PLC used. Programming more than the allowable series elements, parallel branches, or outputs will result in an error message being displayed.

Ladder diagram **Development tools**

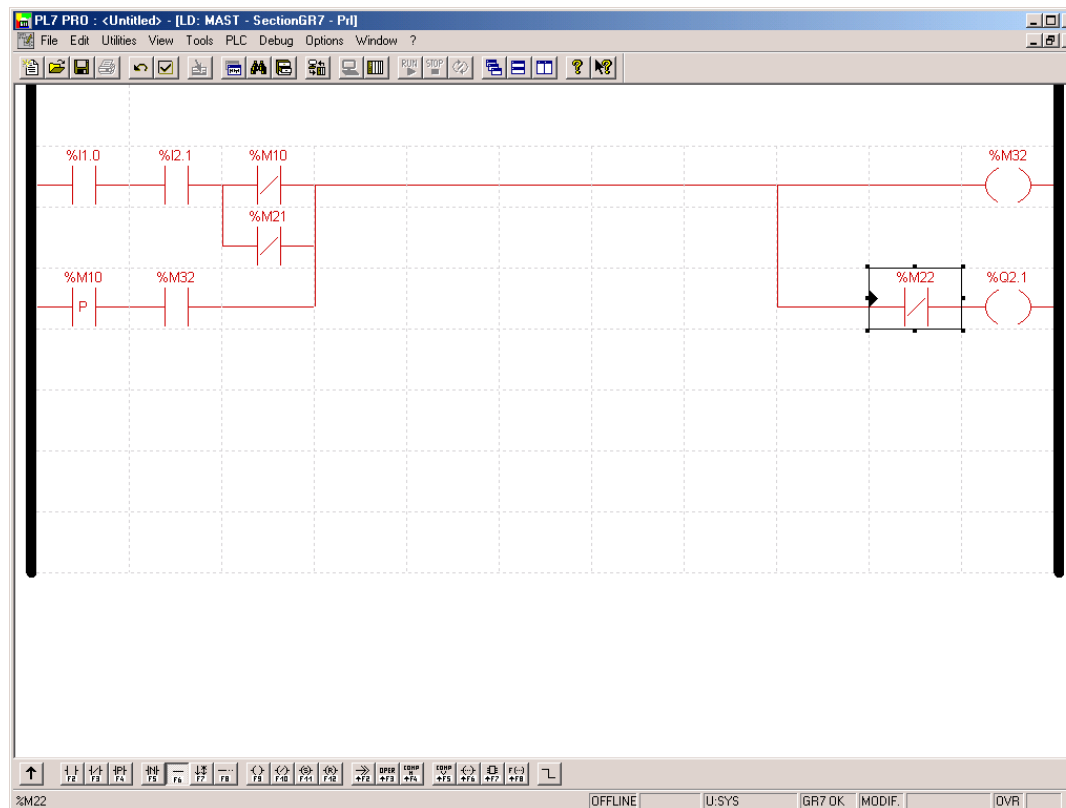It is important to learn the potentialities and ...
 the limitations of the developing tools,
 i.e. ***STUDYING the manuals is a MUST.***



Ladder diagram Development tools

Last but not least, *learn how to develop and debug programs*
(and how to do some fine tuning).

1

2

3

4

Channel	Symbol	State	Error	Fallback	Function
0			ERR	STOP	ALARM
1		0	ERR		
2		F1	ERR		
3		F0	ERR		
4		F0	ERR		
5		0	ERR		
6		0	ERR		
7		0	ERR		
8		0	ERR	STOP	
9		0	ERR		
10		0	ERR		
11		0	ERR		
12		0	ERR		
13		0	ERR		
14		0	ERR		
15		0	ERR		

Channel 4 commands

Forcing

- F4 Force to 0
- F5 Force to 1
- F6 Unforce

Write

- F7 Set
- F8 Reset

Ladder diagram Development tools

Last but not least, *learn how to develop and debug programs* (and how to do some fine tuning).

