

# **Industrial Automation**

**(Automação de Processos Industriais)**

## **PLC Programming languages**

### **Ladder Diagram**

<http://www.isr.tecnico.ulisboa.pt/~jag/courses/api20b/api2021.html>

Prof. Paulo Jorge Oliveira, original slides  
Prof. José Gaspar, rev. 2020/2021

## Syllabus:

**Chap. 2 – Introduction to PLCs [2 weeks]**

...

**Chap. 3 – PLC Programming languages [2 weeks]**

Standard languages (IEC-61131-3):

*Ladder Diagram; Instruction List, and Structured Text.*


Software development resources.

...

**Chap. 4 - GRAFCET (*Sequential Function Chart*) [1 week]**

**PLC Programming languages\***  
**IEC 1131-3 changed to IEC 61131-3**

*Ladder Diagram*

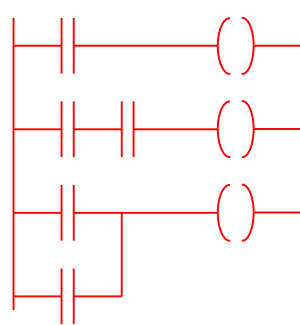

*Structured Text*


```

If %I1.0 THEN
  %Q2.1 := TRUE
ELSE
  %Q2.2 := FALSE
END_IF
    
```

*Instruction List*

LD	%M12
AND	%I1.0
ANDN	%I1.1
OR	%M10
ST	%Q2.0

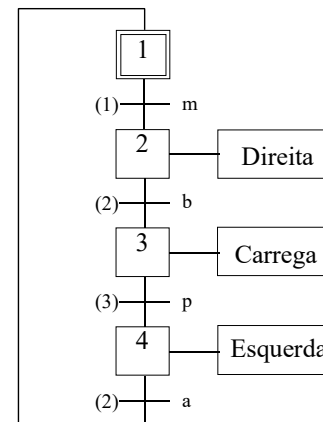*Sequential Function Chart*  
**(GRAFCET)**





## Ladder diagram

**Relay ladder logic**, i.e. electromagnetic relay control, was the basis to create a standard programming language.

A **Program** is a series of instructions that directs the PLC to execute actions.

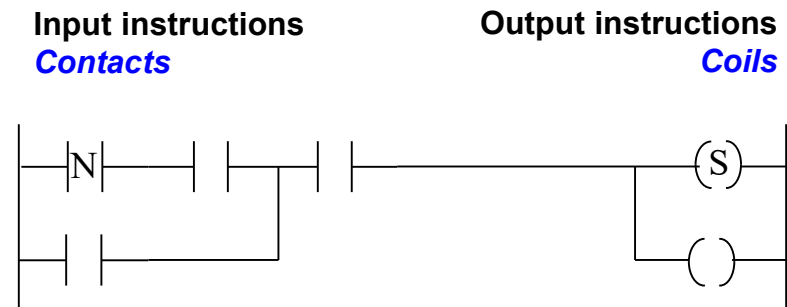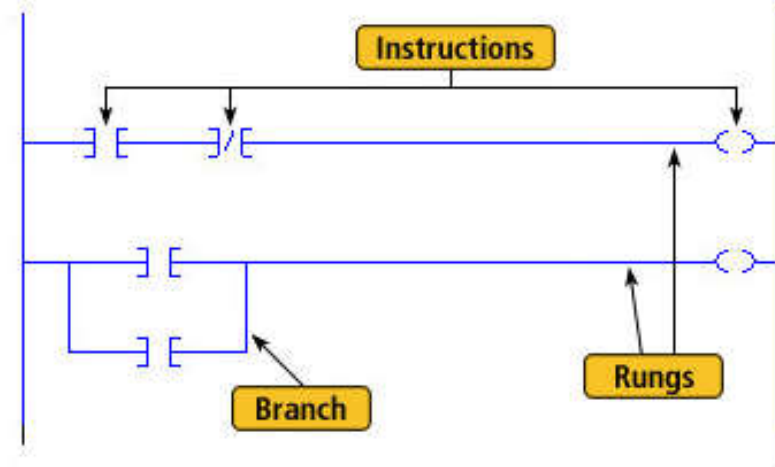Simplest programs are based in **physical addresses** naming **contacts** and **coils** or, in general, the so-called **operands**.




# Ladder diagram

## Unity Pro dev. environment

0- See: Unity Pro SW > Languages Ref > Programming Language > Ladder Diagram (LD)

1- Double click here to edit / see the hardware configuration

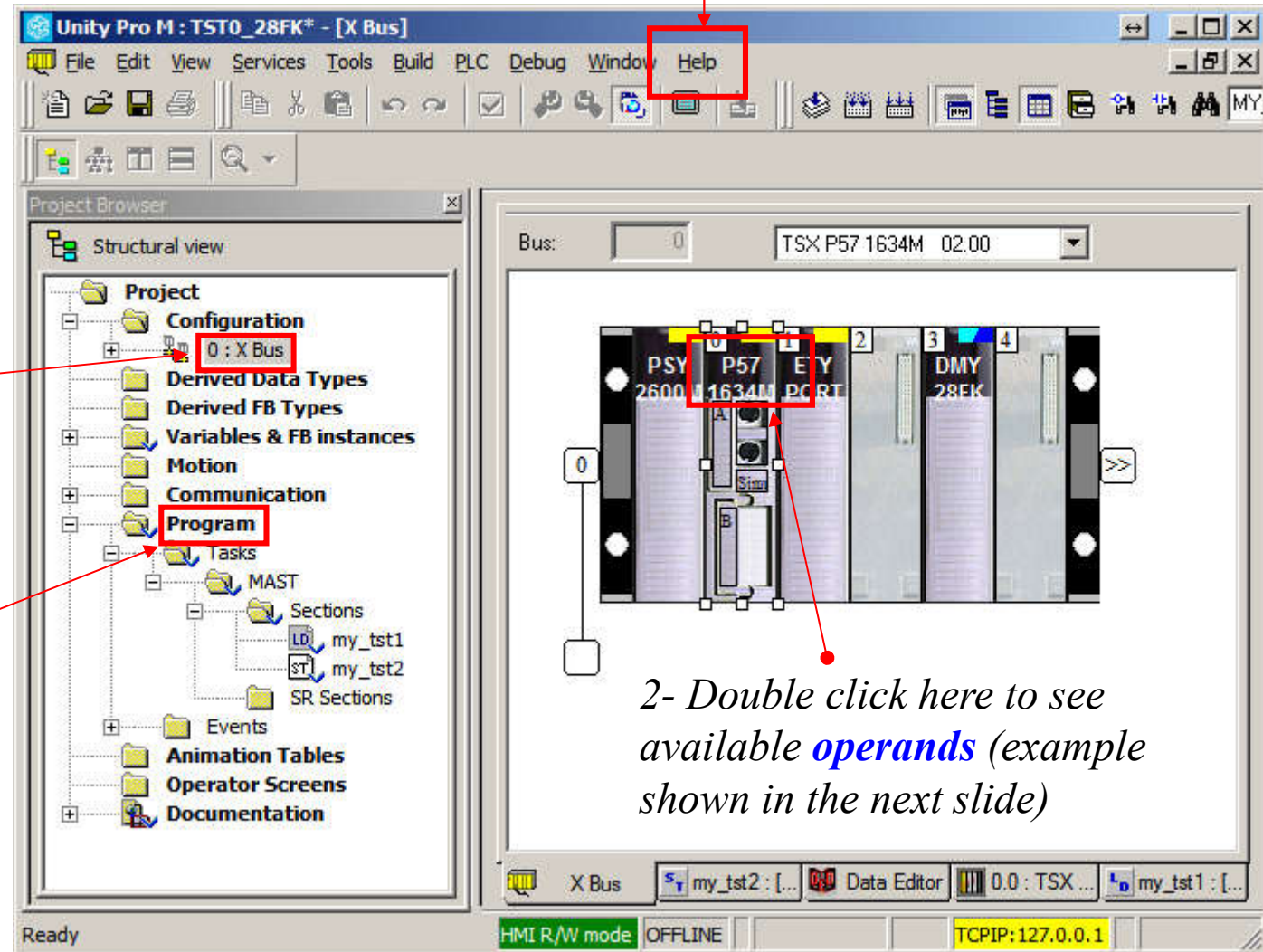3- Programs in Ladder (and other languages) are added here.



2- Double click here to see available operands (example shown in the next slide)

# Ladder diagram    Types of **operands** in Schneider DMY 28FK:

The screenshot shows the configuration interface for Schneider DMY 28FK. It is divided into three main sections: CPU objects, I/O Objects, and Update. The I/O Objects section is highlighted with a blue box, and a table of addresses is also highlighted with a blue border.

**CPU objects**

System:  %S  %SW Select all

Memory:  %M  %MW  %MD  %MF Unselect all

%KW  %KD  %KF

**I/O Objects**

Channel:  %CH

Configuration:  %KW  %KD  %KF Select all

System:  %MW Unselect all

Status:  %MW

Parameter:  %MW  %MD  %MF

Command:  %MW  %MD  %MF

Implicits:  %I  %IW  %ID  %IF  %IERR

%Q  %QW  %QD  %QF

**Update**

Update grid with  addresses  names, types and comments  usages

Filter on usage

	Address	Name	Type	Comment
1	%I0.3.0		EBOOL	
2	%I0.3.1		EBOOL	
3	%I0.3.2		EBOOL	
4	%I0.3.3		EBOOL	
5	%I0.3.4		EBOOL	
6	%I0.3.5		EBOOL	
7	%I0.3.6		EBOOL	
8	%I0.3.7		EBOOL	
9	%I0.3.8		EBOOL	
10	%I0.3.9		EBOOL	
11	%I0.3.10		EBOOL	
12	%I0.3.11		EBOOL	
13	%I0.3.12		EBOOL	
14	%I0.3.13		EBOOL	
15	%I0.3.14		EBOOL	
16	%I0.3.15		EBOOL	
17	%Q0.3.16		EBOOL	
18	%Q0.3.17		EBOOL	
19	%Q0.3.18		EBOOL	
20	%Q0.3.19		EBOOL	
21	%Q0.3.20		EBOOL	
22	%Q0.3.21		EBOOL	
23	%Q0.3.22		EBOOL	
24	%Q0.3.23		EBOOL	
25	%Q0.3.24		EBOOL	
26	%Q0.3.25		EBOOL	


## Ladder diagram    Types of operands:

Bits	Description	Examples	Write access
Immediate values	0 or 1 (False or True)	0	-
Inputs/outputs	<p>These bits are the "logic images" of the electrical states of the inputs/ outputs. They are stored in the data memory and updated each time the task in which they are configured is polled.</p> <p><b>Note:</b> The unused input/output bits may not be used as internal bits.</p>	%I23.5 %Q51,2	No Yes
Internal	The internal bits are used to store the intermediary states during execution of the program.	%M200	Yes
System	The system bits %S0 to %S127 monitor the correct operation of the PLC and the running of the application program.	%S10	According to i
Function blocks	<p>The function block bits correspond to the outputs of the function blocks or DFB instance. These outputs may be either directly connected or used as an object.</p>	%TM8.Q	No
Word extracts	With the PL7 software it is possible to extract one of the 16 bits of a word object.	%MW10:X5	According to the type of words
Grafcet steps and macro-steps	The Grafcet status bits of the steps, macro-steps and macro-step steps are used to recognize the Grafcet status of step i, of macro-step j or of step i of the macro-step j.	%X21 %X5.9	Yes Yes


## Ladder diagram

### Basic Instructions (*input*)


**Load**

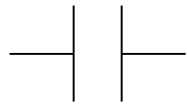

 
**Normally open** contact: contact is active (result is 1) when the control bit is 1.



 
**Normally closed** contact: contact is active (result is 1) when the control bit is 0.



 Contact in the **rising edge**: contact is active during a scan cycle where the control bit has a rising edge.



 Contact in the **falling edge**: contact is active during a scan cycle where the control bit has a falling edge.






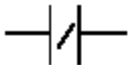
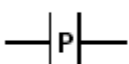
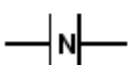
## Ladder diagram

### Basic Instructions

#### *Load operands*


##### Permitted operands


The following table gives a list of the operands used for these instructions.


Ladder	Instruction list	Structured text	Operands
	LD	:=	%I,%Q,%M,%S,%BLK,%•:Xk, %Xi, (True and False in instruction list or structured text)
	LDN	:=NOT	%I,%Q,%M,%S,%BLK,%•:Xk, %Xi, (True and False in instruction list or structured text)
	LDR	:=RE	%I,%Q,%M
	LDF	:=FE	%I,%Q,%M

# Ladder diagram


## Basic Instructions (*output*)

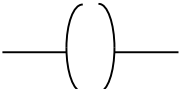**Store**  The result of the logic function activates the coil.

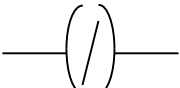 The inverse result of the logic function activates the coil.

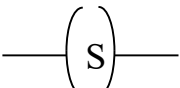 The result of the logic function energizes the relay (sets the latch).

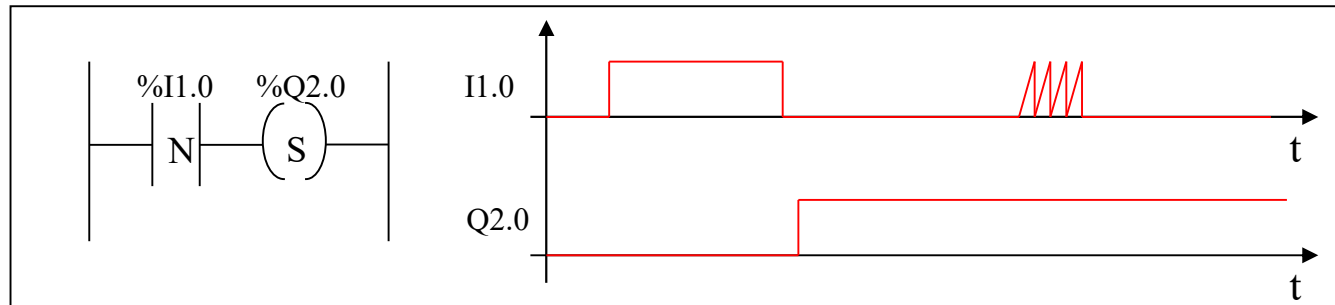 The result of the logic function de-energizes the relay (resets the latch)..







# Ladder diagram

## Basic Instructions

### *Store operands*

**Permitted operands**


The following table gives a list of the operands used for these instructions

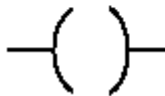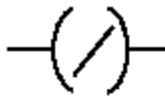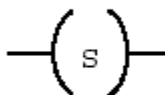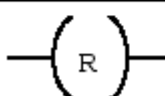Language data	Instruction list	Structured text	Operands
	ST	:=	%I,%Q,%M,%S,%•:Xk
	STN	:=NOT	%I,%Q,%M,%S,%•:Xk
	S	SET	%I,%Q,%M,%S,%•:Xk,%Xi Only in the preliminary processing.
	R	RESET	%I,%Q,%M,%S,%•:Xk,%Xi Only in the preliminary processing.

# Ladder diagram

## Allen Bradley notation


### Relays with *latch* and *unlatch*

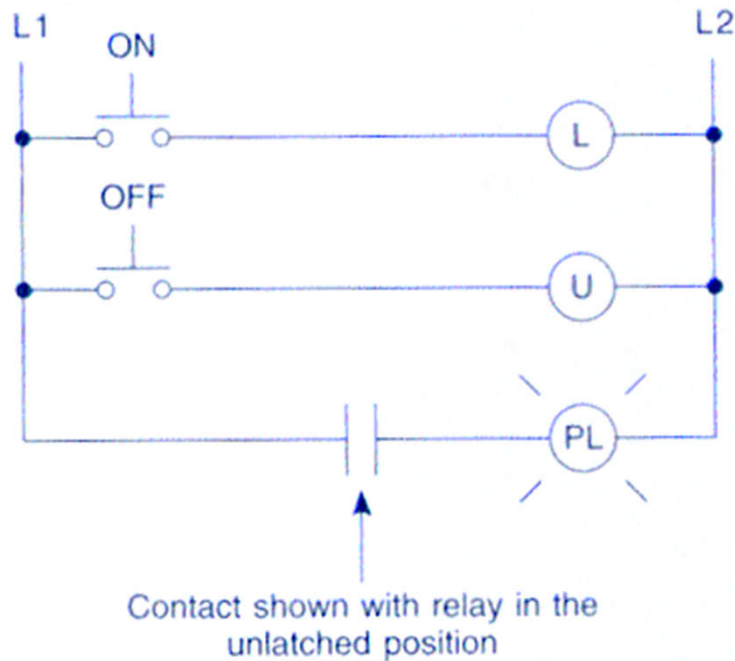


**Fig. 6-50**

Schematic of electromagnetic latching relay.

Instruction	Symbol	Mnemonic
Output latch	-(L)-	OTL
Output unlatch	-(U)-	OTU

 

 (a) Latch and unlatch coils have the same address



(b) Control logic




**Fig. 6-51**

OUTPUT LATCH and OUTPUT UNLATCH instructions.

# Ladder diagram


## Relay-type instructions

*Example:*

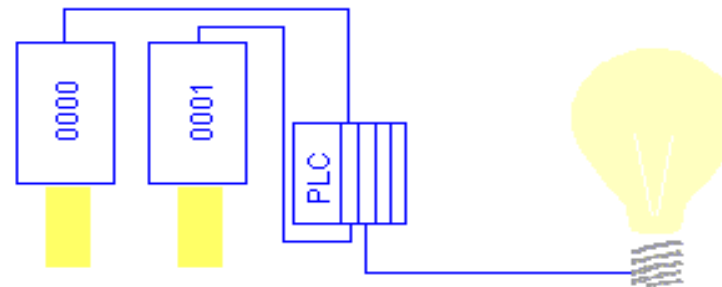  

# Ladder diagram

## Basic Instructions

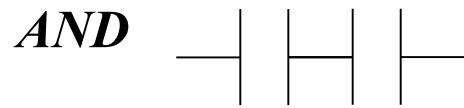


AND of the operand with the result of the previous logical operation.




AND of the inverted operand with the result of the previous logical operation.



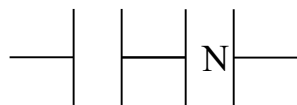AND of the rising edge with the result of the previous logical operation.



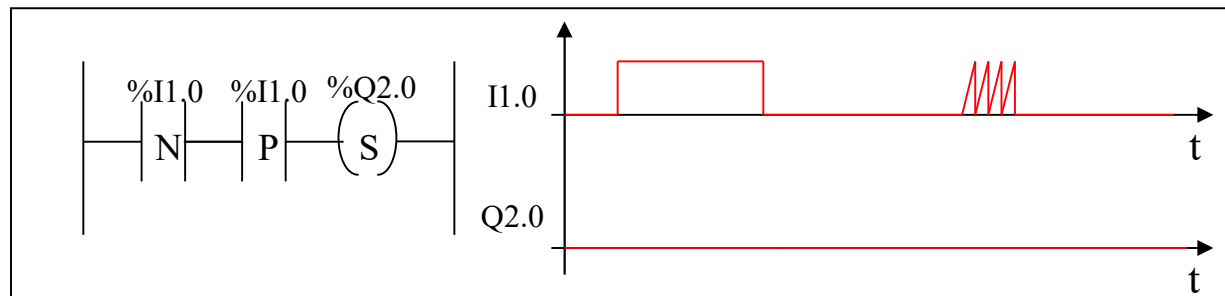
AND of the falling edge with the result of the previous logical operation.





# Ladder diagram

## Basic Instructions



**OR**

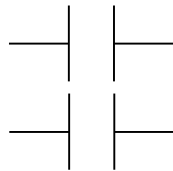

  OR of the operand with the result of the previous logical operation.




  OR of the inverted operand with the result of the previous logical operation.



OR of the rising edge with the result of the previous logical operation.

$$C = A + B \uparrow$$

 


OR of the falling edge with the result of the previous logical operation.

$$C = A + B \downarrow$$

# Ladder diagram

## Basic Instructions

### XOR

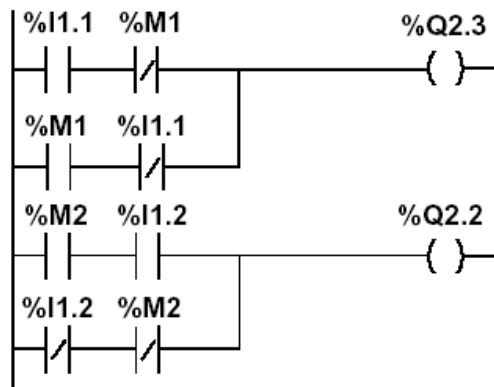

```


%Q2.3 := %I1.1 XOR %M1;
%Q2.2 := NOT(%M2 XOR %I1.2);
%Q2.2 := %M2 XOR NOT(%I1.2);
    
```

Instruction list	Structured text	Description	Timing diagram
XOR	XOR	OR Exclusive between the operand and the previous instruction's Boolean result	
XORN	XOR (NOT...)	OR Exclusive between the operand inverse and the previous instruction's Boolean result	
XORR	XOR (RE...)	OR Exclusive between the operand's rising edge and the previous instruction's Boolean result	
XORF	XOR (FE...)	OR Exclusive between the operand's falling edge and the previous instruction's Boolean result.	



## Ladder diagram

### Ladder assembling

 


The **outputs** that have a **TRUE** logical value, evaluated from the left to right and from the top to the bottom, are **energized** .


[Schneider, Micro PLCs]

# Ladder diagram

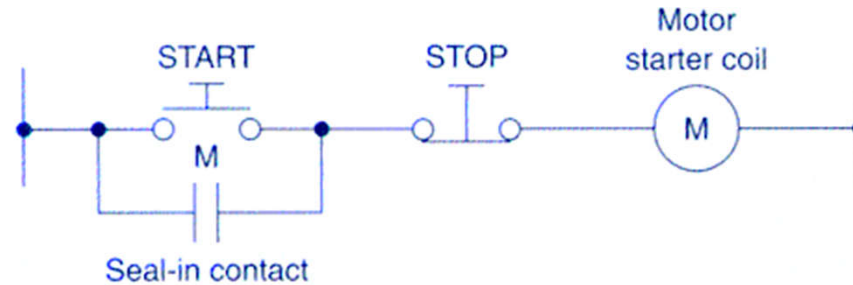**Example:**  
Latch / Sealing,  
Feedback



(a) Hard-wired circuit

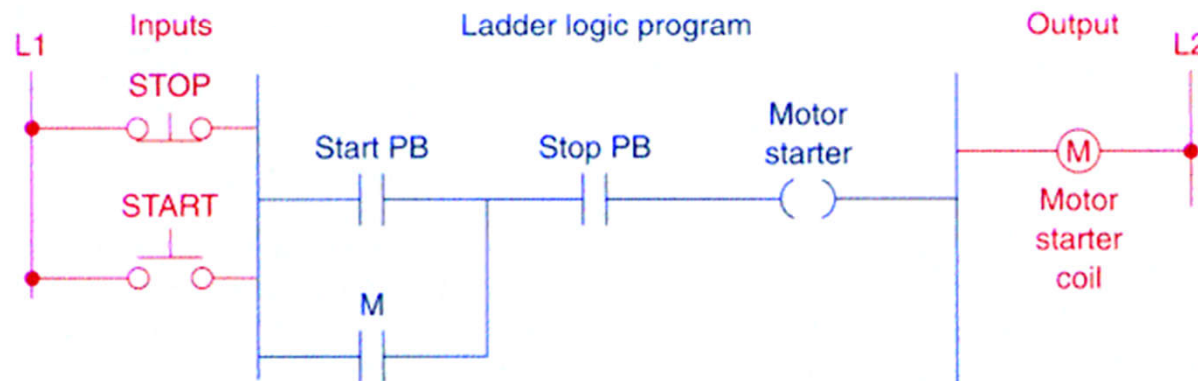

(b) Programmed circuit

**Fig. 6-48**


Seal-in circuit.

The **normally closed** push button **STOP** drives the normally open contact **Stop PB**

# Ladder diagram

## Example:


Latch / Sealing,  
Feedback

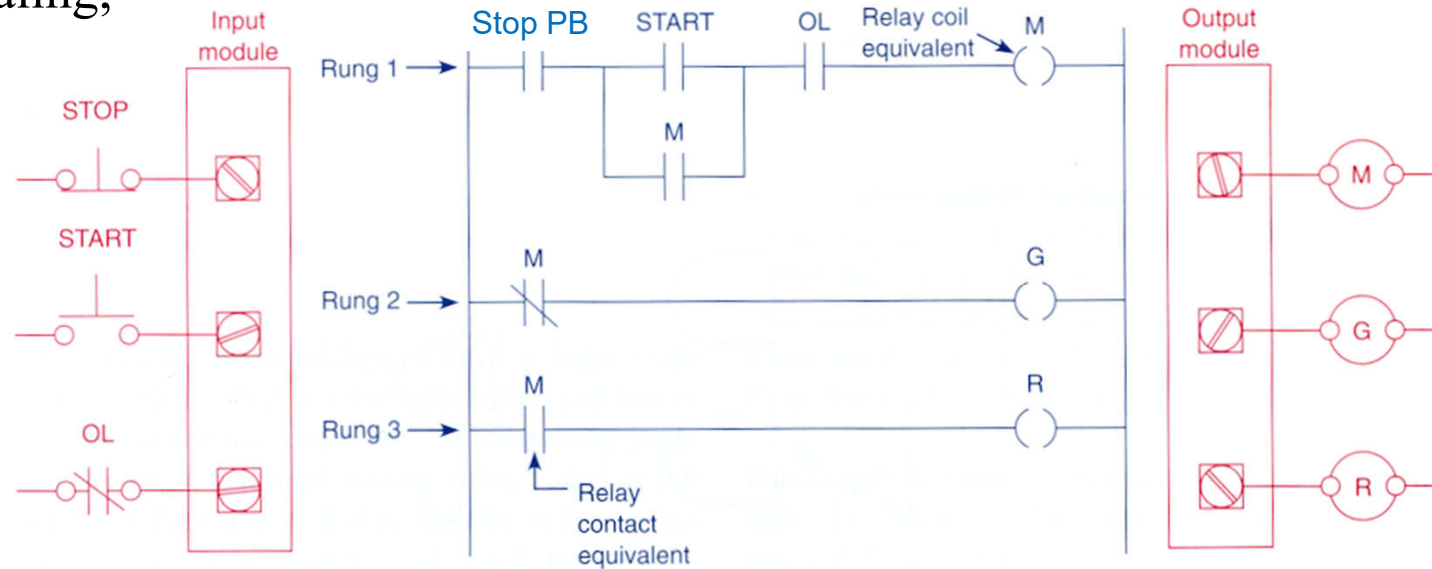

The **normally closed** push button **STOP** drives the normally open contact **Stop PB**

# Ladder diagram

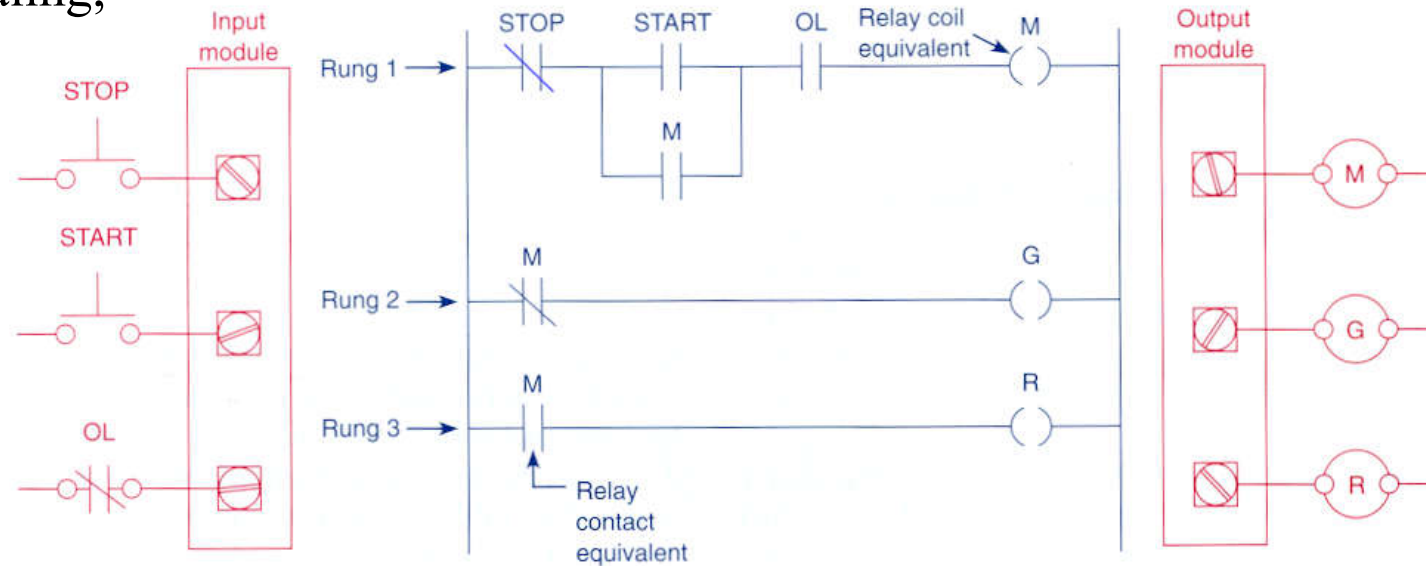**Example:**  
Latch / Sealing,  
Feedback



*STOP* button **normally open** implies **inverting that input** in the ladder diagram.

# Ladder diagram


**Example:**  
Latch / Sealing,  
Feedback

**Example 4-9**


A motor control circuit with two stop buttons:

- When the start button is depressed, the motor runs.
- By sealing, it continues to run when the start button is released.
- The stop buttons stop the motor when they are depressed.


Relay Schematic

 

Ladder logic program

 


Gate logic

 


# Ladder diagram

General case of Inputs and Outputs in **parallel**, with **derivations**

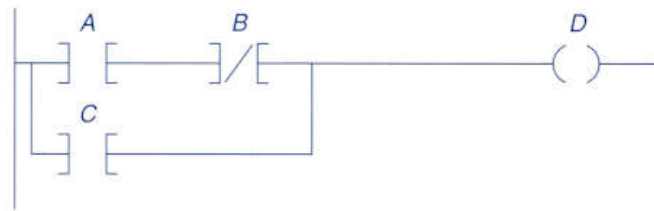


**Fig. 5-21**  
Parallel input branching.

 

**Fig. 5-23**  
Parallel output branching with conditions.



**Fig. 5-22**  
Parallel output branching.

 


**Fig. 5-24**  
Nested input and output branches.


Note: it is important to study the **constraints** and **potentialities** of the development tools.

# Ladder diagram

**Imbricated** (nested) contacts and **alternative** solution

 


**Fig. 5-25**  
Nested contact program.

 


**Fig. 5-26**  
Program required to eliminate nested contact.

# Ladder diagram

Contacts in the **vertical** and **alternative** solution

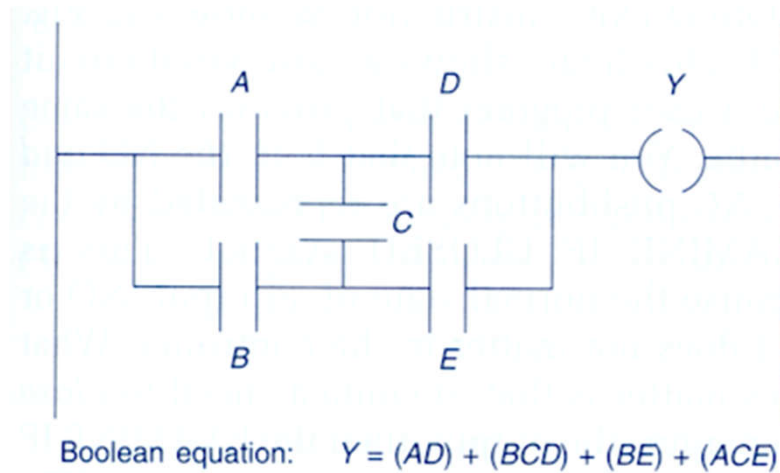

**Fig. 5-28**  
Program with vertical contact

 


**Fig. 5-29**  
Reprogrammed to eliminate vertical contact.



# Ladder diagram

Contacts in the **vertical** and **alternative** solution


Another example:

 

Boolean equation:  $Y = (ABC) + (ADE) + (FE) + (FDBC)$

**Fig. 5-30**

Original circuit.

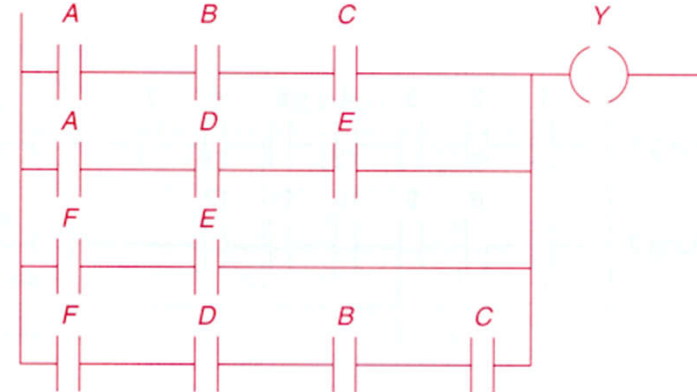

**Fig. 5-31**

Reprogrammed circuit.

*Solves the problem of disallowed right to left scanning (FDBC in fig5.30).*

**Ladder diagram**     *Temporized Relays or Timers*



Solid-state timing relay




Pneumatic timing relay




Plug-in timing relay

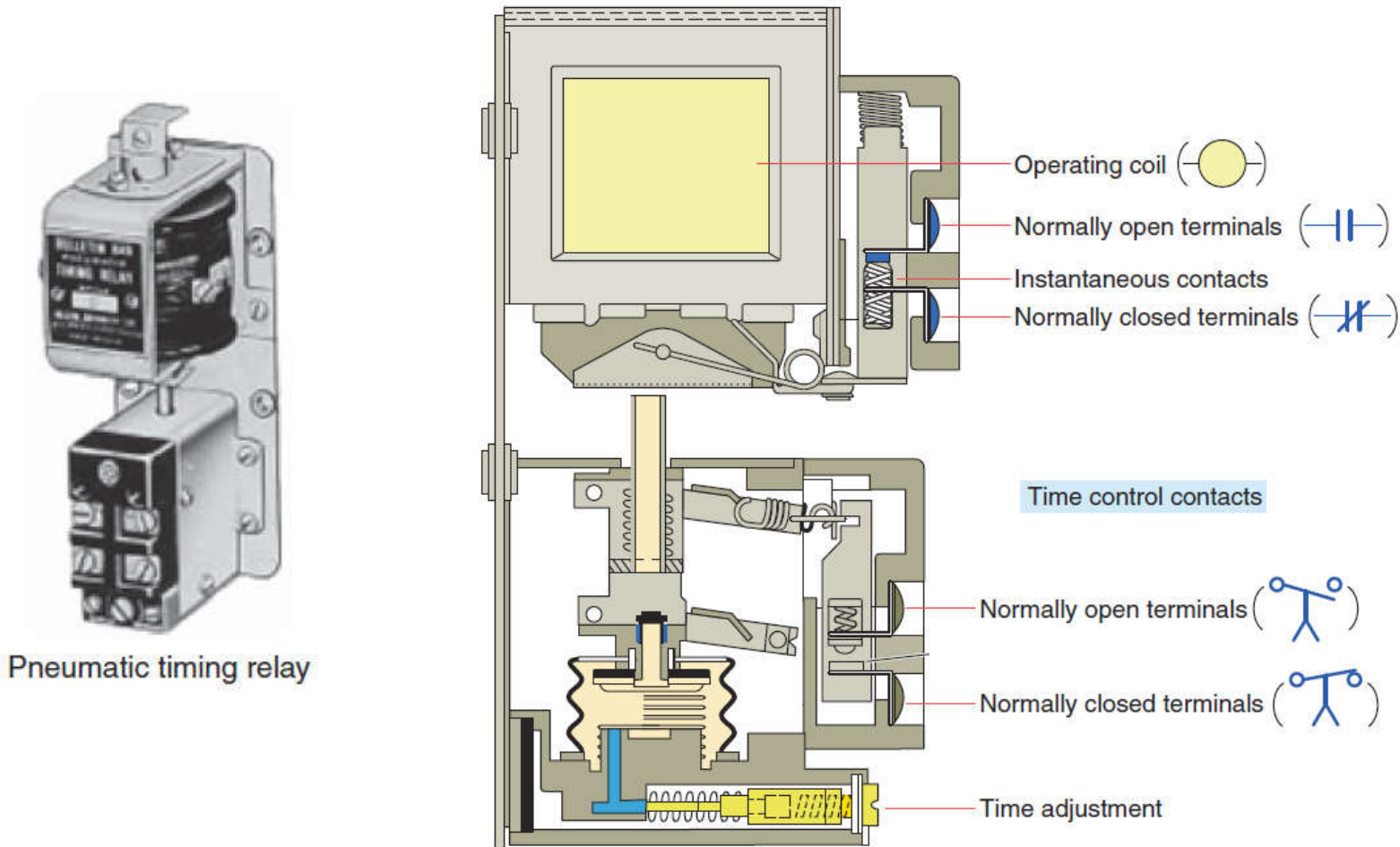Ladder diagram *Temporized Relays or Timers (pneumatic)*




The **instantaneous** contacts change state as soon as the timer coil is powered.  
 The **delayed** contacts change state at the end of the time delay.
 
# Ladder diagram *Temporized Relays or Timers (pneumatic)*



Pneumatic timing relay

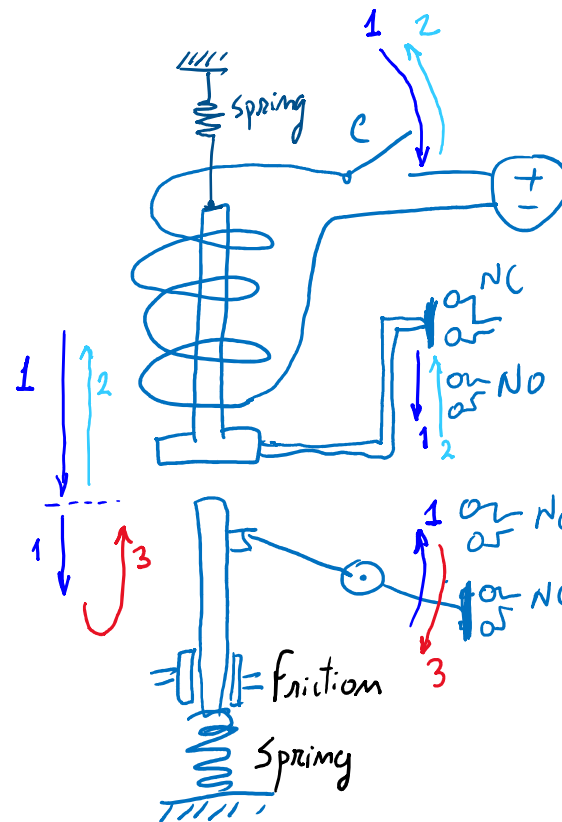

1 - fast  
2 - fast  
3 - SLOW

Input  
Output  
NOTC  
NCTO

The **instantaneous** contacts change state as soon as the timer coil is powered.  
The **delayed** contacts change state at the end of the time delay.

## Ladder diagram *Temporized Relays or Timers*

**On-delay**, provides time delay when the relay coil is energized.

On-delay symbols	
<p>Normally open, timed closed contact (NOTC).</p> <p>Contact is open when relay coil is de-energized.</p> <p>When relay is energized, there is a time delay in closing.</p>	<p>Normally closed, timed open contact (NCTO).</p> <p>Contact is closed when relay coil is de-energized.</p> <p>When relay is energized, there is a time delay in opening.</p>


**Off-delay**, provides time delay when the relay coil is de-energized.

Off-delay symbols	
<p>Normally open, timed open contact (NOTO).</p> <p>Contact is normally open when relay coil is de-energized.</p> <p>When relay coil is energized, contact closes instantly.</p> <p>When relay coil is de-energized, there is a time delay before the contact opens.</p>	<p>Normally closed, timed closed contact (NCTC).</p> <p>Contact is normally closed when relay coil is de-energized.</p> <p>When relay coil is energized, contact opens instantly.</p> <p>When relay coil is de-energized, there is a time delay before the contact closes.</p>

Tables: Relay *symbols* used for timed contacts.


# Ladder diagram *Temporized Relays or Timers*

**Timer  
On-delay  
(TON)**

 

Sequence of operation:  
 S1 open, TD de-energized, TD1 open, L1 off.  
 S1 closes, TD energizes, timing period starts, TD1 is still open, L1 is still off.  
 After 10 s, TD1 closes, L1 is switched on.  
 S1 is opened, TD de-energizes, TD1 opens instantly, L1 is switched off.


(a)

 

(b)


**Fig. 7-3**

 On-delay timer circuit (NOTC contact). (a) Operation. (b) Timing diagram.



Sequence of operation:  
 S1 open, TD de-energized, TD1 closed, L1 on.  
 S1 closes, TD energizes, timing period starts, TD1 is still closed, L1 is still on.  
 After 10 s, TD1 opens, L1 is switched off.  
 S1 is opened, TD de-energizes, TD1 closes instantly, L1 is switched on.

(a)

 


(b)

**Fig. 7-4**

On-delay timer circuit (NCTO contact). (a) Operation. (b) Timing diagram.


# Ladder diagram *Temporized Relays or Timers*

**Timer  
Off-delay  
(TOF)**

 

Sequence of operation:  
 S1 open, TD de-energized, TD1 open, L1 off.  
 S1 closes, TD energizes, TD1 closes instantly, L1 is switched on.  
 S1 is opened, TD de-energizes, timing period starts, TD1 is still closed, L1 is still on.  
 After 10 s, TD1 opens, L1 is switched off.


(a)

 

(b)


**Fig. 7-5**

 Off-delay timer circuit (NOTO contact). (a) Operation. (b) Timing diagram.



Sequence of operation:  
 S1 open, TD de-energized, TD1 closed, L1 on.  
 S1 closes, TD energizes, TD1 opens instantly, L1 is switched off.  
 S1 is opened, TD de-energizes, timing period starts, TD1 is still open, L1 is still off.  
 After 10 s, TD1 closes, L1 is switched on.

(a)

 

(b)


**Fig. 7-6**

Off-delay timer circuit (NCTC contact). (a) Operation. (b) Timing diagram.

# Ladder diagram

## *Temporized Relays*

### *or Timers (PLC)*

 

#### Characteristics:

Identifier:	%Tmi	0..63 in the TSX37
Input:	IN	to activate
Mode:	<b>TON</b>	<b>Timer On delay</b>
	<b>TOF</b>	<b>Timer Off delay</b>
	<b>TP</b>	<b>Monostable</b>
Time basis:	TB	1mn (def.), 1s, 100ms, 10ms
Programmed value:	%Tmi.P	0...9999 (def.) period=TB*Tmi.P
Actual value:	%Tmi.V	0...Tmi.P (can be read or tested)
Modifiable:	Y/N	can be modified from the console





# Ladder diagram

## Temporized Relays

### or Timers (PLC)

**TON mode**

  

Phase	Description
1	The timer is started with a rising edge on the IN input
2	The current value %Tmi.V of the timer increases from 0 to %Tmi.P by one unit at each pulse of the time base TB
3	The %Tmi.Q output bit moves to 1 when the current value has reached %Tmi.P
4	The %Tmi.Q output bit stays at 1 while the IN input is at 1.
5	When the IN input is at 0, the timer is stopped even if it is still running: %Tmi.V takes the value 0.



*App. example: start ringing the alarm if N sec after door open there is no disarm of the alarm.*

# Ladder diagram

## Temporized Relays

### or Timers (PLC)

*TOF mode*

  

Phase	Description
1	The current value %Tmi.V takes 0, on a rising edge of the IN input (even if the timer is running)
2	The %Tmi.Q output bit moves to 1.
3	The timer is started with a falling edge on the IN input.
4	The current value %Tmi.P increases to %Tmi.P by one unit at each pulse of the time base TB.
5	The %Tmi.Q output bit returns to 0 when the current value has reached %Tmi.P

*App. example: turn off stairways lights after N sec the lights' button has been released.*



# Ladder diagram

*TP mode*

## Temporized Relays
  
### or Timers (PLC)

Works as a monostable or as a pulse generator (with pre-programmed period)





Phase	Description
1	The timer is started with a rising edge on the IN input
2	The %TMi.Q output bit moves to 1.
3	The current value %TMi.V of the timer increases from 0 to %TMi.P by one unit at each pulse of the time base TB
4	The %TMi.Q output bit returns to 0 when the current value has reached %TMi.P.
5	When the IN input and the %TMi.Q output are at 0, %TMi.V takes the value 0.
6	This monostable cannot be reactivated.

*App. example: positive input edge give a controlled (fixed) duration pulse to start a motor.*

## Ladder diagram

### *Timers in PL7 vs Unity (Schneider)*

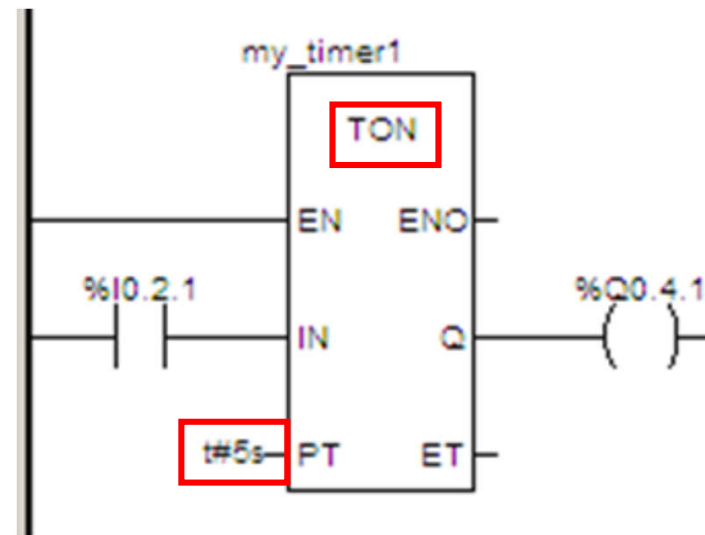
 


*Input EN and output ENO  
are facultative*

# Ladder diagram

## Timers in the Allen-Bradley PLC-5
  
### Two alternative representations

 


**Fig. 7-8**

Block-formatted timer instruction.



## Ladder diagram

### *Timers implementation in the Allen-Bradley PLC-5:*



# Ladder diagram

## Timers operation in the Allen-Bradley PLC-5

 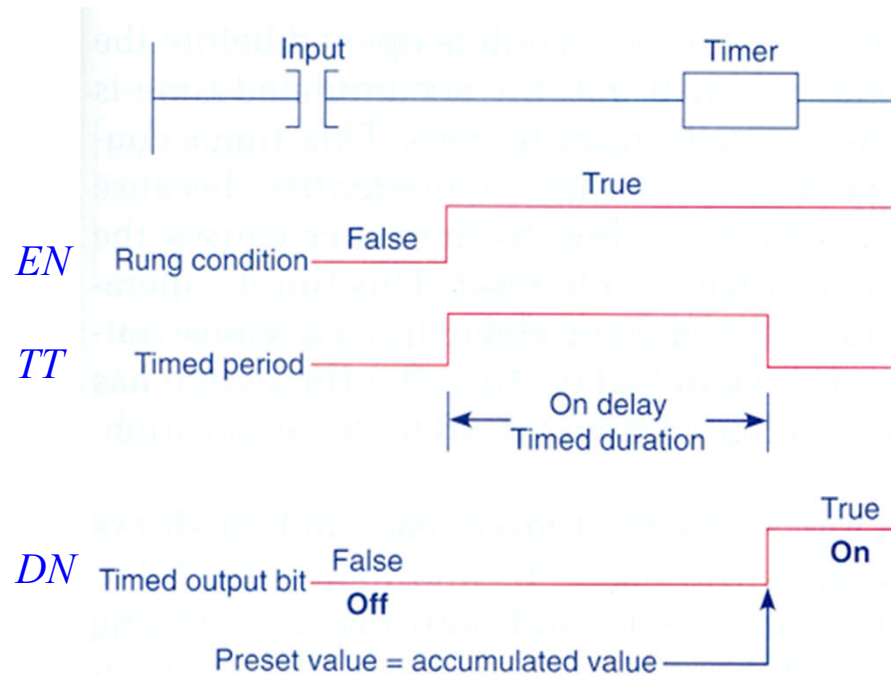


**Fig. 7-10**

On-delay timer instruction.

*EN = Enable Bit    TT = Timer-Timing Bit    DN = Done Bit*

# Ladder diagram

## Example of *timer on-delay*

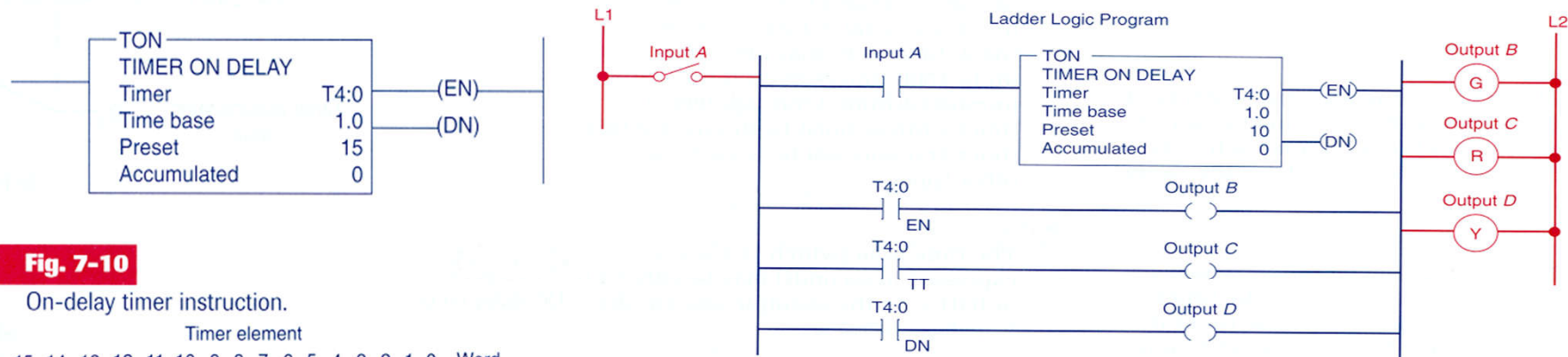

**Fig. 7-10**

On-delay timer instruction.

Timer element															Word	
15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	
EN	TT	DN														0
Preset value PRE															1	
Accumulated value ACC															2	

**Addressable bits**      **Addressable words**  
 EN = Bit 15 enable      PRE = Preset value  
 TT = Bit 14 timer timing      ACC = Accumulated value  
 DN = Bit 13 done


(c) Timers are 3-word elements. Word 0 is the control word, word 1 stores the preset value, and word 2 stores the accumulated value (Allen-Bradley PLC-5 and SLC-500 format).

**Fig. 7-11 (continued)**

On-delay timer.

**Fig. 7-11**



On-delay timer.

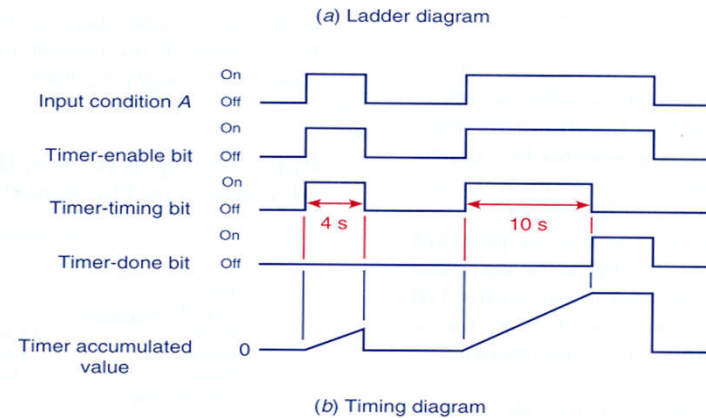



# Ladder diagram


Example of a *timer on-delay* that sets an output after a count-down

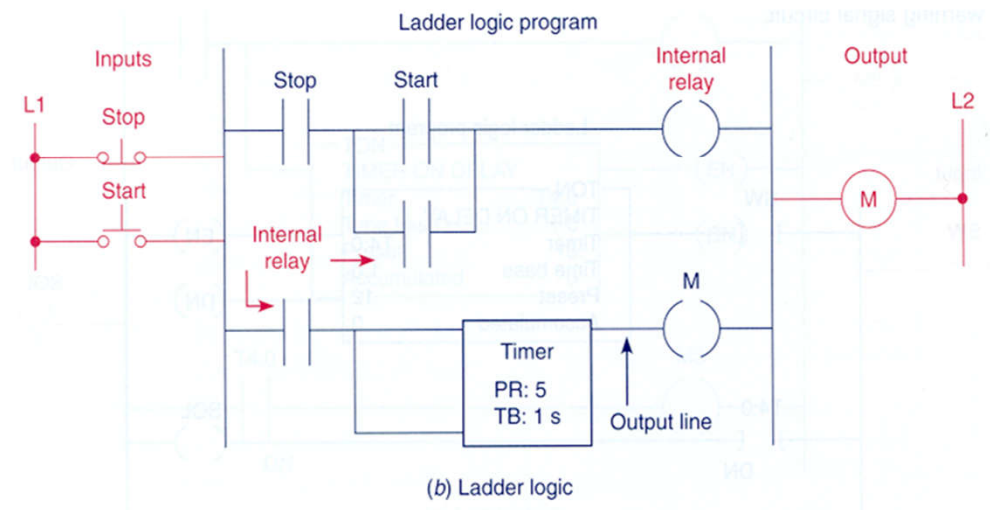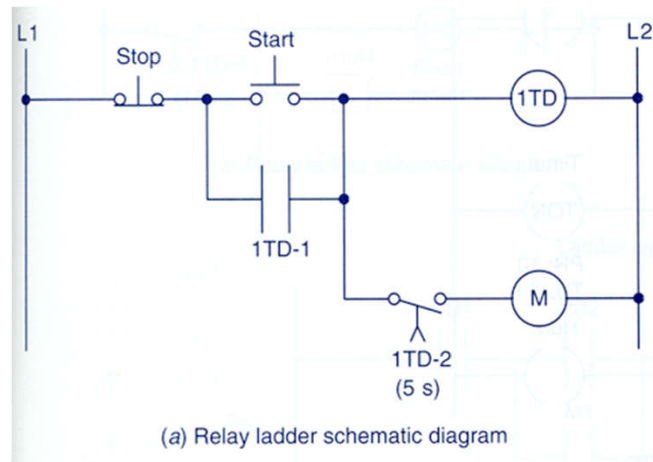


**Fig. 7-12**  
On-delay timer with instantaneous output programming.

# Ladder diagram

## Example of *timer on-delay*

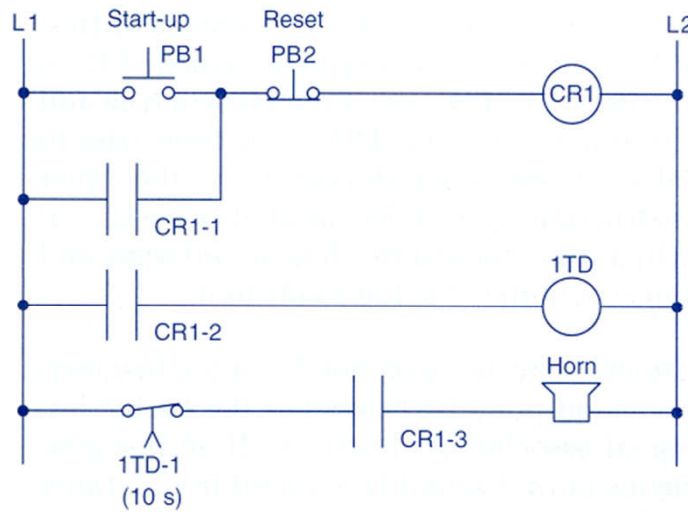

(a) Relay ladder schematic diagram

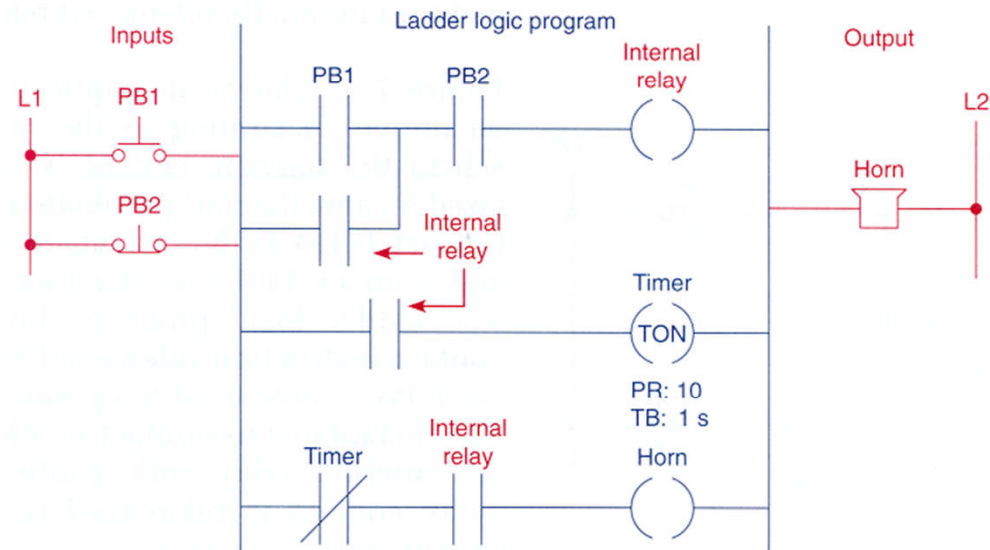

(b) Ladder logic


**Fig. 7-13**

Starting-up warning signal circuit.

# Ladder diagram

## Example of *timer on-delay*

Coil is energized if the switch remains closed for 12 seconds

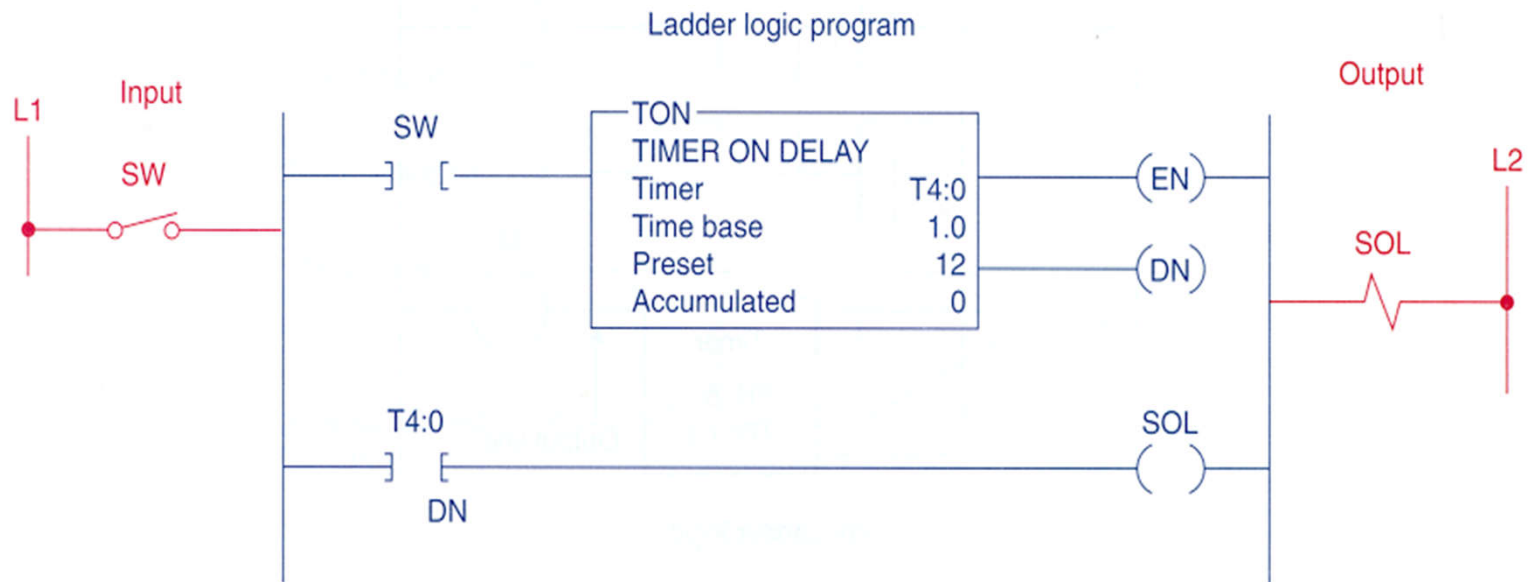


**Fig. 7-14**

Solenoid valve timed closed.


# Ladder diagram
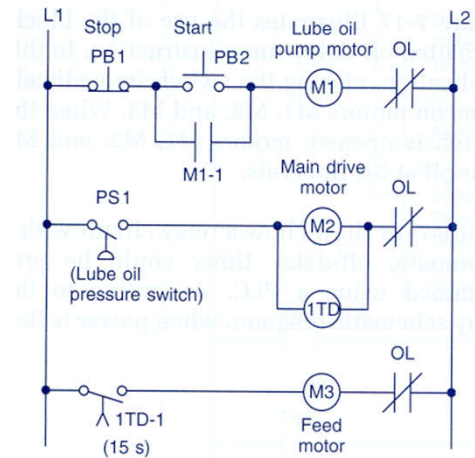
## Example of *timer on-delay*

- If PB2 is activated, powers on the oil pumping motor.
- When the pressure augments, PS1 detects the increase and activates the main motor.
- 15 seconds later the main drive motor starts.



(a) Relay ladder schematic diagram

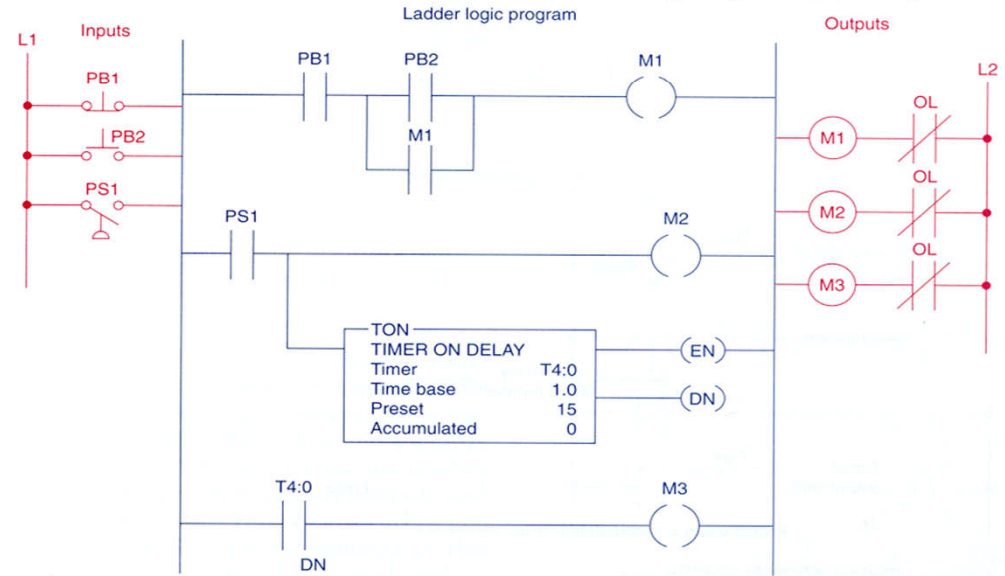


(b) Ladder logic

**Fig. 7-15**  
Automatic sequential control system.

# Ladder diagram


## Example of *timer* programmed as *off-delay*

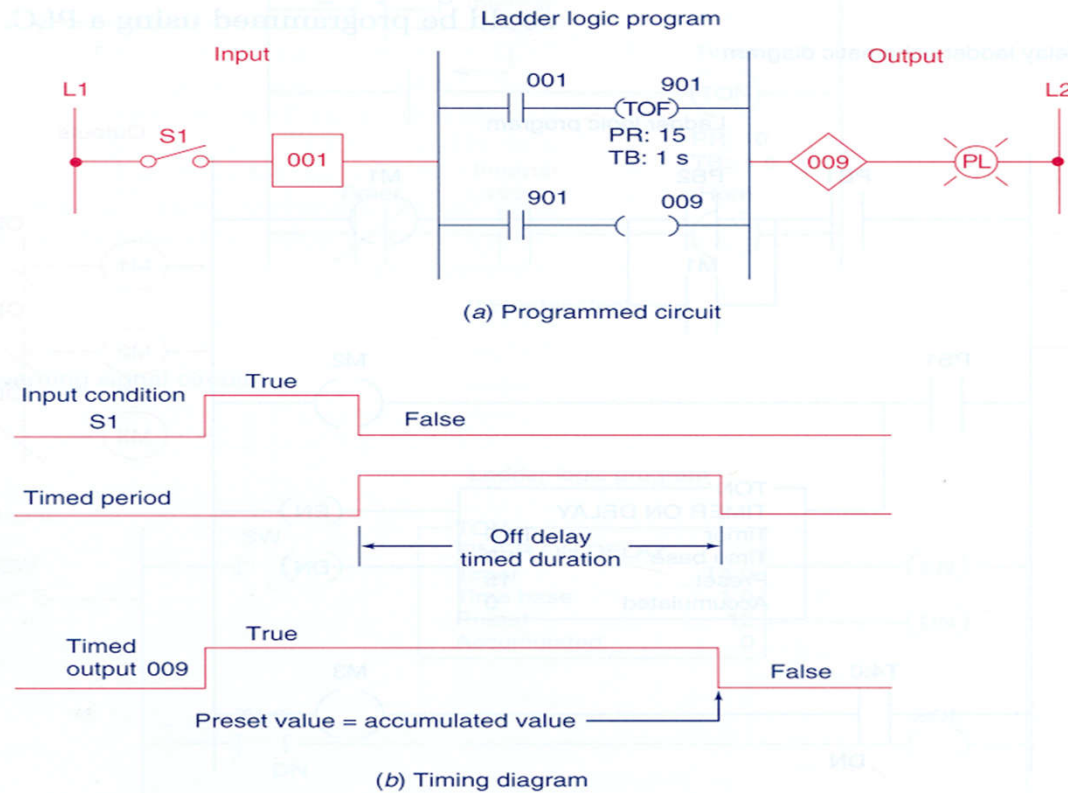

**Fig. 7-16**  
Off-delay programmed timer.

# Ladder diagram

## Example of *timer* programmed as *off-delay*

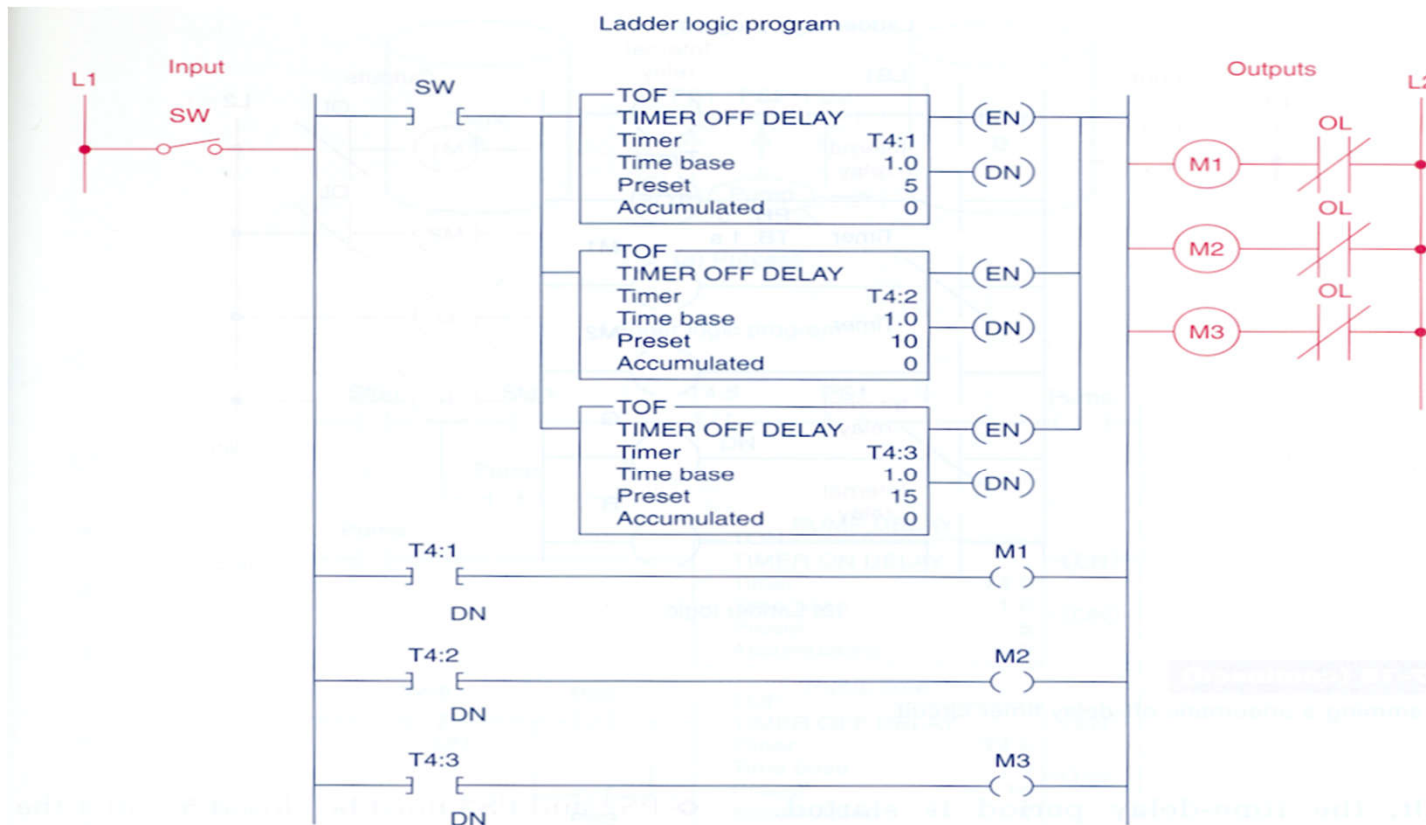


**Fig. 7-17**

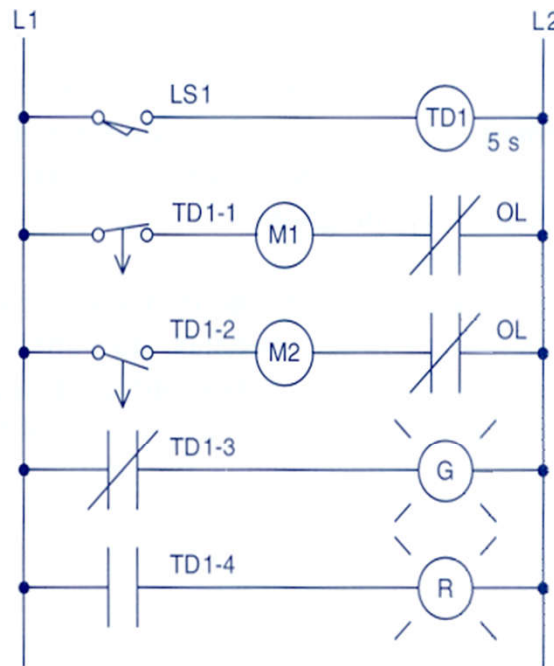
Off-delay timer instructions programmed to switch motors off at 5-s intervals.

# Ladder diagram

## Example of *timer* programmed as *off-delay*



(a) Relay schematic diagram

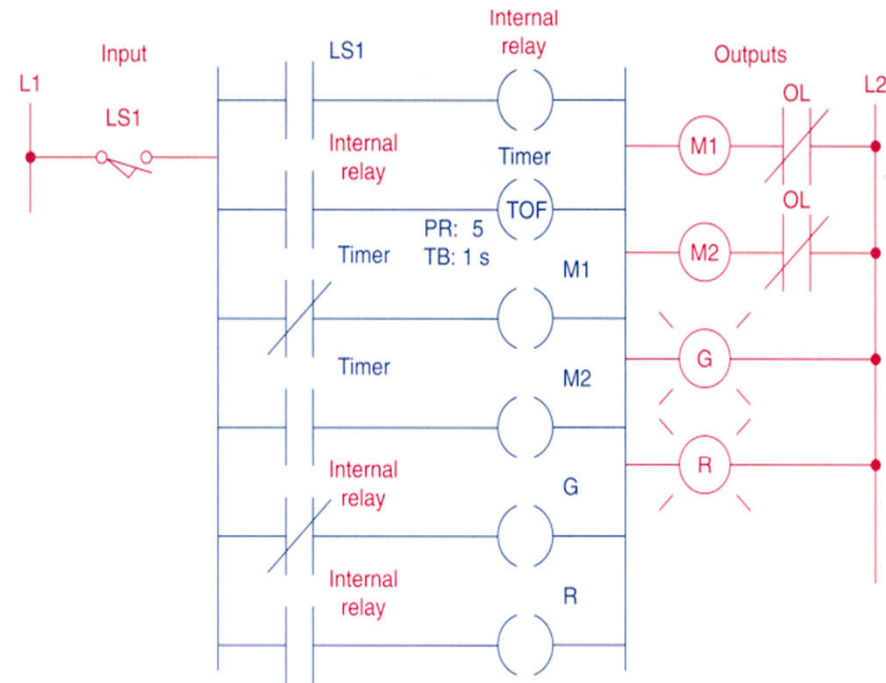

(b) Ladder logic

**Fig. 7-18**

Programming a pneumatic off-delay timer circuit.

**Fig. 7-18 (continued)**

Programming a pneumatic off-delay timer circuit.

# Ladder diagram

Example of *timers* programmed as *off-delay* and *on-delay*

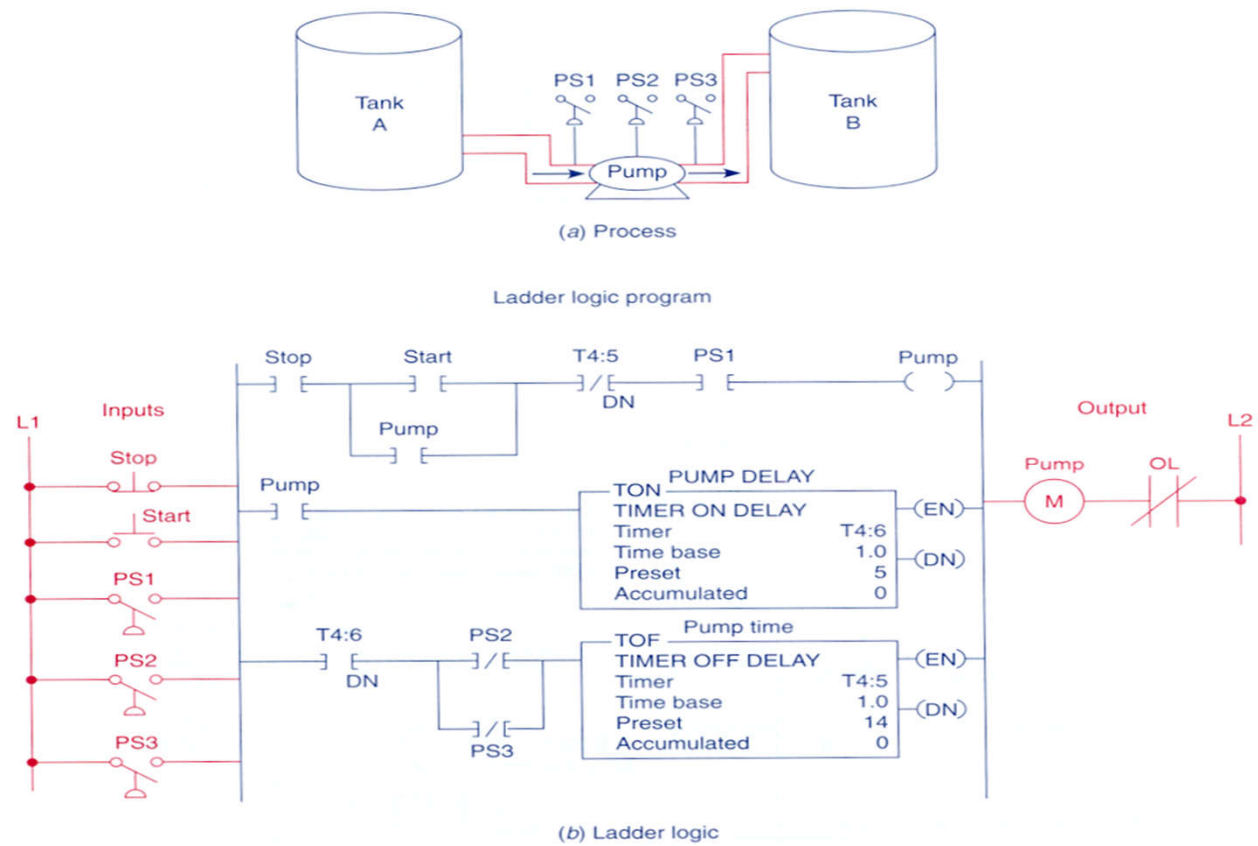



Fig. 7-19



# Ladder diagram


## *Timers*

**Animated demonstration:**

 

# Ladder diagram


## Retentive Timers

 


Motor accumulated motion (rotation) defines the on/off timing.

**Fig. 7-20**

Electromechanical retentive timer.

 


(b) Timing chart

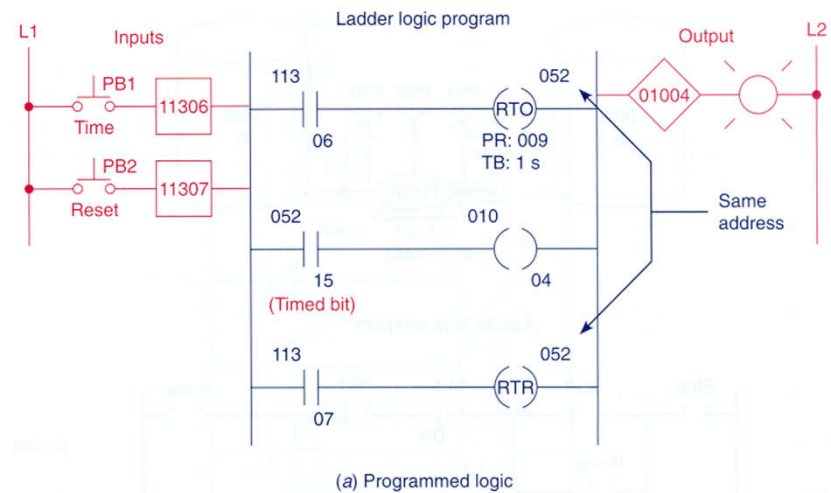

(a) Programmed logic

# Ladder diagram

## Example of *retentive timers*

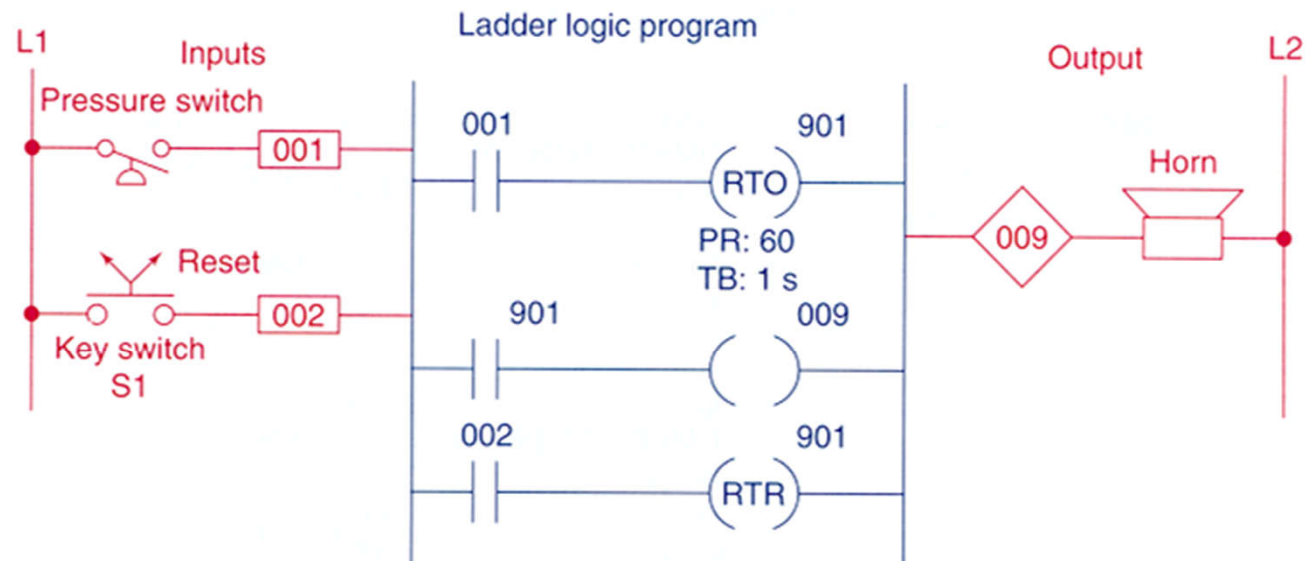


**Fig. 7-22**

Retentive on-delay alarm program.

## ~~adder~~ Timers
 
### Animated demonstration:

*(search this function on Schneider PLCs or discuss implementation)*



*T000 = retentive timer*

*0002 = push button (counted while ON)*


*0001 = reset push button*

*0500 = lamp output*

# Ladder diagram

## Example:

- SW ON to start operation
- Before motor starts, lubricate 10 s with oil.
- SW OFF to stop. (lubricate 15 s more).
- After 3 hours of pump operation, stop motor and signal with pilot light.
- Reset available after servicing.

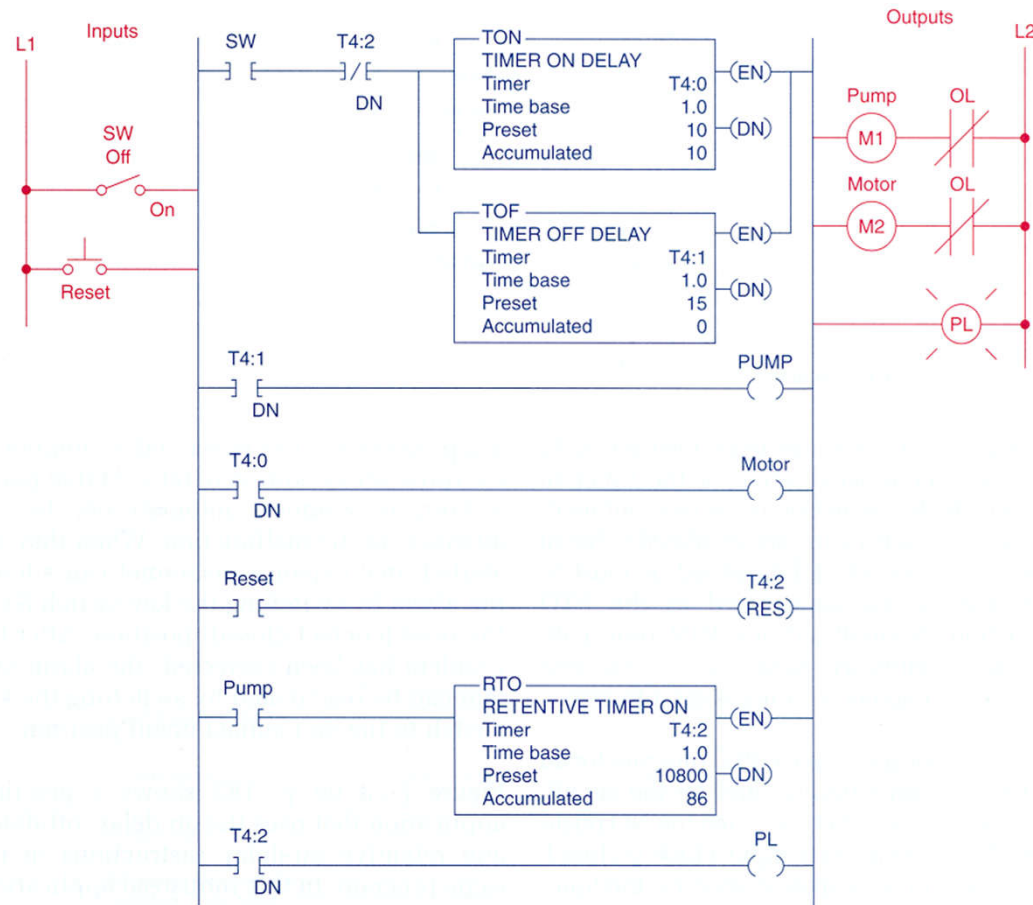


**Fig. 7-23**

Bearing lubrication program.

# Ladder diagram

## Cascaded Timers

 

**Fig. 7-24**


Sequential time-delayed motor-starting circuit.

*Start 3 motors*

*T=0, t=20, t=40sec*

# Ladder diagram

## *Cascaded Timers (bistable system)*

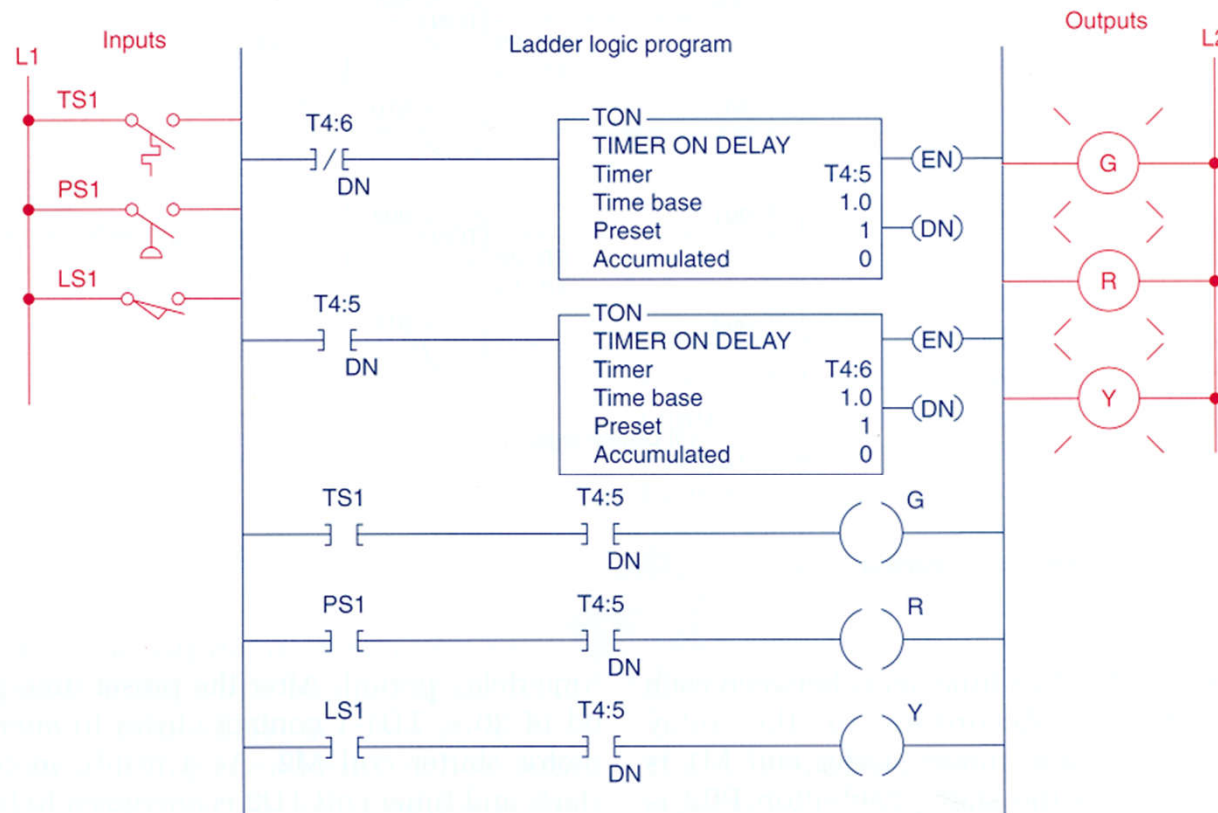


**Fig. 7-25**

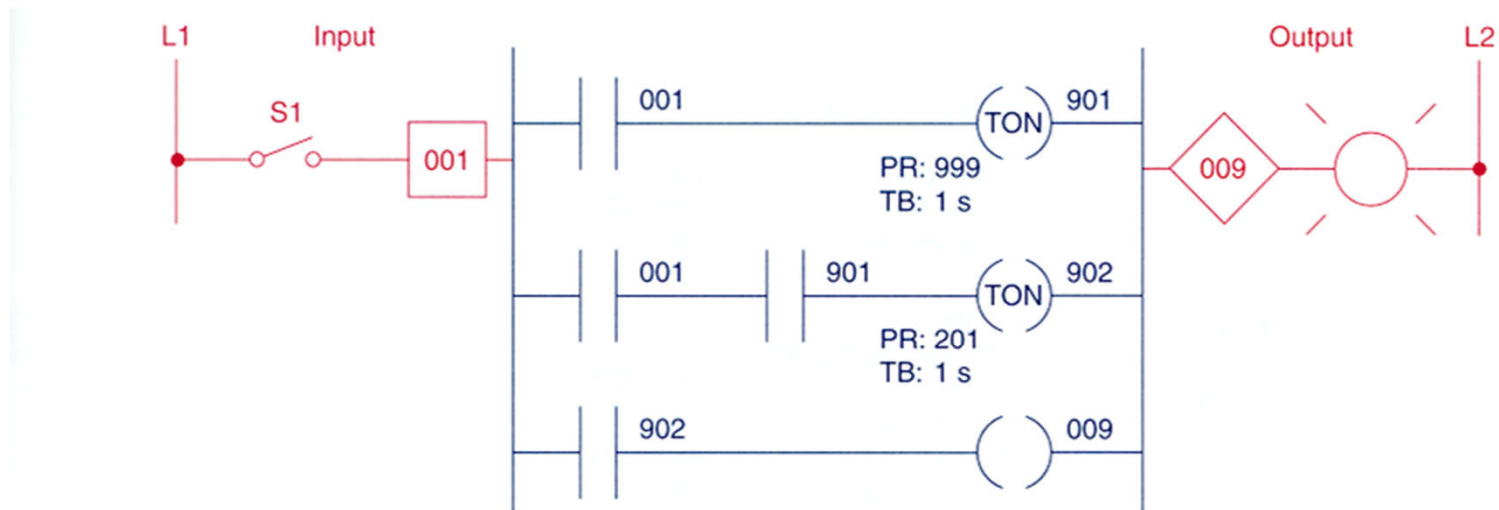Annunciator flasher program.

# Ladder diagram

## Timers for very long time intervals





**Fig. 7-26**

Cascading of timers for longer time delays.



# Ladder diagram

## Example of a semaphore

 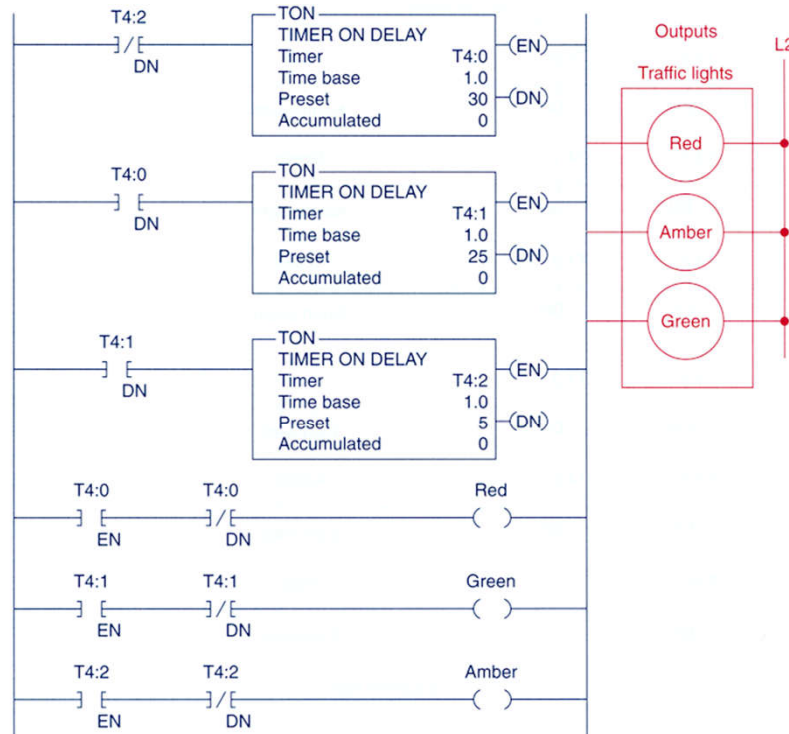


Red 30 s on  
 Green 25 s on  
 Amber 5 s on



**Fig. 7-27**

Control of traffic lights in one direction.

# Ladder diagram Example of a semaphore

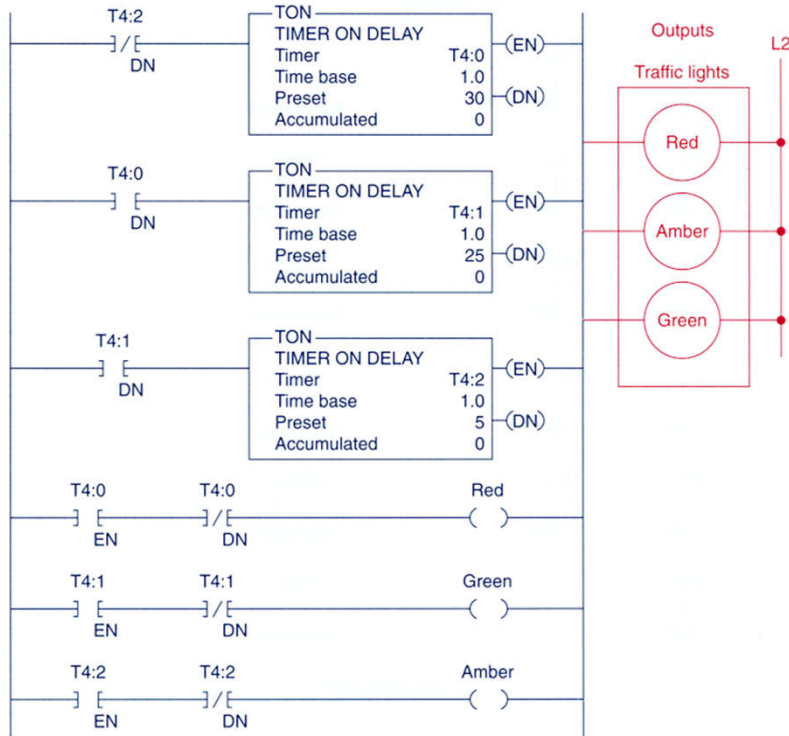


Red	30 s on
Green	25 s on
Amber	5 s on

  

**Example of a semaphore in both directions**

Red	30 s on
Green	25 s on
Amber	5 s on

 

Red = north/south		Green = north/south	Amber = north/south
Green = east/west	Amber = east/west	Red = east/west	





(b) Timing chart

**Fig. 7-28 (continued)**

Control of traffic lights in two directions.

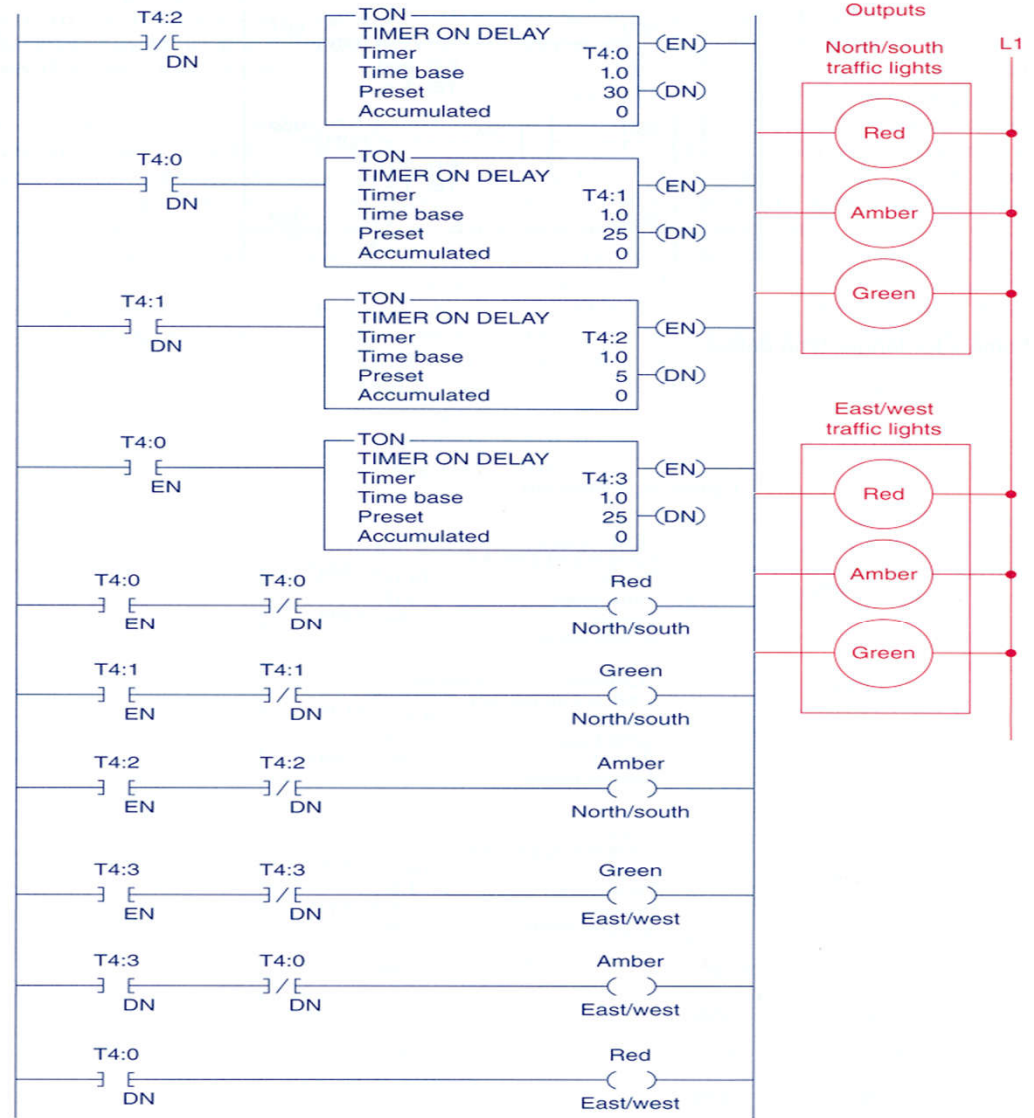 
Example of a semaphore in both directions




(a) Ladder logic

**Fig. 7-28** Control of traffic lights in two directions.
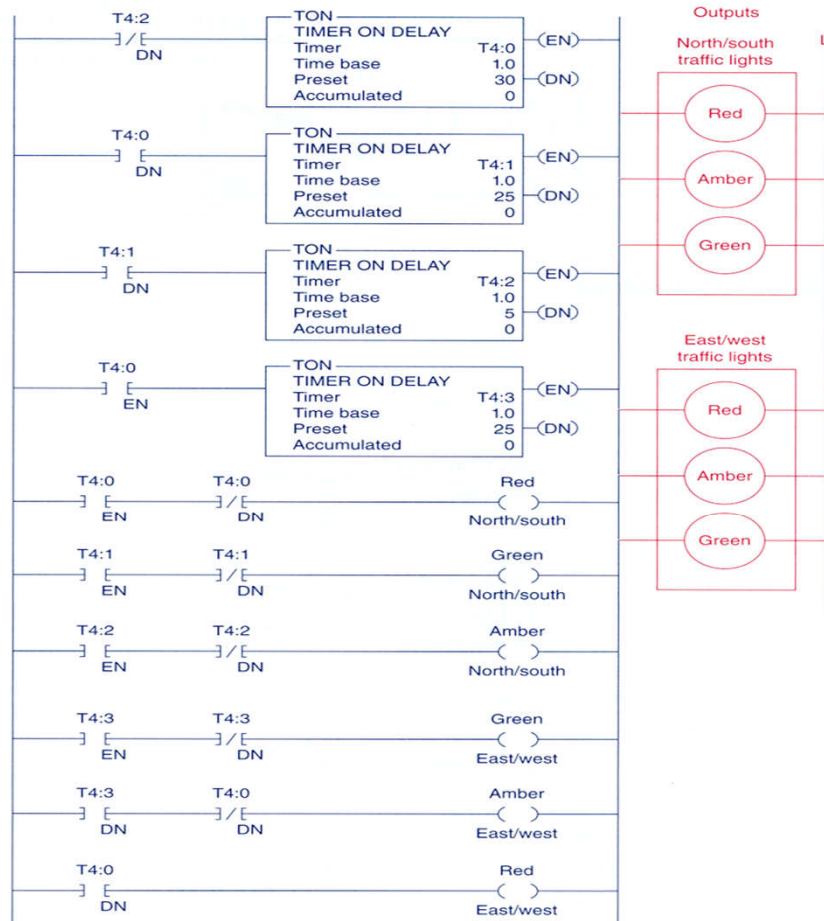
### Example of a semaphore in both directions




(a) Ladder logic

 


**Fig. 7-28**  
Control of traffic lights in two directions.

# Ladder diagram

## Counters

 

Some applications...

 


**Fig. 8-3**

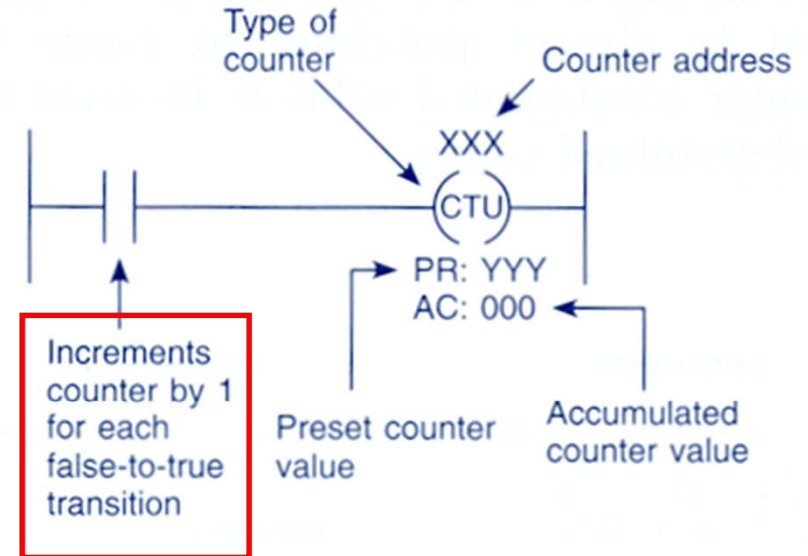
Counter applications. (Courtesy of Dynapar Corporation, Gurnee, Illinois.)

## Ladder diagram

### Implementation of Counters in the PLC-5 of Allen-Bradley:



### Internal structure representation

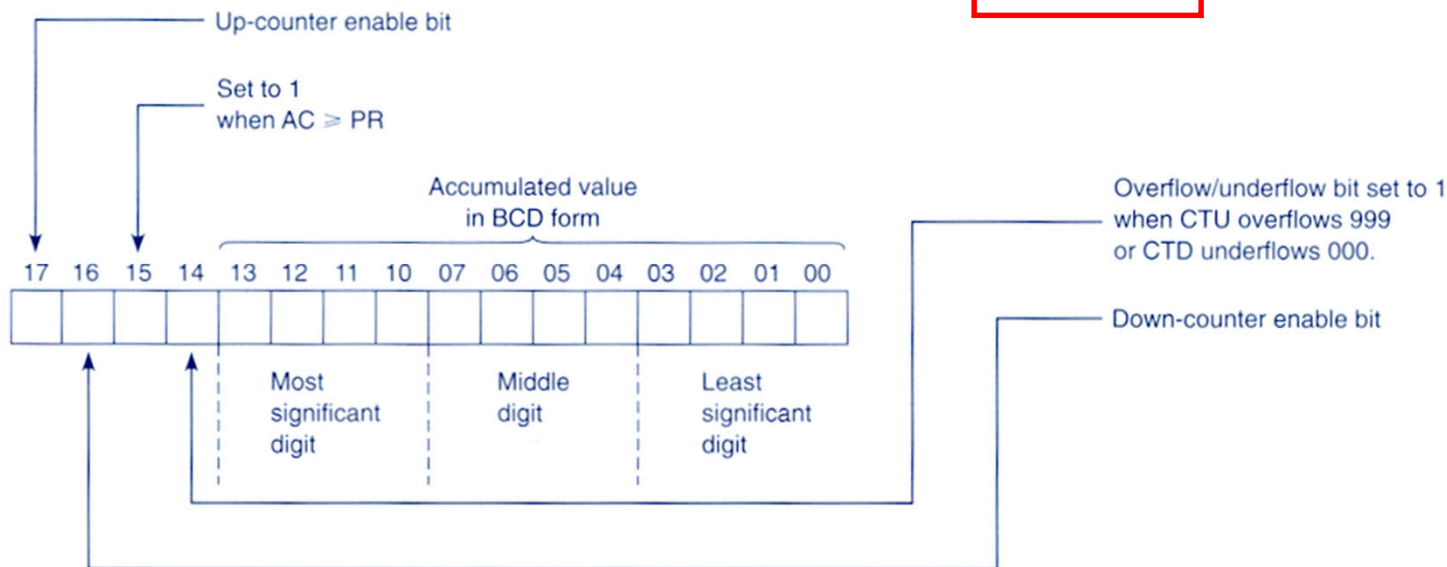


(b) Allen-Bradley PLC-2 timer accumulated value word (bit addressing is in octal)


## Ladder diagram

### Implementation of Counters in the PLC-5 of Allen-Bradley:

Two alternative representations:

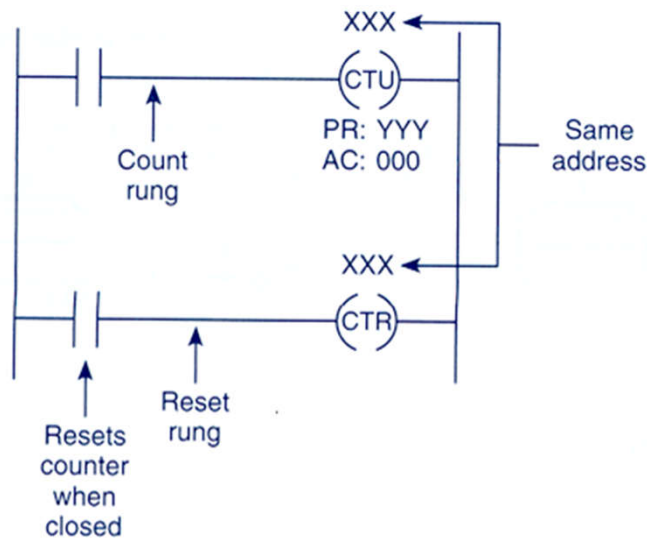

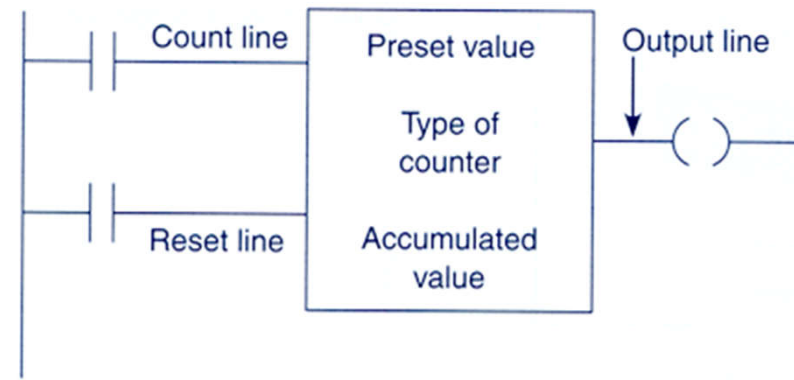**Coil-formatted** counter and reset instructions





**Block-formatted** counter instruction



# Ladder diagram

## Up-counters

 
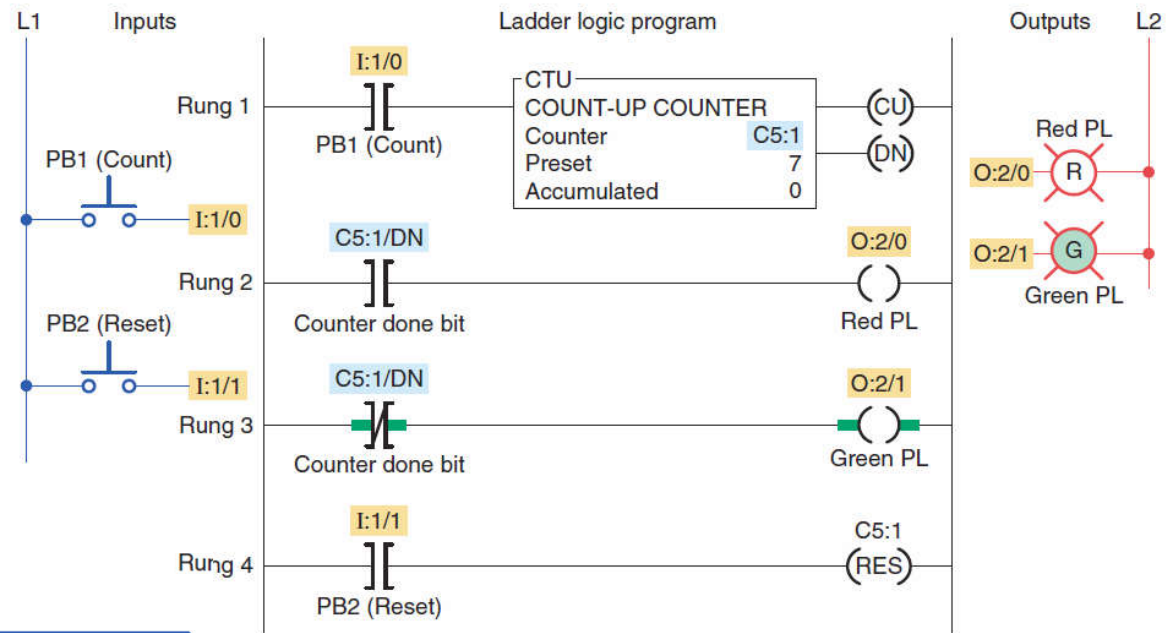


Usage of an **incremental up-counter** and the corresponding **temporal diagram:**

PB1 increments counting  
PB2 resets the counting


# Ladder diagram

**Example:**  
*Counting parts*

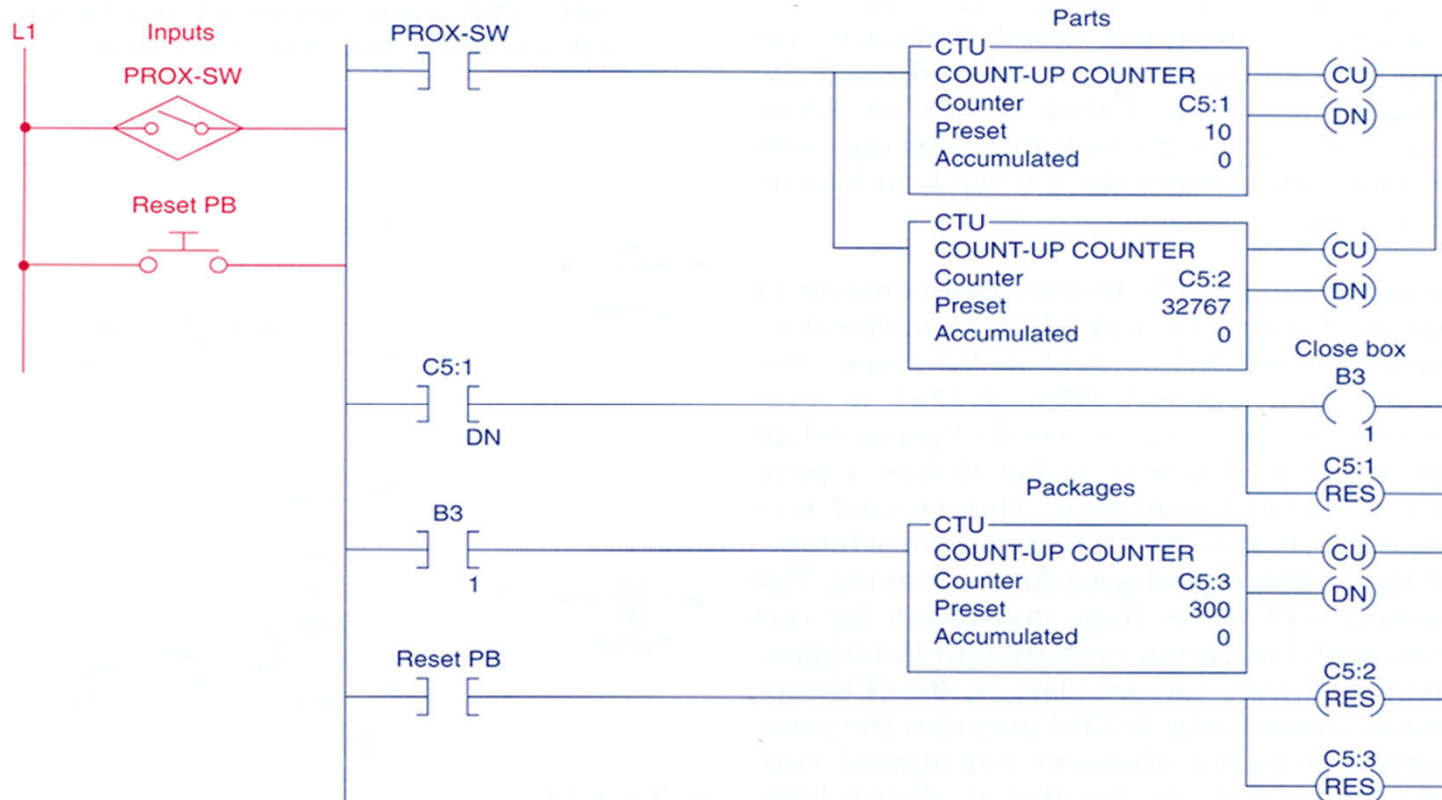 


# Ladder diagram

## Example

 

(a) Process flow diagram

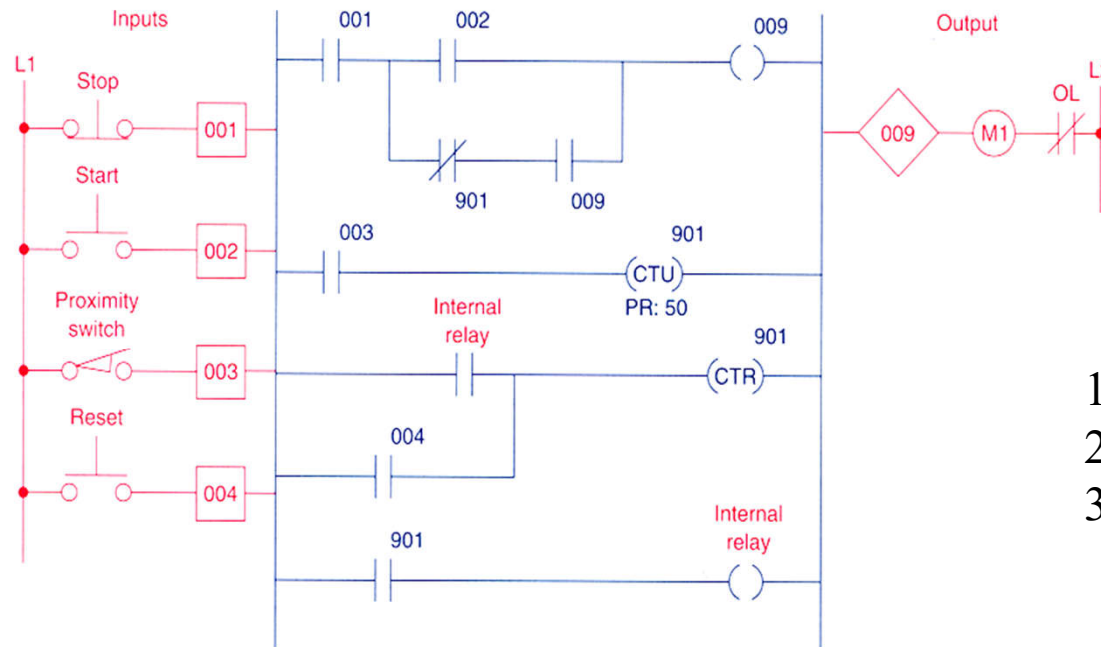

(b) Program


1. Start conveyor motor
2. Passing cases increment counter
3. After 50 cases, stop motor

**Fig. 8-13**

Conveyor motor program.

# Ladder diagram

## *Up/down-counters*

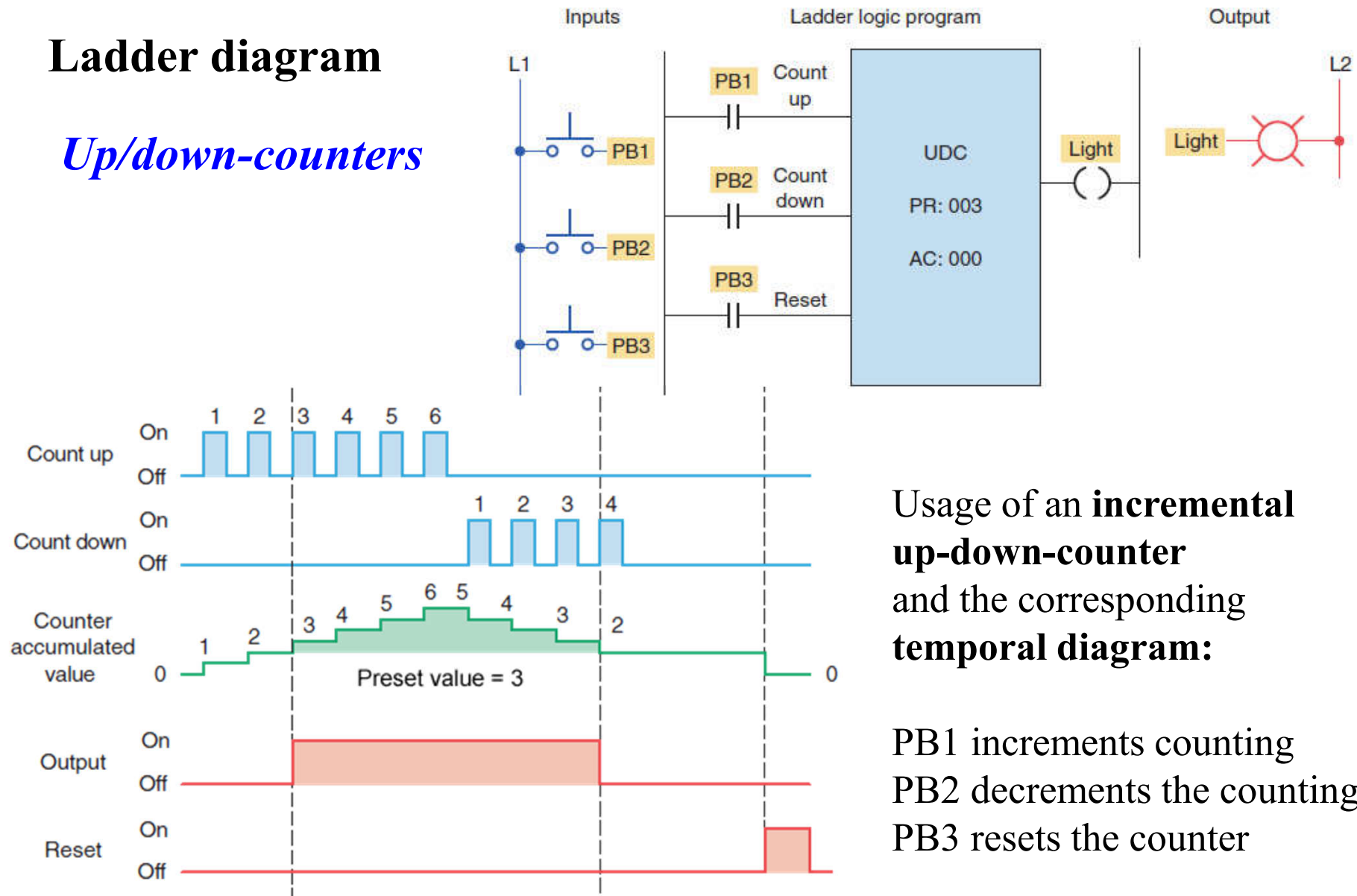

Usage of an **incremental up-down-counter** and the corresponding **temporal diagram:**


PB1 increments counting  
 PB2 decrements the counting  
 PB3 resets the counter

# Ladder diagram

## *Up/down-counters*

**Example:**

Finite parking garage

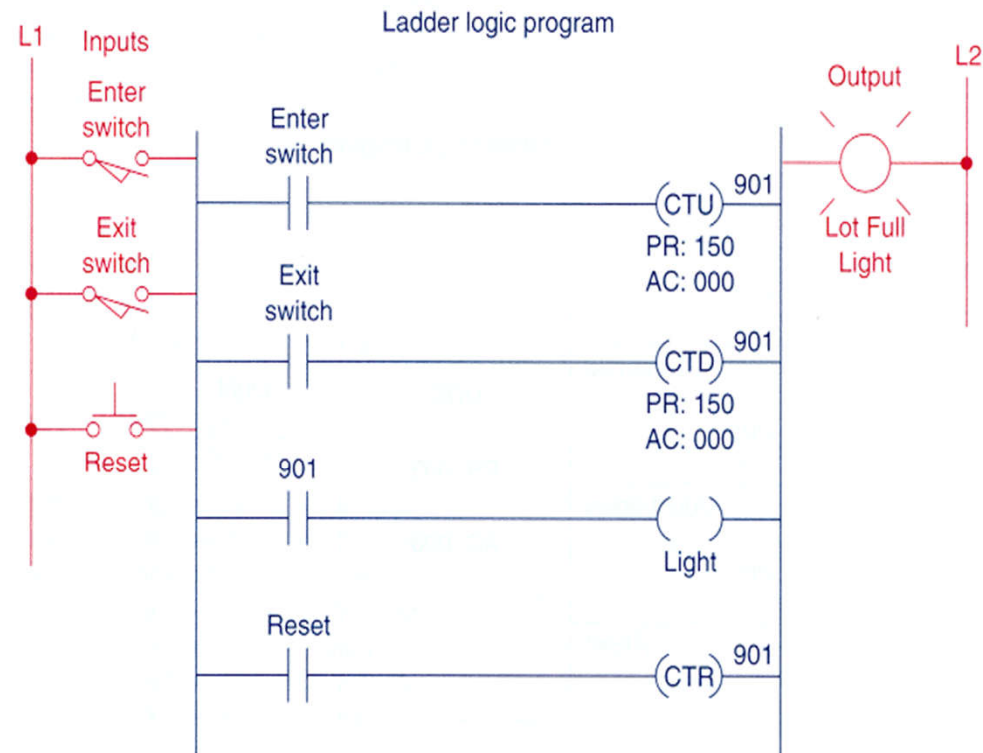


**Fig. 8-17**

Parking garage counter.

# Ladder diagram

## Cascaded Counters

Example:

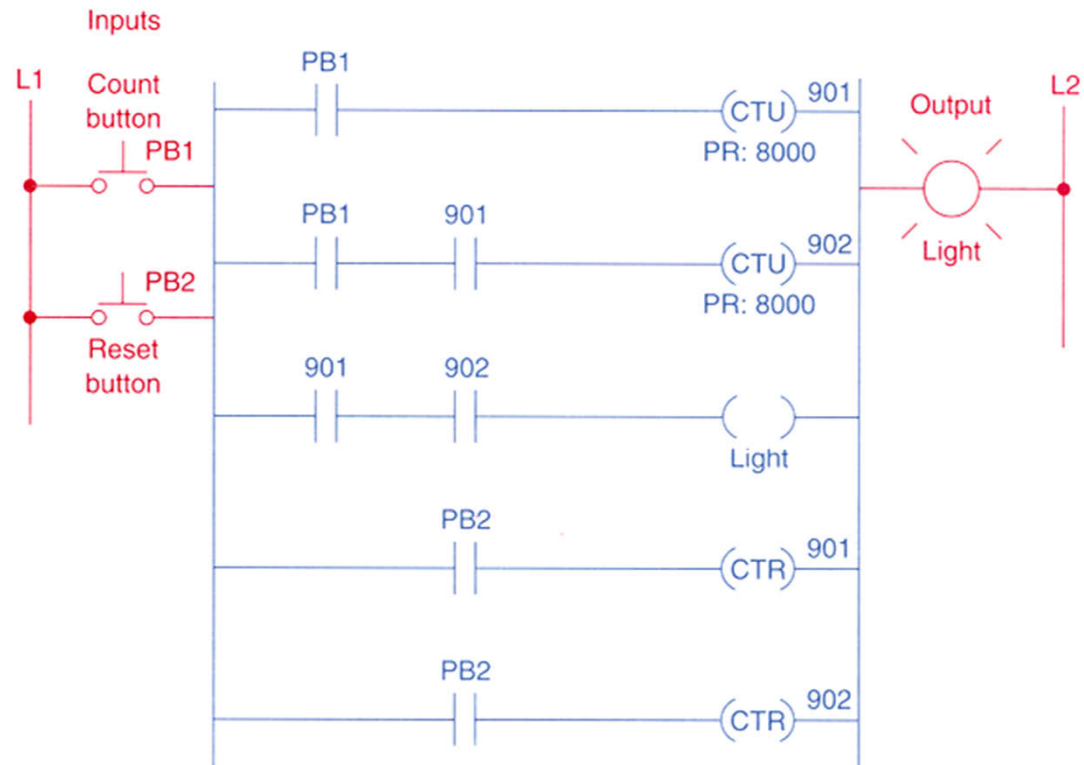

**Fig. 8-21**

Counting beyond the maximum count.


# Ladder diagram

## *Cascaded Counters*

**Example:**

24 hours clock

*Note “auto-reset” of counters after “count-done”.*

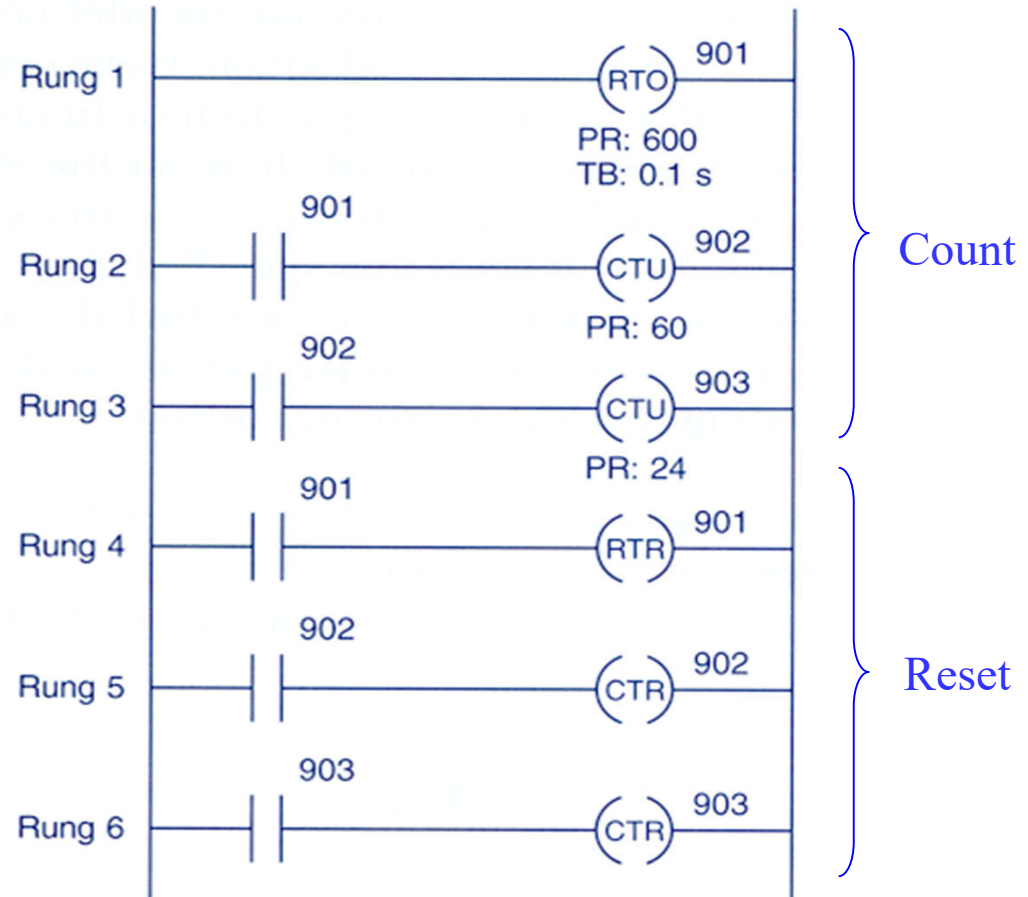

**Fig. 8-23**


A 24-h clock program.

# Ladder diagram

## Cascaded Counters

### Example:

Memory time of event  
*Internal relay OFF* stops clock

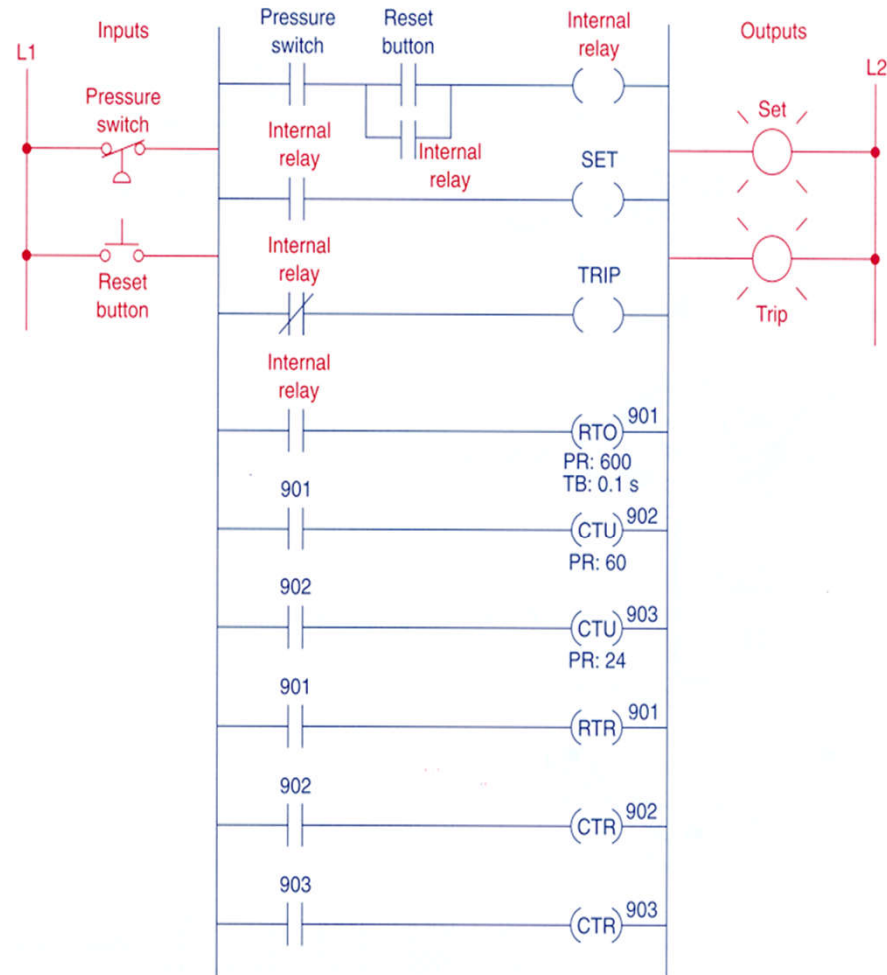


**Fig. 8-24**  
 Program for monitoring the time of an event.



# Ladder diagram


## Incremental Encoder

counter measures **rotation angle** or **rotation speed** (if divided by time)

 

**Fig. 8-26**

Cutting objects to a specified size.

 


**Fig. 8-25**

Incremental encoder. (Courtesy of BEI Motion Systems Company.)


# Ladder diagram

## Incremental *Encoder*

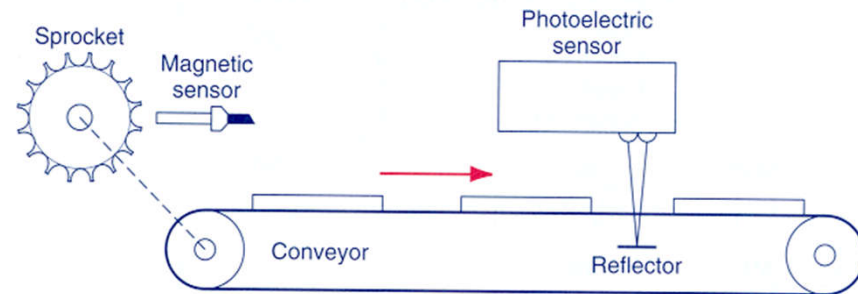**Example:**  
counter as a "length sensor"



(a) Process

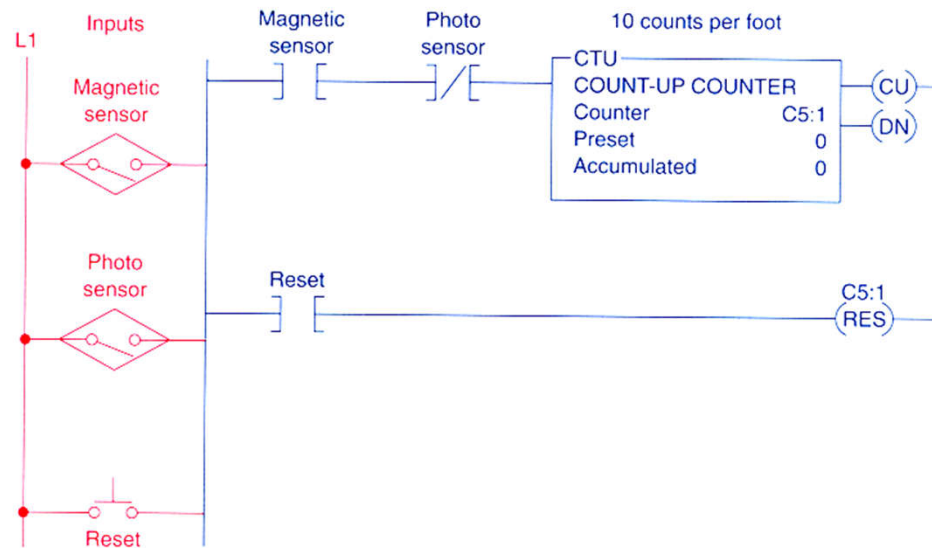

(b) Program

**Fig. 8-27**


Counter used for length measurement.

## Ladder diagram
 
### Example with counters and timers (cont.):

Specs:

- Starts M1 conveyor upon pushing button .
- After 15 plates stops M1 and starts conveyor M2 .
- M2 operates for 5 seconds and then stops.
- Restart sequence.



(a) Process

# Ladder diagram

## Example with counters and timers (cont.):

Specs:

- Starts M1 conveyor upon pushing button .
- After 15 plates stops M1 and starts conveyor M2 .
- M2 operates for 5 seconds and then stops.
- Restart sequence.

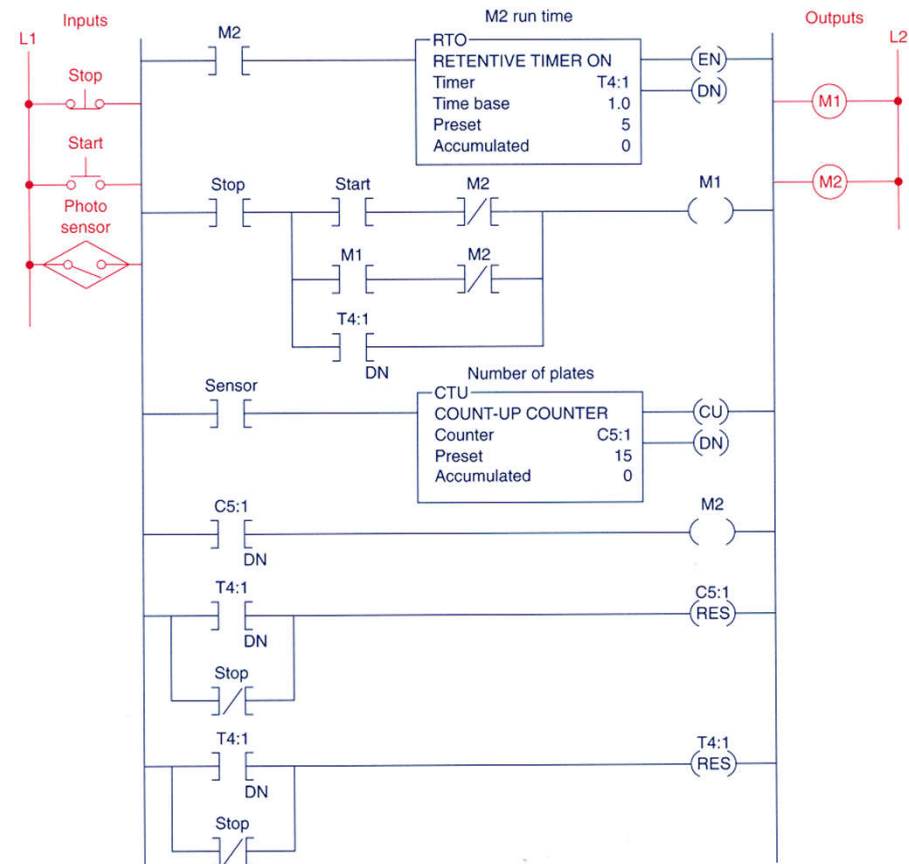


Fig. 8-28

Automatic stacking program.


(b) Program

# Ladder diagram

## Example with counters and timers (cont.):

Specs:

- Starts M1 conveyor upon pushing button .
- After 15 plates stops M1 and starts conveyor M2 .
- M2 operates for 5 seconds and then stops.
- Restart sequence.

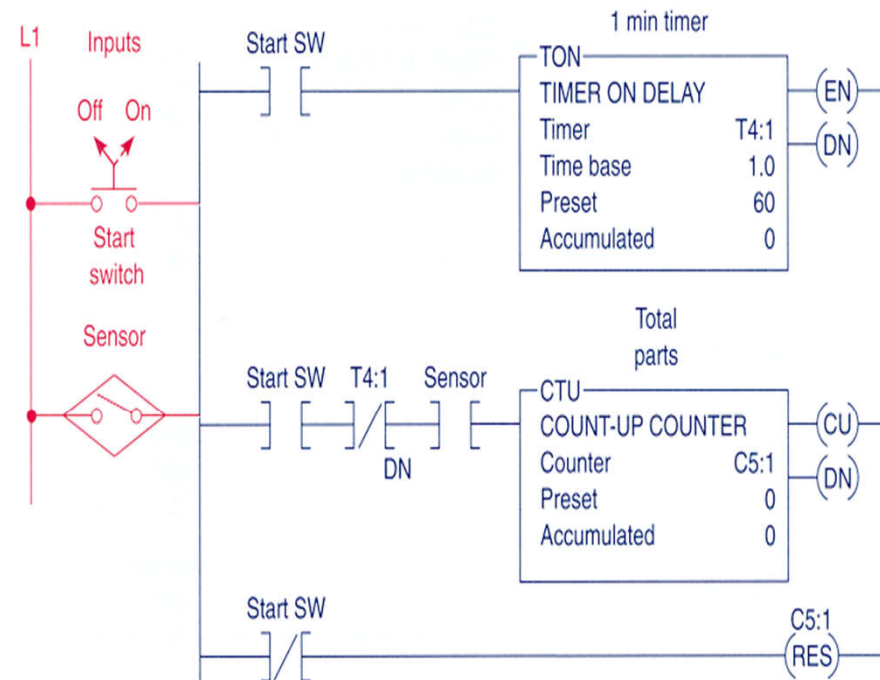


**Fig. 8-30**

Product flow rate program.

# Ladder diagram

## Example with counters and timers (cont.):

To use a timer to command a counter, to implement large periods of time.

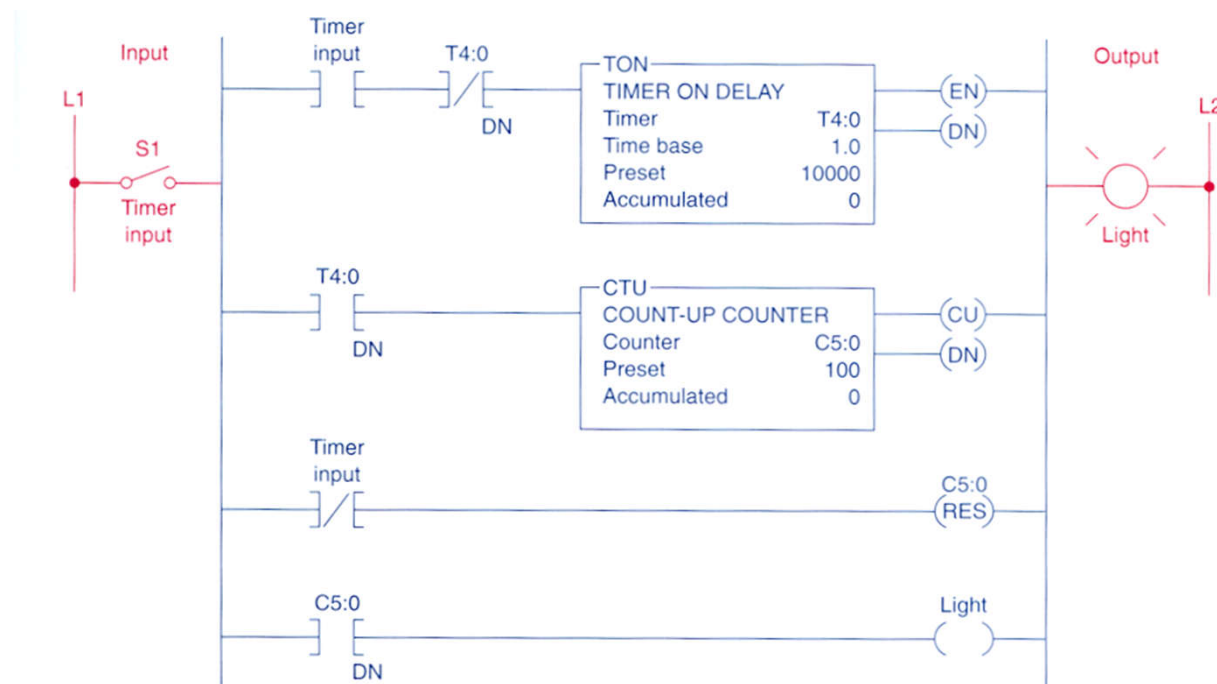


**Fig. 8-31**

Timer driving a counter to produce an extremely long time-delay period.

# Ladder diagram


## Counters

Example:

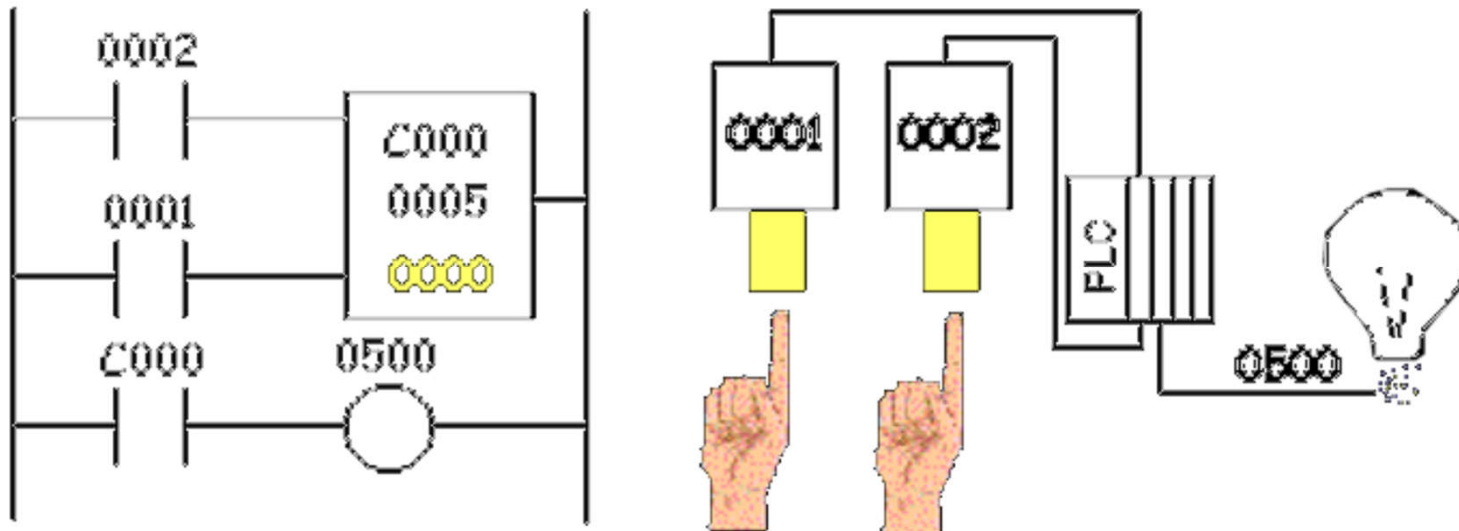

# Ladder diagram

## Counters in PL7

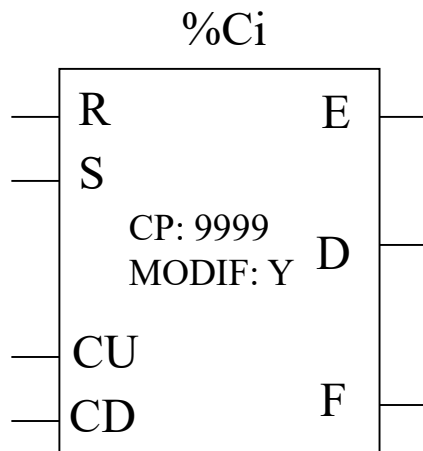


## Characteristics:

Identifier: %Ci	0..31 in the TSX37
Value progr.:	%Ci.P 0...9999 (def.)
Value Actual:	%Ci.V 0...Ci.P (only to be read)
Modifiable:	Y/N can be modified from the console
Inputs:	R Reset Ci.V=0 S Preset Ci.V=Ci.P CU <i>Count Up</i> CD <i>Count Down</i>
Outputs:	E Overrun %Ci.E=1 %Ci.V=0->9999 D Done %Ci.D=1 %Ci.V=Ci.P F Full %Ci.F=1 %Ci.V=9999->0



# Ladder diagram


## Counters in Unity Pro

 

**CU "0" to "1"** => CV is incremented by 1

**CV ≥ PV** => Q:=1

**R=1** => CV:=0

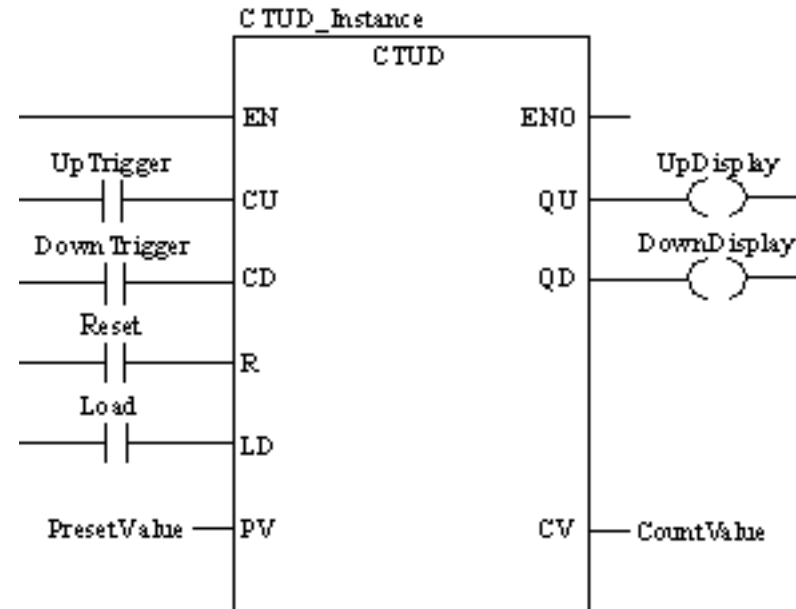

**CU "0" to "1"** => CV is incremented by 1

**CD "0" to "1"** => CV is decremented by 1

**CV ≥ PV** => QU:=1

**CV ≤ 0** => QD:=1

**R=1** => CV:=0    **LD=1** => CV:=PV

R has precedence over LD

*NOTE: counters are saturated such that no overflow occurs*

# Ladder diagram

## Numerical Processing


### Algebraic / Arithmetic and Logic Functions

Note:

- %M memory
- %K constant
- %S system

Compare block →

Operate block →

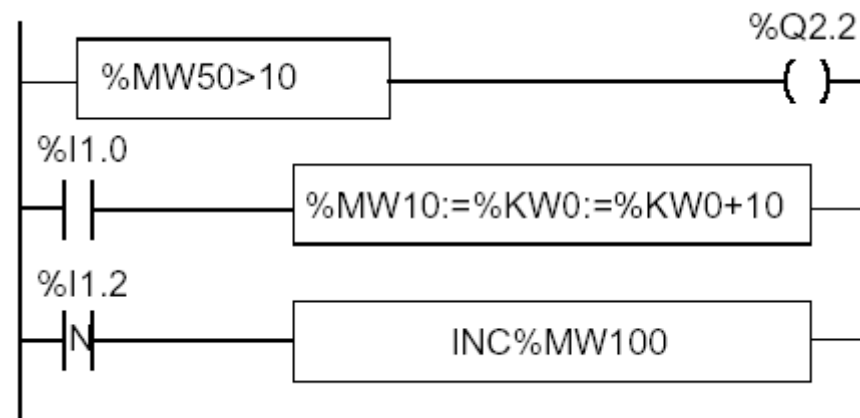

## Ladder diagram

### Numerical Processing

#### Arithmetic Functions

<b>+</b>	addition of two operands	<b>SQRT</b>	square root of an operand
<b>-</b>	subtraction of two operands	<b>INC</b>	incrementation of an operand
<b>*</b>	multiplication of two operands	<b>DEC</b>	decrementation of an operand
<b>/</b>	division of two operands	<b>ABS</b>	absolute value of an operand
<b>REM</b>	remainder from the division of 2 operands		

#### Operands


Type	Operand 1 (Op1)	Operand 2 (Op2)
Indexable words	%MW	%MW,%KW,%Xi.T
Non-indexable words	%QW,%SW,%NW,%BLK	Imm.Val.,%IW,%QW,%SW,%NW,%BLK, Num.expr.
Indexable double words	%MD	%MD,%KD
Non-indexable double words	%QD,%SD	Imm.Val.,%ID,%QD,%SD, Numeric expr.

# Ladder diagram

## Numerical Processing

### Example:

#### Arithmetic functions

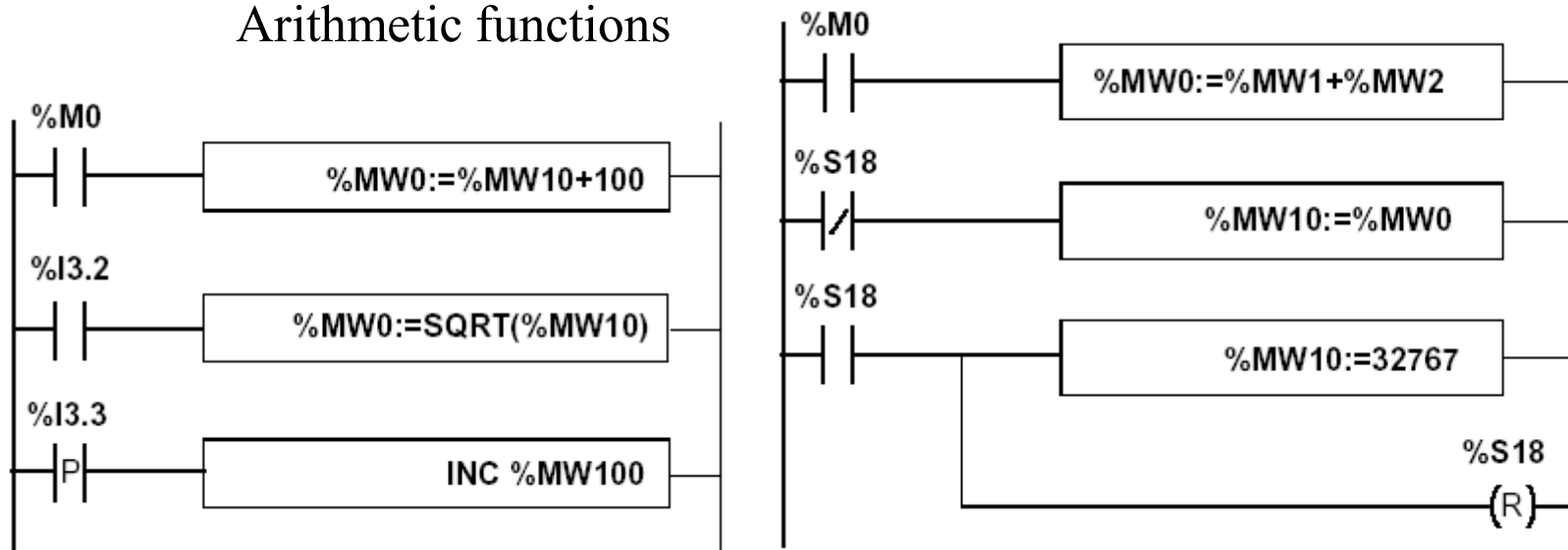

Use of a system variable:

`%S18` – flag de overflow

## Ladder diagram

### Numerical Processing

#### Logic Functions

<b>AND</b>	AND (bit by bit) between two operands
<b>OR</b>	logical OR (bit by bit) between two operands
<b>XOR</b>	exclusive OR (bit by bit) between two operands
<b>NOT</b>	logical complement (bit by bit) of an operand

Comparison instructions are used to compare two operands.

- >: tests whether operand 1 is greater than operand 2,
- >=: tests whether operand 1 is greater than or equal to operand 2,
- <: tests whether operand 1 is less than operand 2,
- <=: tests whether operand 1 is less than or equal to operand 2,
- =: tests whether operand 1 is different from operand 2.

#### Operands


Type	Operands 1 and 2 (Op1 and Op2)
Indexable words	%MW, %KW, %Xi.T
Non-indexable words	Imm.val., %IW, %QW, %SW, %NW, %BLK, Numeric Expr.
Indexable double words	%MD, %KD
Non-indexable double words	Imm.val., %ID, %QD, %SD, Numeric expr.

# Ladder diagram

## Numerical Processing

### Example:

Logic functions

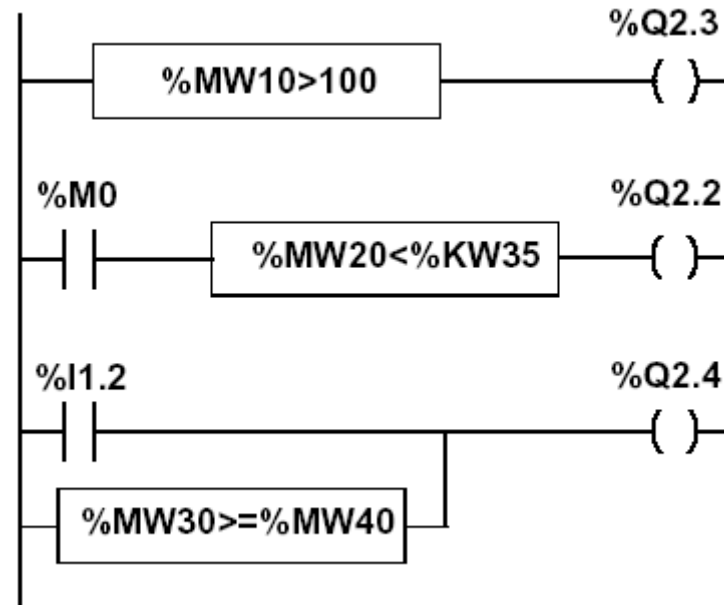

## Ladder diagram

### Numerical Processing

#### Priorities on the execution of the operations

Rank	Instruction
1	Instruction to an operand
2	*,/,REM
3	+,-
4	<,>,<=,>=
5	=,<>
6	AND
7	XOR
8	OR

## Ladder diagram

### Structures for Control of Flux

#### JUMP instructions:

##### Conditional and unconditional

---

Jump instructions are used to go to a programming line with an %Li label address:

- **JMP**: unconditional program jump
  - **JMPC**: program jump if the instruction's Boolean result from the previous test is set at 1
  - **JMPCN**: program jump if the instruction's Boolean result from the previous test is set at 0. %Li is the label of the line to which the jump has been made (address i from 1 to 999 with maximum 256 labels)
-



## Ladder diagram


### Structures for Control of Flux

#### Example:

Use of jump instructions
 
#### Attention to:

- **INFINITE LOOPS ...**
- **It is not a good style of programming!...**
- **Does not improve the legibility of the proposed solution.**




# Ladder diagram


## Structures for Control of Flux

### Subroutines



### Call and Return

 

main2

 


SR10

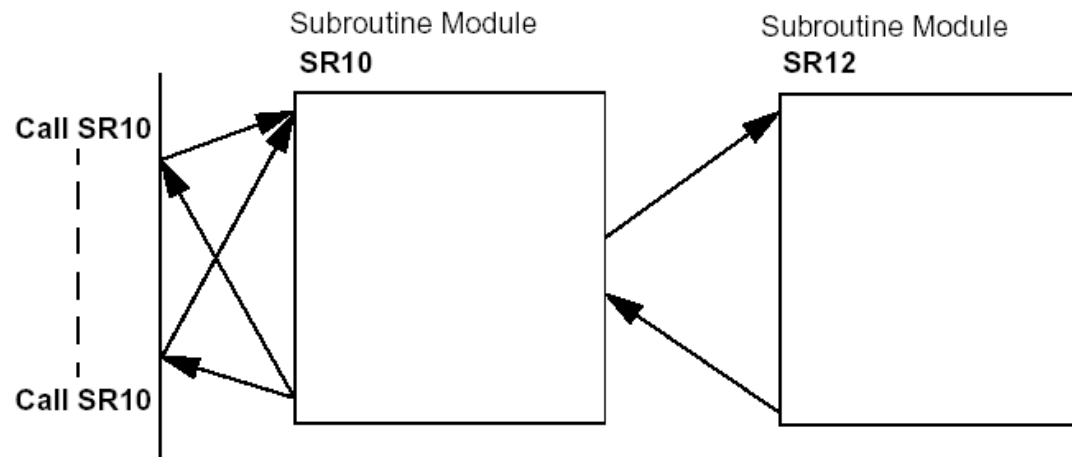 

## Ladder diagram


### Structures for Control of Flux

#### Halt

 

Stops all processes!

#### Events masking

 

## Ladder diagram


**There are other advanced instructions (see manual)**

- **Monostable**
- **Registers of 256 words (LIFO ou FIFO)**
- ***DRUMs***
- **Comparators**
- ***Shift-registers***
- **...**
- **Functions to manipulate *floats***
- **Functions to convert bases and types**


# Ladder diagram

## Numerical Tables

Type	Format	Maximum address	Size	Write access
Internal words	Simple length	%MWi:L	i+L<=Nmax (1)	Yes
	Double length	%MWDi:L	i+L<=Nmax-1 (1)	Yes
	Floating point	%MFi:L	i+L<=Nmax-1 (1)	Yes
Constant words	Single length	%KWi:L	i+L<=Nmax (1)	No
	Double length	%KWDi:L	i+L<=Nmax-1 (1)	No
	Floating point	%KFi:L	i+L<=Nmax-1 (1)	No
System word	Single length	%SW50:4 (2)	-	Yes

 

## Ladder diagram [Schneider Micro PLC, system information: system bits](#)

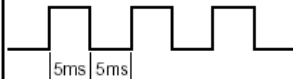Bit	Function	Description	Initial state	TSX37	TSX57
%S0	Cold start	Normally on 0, this bit is set on 1 by: <ul style="list-style-type: none"> <li>● loss of data on power restart (battery fault),</li> <li>● the user program,</li> <li>● the terminal,</li> <li>● cartridge uploading,</li> <li>● pressing on the RESET button.</li> </ul> This bit goes to 1 during the first complete cycle. It is reset to 0 before the following cycle. (Operation)	0	YES	YES
%S1	Warm restart	Normally on 0, this bit is set on 1 by: <ul style="list-style-type: none"> <li>● power restart with data save,</li> <li>● the user program,</li> <li>● the terminal.</li> </ul> It is reset to 0 by the system at the end of the first complete cycle and before output is updated. (Operation)	0	YES	YES
%S4	Time base 10ms	An internal timer regulates the change in status of this bit. It is asynchronous in relation to the PLC cycle. Graph : 	-	YES	YES
%S5	Time base 100 ms	Idem %S4	-	YES	YES
%S6	Time base 1 s	Idem %S4	-	YES	YES
%S7	Time base 1 mn	Idem %S4	-	YES	YES

**See manual  
for the remaining  
100 bits generated...**

## Ladder diagram [Schneider Micro PLC, System information: system \*words\*](#)

Words	Function	Description	Management
%SW0	Master task scanning period	The user program or the terminal modify the duration of the master task defined in configuration. The duration is expressed in ms (1.255 ms) %SW0=0 in cyclic operation. On a cold restart: it takes on the value defined by the configuration.	User
%SW1	Fast task scanning period	The user program or the terminal modify the duration of the fast task as defined in configuration. The duration is expressed in ms (1.255 ms) On a cold restart: it takes on the value defined by the configuration.	User
%SW8	Acquisition of task input monitoring	Normally on 0, this bit can be set on 1 or 0 by the program or the terminal. It inhibits the input acquisition phase of each task. <ul style="list-style-type: none"> <li>● %SW8:X0 =1 assigned to MAST task: outputs linked to this task are no longer guided.</li> <li>● %SW8:X1 =1 assigned to FAST task: outputs linked to this task are no longer guided.</li> </ul>	User
%SW9	Monitoring of task output update	Normally on 0, this bit can be set on 1 or 0 by the program or the terminal. Inhibits the output updating phase of each task. <ul style="list-style-type: none"> <li>● %SW9:X0 =1 assigned to MAST task: outputs linked to this task are no longer guided.</li> <li>● %SW9:X1 =1 assigned to FAST task: outputs linked to this task are no longer guided.</li> </ul>	User
%SW10	First cycle after cold start	If the bit for the current task is on 0, this indicates that the first cycle is being carried out after a cold start. <ul style="list-style-type: none"> <li>● %SW10:X0: is assigned to the MAST Master task</li> <li>● %SW10:X1: is assigned to the FAST fast task</li> </ul>	System
%SW11	Watchdog duration	Reads the duration of the watchdog as set in configuration. It is expressed in ms (10...500 ms).	System

**See manual  
for the remaining  
140 words generated...**

## Schneider Premium System information: system *bits*, system *words*

Operating Modes

Hide Locate Back Forward Print

Contents Index Search

- Welcome to the Unity Pro On-line Help
- How to Use the On-line Help
- Addendum
- General Safety Instructions
- Compatibility Rules
- Cyber Security
- Unity Pro Software
  - Languages Reference
  - Operating Modes
  - Unity Pro System Bits and Words
    - Safety Information
    - About the Book
    - System Bits**
      - System Bits Introduction
      - Description of System Bits %S0 to %S7
      - Description of System Bits %S9 to %S13
      - Description of System Bits %S15 to %S21
      - Description of System Bits %S30 to %S59
      - Description of System Bits %S62 to %S79
      - Description of System Bits %S80 to %S97
      - Description of System Bits %S100 to **%S124**
    - System Words

Operating Modes

Hide Locate Back Forward Print

Contents Index Search

- Welcome to the Unity Pro On-line Help
- How to Use the On-line Help
- Addendum
- General Safety Instructions
- Compatibility Rules
- Cyber Security
- Unity Pro Software
  - Languages Reference
  - Operating Modes
  - Unity Pro System Bits and Words
    - Safety Information
    - About the Book
    - System Bits
    - System Words
      - System Words %SW0 to %SW127**
        - Description of System Words %SW0 to %SW11
        - Description of System Words %SW12 to %SW29
        - Description of System Words %SW30 to %SW47
        - Description of System Words %SW48 to %SW69
        - Description of Hot Standby Quantum System Words %SW60 to %SW69
        - Description of Hot Standby Premium System Words %SW60 to %SW65
        - Description of System Words %SW70 to %SW99
        - Description of System Words %SW100 to %SW116
        - Description of System Words %SW124 to %SW127
      - Premium/Atrium-specific System Words
        - Description of Premium/Atrium-specific System Words %SW128 to %SW143
        - Description of Premium/Atrium-specific System Words %SW144 to %SW146
        - Description of Premium/Atrium-specific System Words %SW147 to %SW152
        - Description of Premium/Atrium-specific System Word %SW153
        - Description of Premium/Atrium-specific System Word %SW154
        - Description of Premium/Atrium-specific System Words %SW155 to **%SW167**
      - Quantum-specific System Words




# IST / DEEC / API

<b>%S0</b>  COLDSTART	Function	Cold start		
	Initial State	1 (1 cycle)		
	Platforms	<b>M340:</b> Yes <b>M580:</b> Yes	<b>Quantum:</b> Yes <b>Momentum Unity:</b> Yes	<b>Premium:</b> Yes <b>Atrium:</b> Yes
	<p>Normally on 0, this bit is set on 1 by:</p> <ul style="list-style-type: none"> <li>power restoral with loss of data (battery fault found)</li> <li>the user program</li> <li>the terminal</li> <li>a change of cartridge (PCMCIA on Premium and Quantum)</li> </ul> <p>This bit is set to 1 during the first complete restored cycle of the PLC either in RUN or in STOP mode. It is reset to 0 by the system at the end of the first complete cycle and before the outputs are updated.</p> <p>To detect the first scan of the PLC in Safe mode, this bit is set to 1. In Safe mode, this bit is not always needed, %S21 should be used instead. For details on operation, see:</p> <ul style="list-style-type: none"> <li><a href="#">Premium, Quantum</a></li> <li>or <a href="#">Modicon M3</a></li> <li>or <a href="#">BME P58 xx</a></li> </ul>			
<b>%S1</b>  WARMSTART	Function	Warm restart		
	Initial State	0		
	Platforms	<b>M340:</b> Yes <b>M580:</b> Yes	<b>Quantum:</b> Yes <sup>(1)</sup> <b>Momentum Unity:</b> Yes	<b>Premium:</b> Yes <b>Atrium:</b> Yes
	<p>(1) except for safety PLCs</p> <p>Normally at 0, this bit is set to 1 by:</p> <ul style="list-style-type: none"> <li>power is restored with data save,</li> <li>the user program,</li> <li>the terminal,</li> </ul> <p>It is reset to 0 by the system at the end of the first complete cycle and before the outputs are updated.</p> <p>This bit is not available on Quantum Safety PLCs.</p> <p>%S1 is not always set in the first scan of the PLC. If a signal set for every start of the PLC is needed, %S21 should be used instead.</p>			

# IST / DEEC / API

<b>%SW0</b> MASTPERIOD  <div style="border: 1px solid blue; padding: 5px; display: inline-block; color: blue;"> <i>Not the cyclic period</i> </div>	Function	Master task scanning period			
	Initial State	0			
	Platforms	M340: Yes M580: Yes	Quantum: Yes <sup>(1)</sup> Momentum Unity: Yes	Premium: Yes Atrium: Yes	
		(1) except for safety PLCs			
	<p>This word is used to modify the period of the master task via the user program or via the terminal.</p> <p>The period is expressed in ms (1...255 ms)</p> <p>%SW0=0 in cyclic operation.</p> <p>On a cold restart: it takes the value defined by the configuration.</p>				
<b>%SW1</b> FASTPERIOD	Function	FAST task scanning period			
	Initial State	0			
	Platforms	M340: Yes M580: Yes	Quantum: Yes <sup>(1)</sup> Momentum Unity: No	Premium: Yes Atrium: Yes	
		(1) except for safety PLCs			
	<p>This word is used to modify the period of the FAST task via the user program or via the terminal.</p> <p>The period is expressed in milliseconds (1...255 ms).</p> <p>On a cold restart, it takes the value defined by the configuration.</p> <p><b>NOTE:</b> This word is not available on Quantum safety PLCs.</p>				
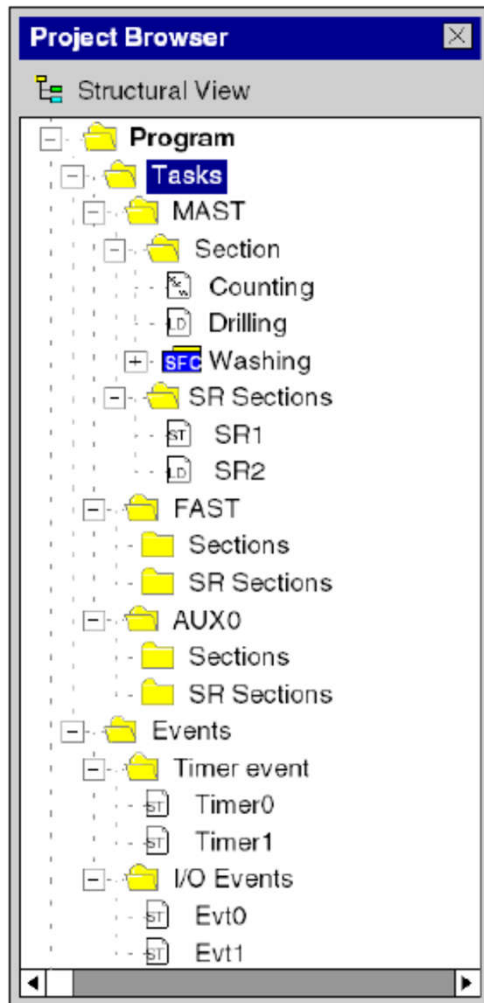
## Ladder diagram      Software Organization



*Unity - Project Browser*

A program can be built from:

Tasks, that are executed cyclically or periodically.

Tasks **MAST** / **FAST** / **AUX** are built from:

Sections

Subroutines

Event processing, that is carried out before all other tasks.

Event processing is built from:



Sections for processing time controlled events

Sections for processing hardware controlled events

# Ladder diagram      Software Organization
 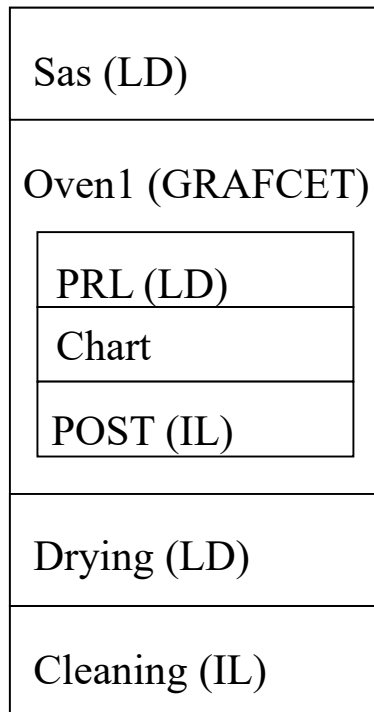
## MAST – Master Task Program

- Composed by **sections**
- Execution **Cyclic** or **Periodic**




**Cyclical** execution consists of stringing cycles together one after the other with no waiting time between the cycles.

In **Periodic** mode, you determine a specific time (period) in which the master task must be executed. If it is executed under this time, a waiting time is generated before the next cycle. If it is executed over this time, a control system indicates the overrun. If the overrun is too high, the PLC is stopped.

## Ladder diagram      Software Organization

### **FAST – Fast Task Program**

**Priority greater than MAST**

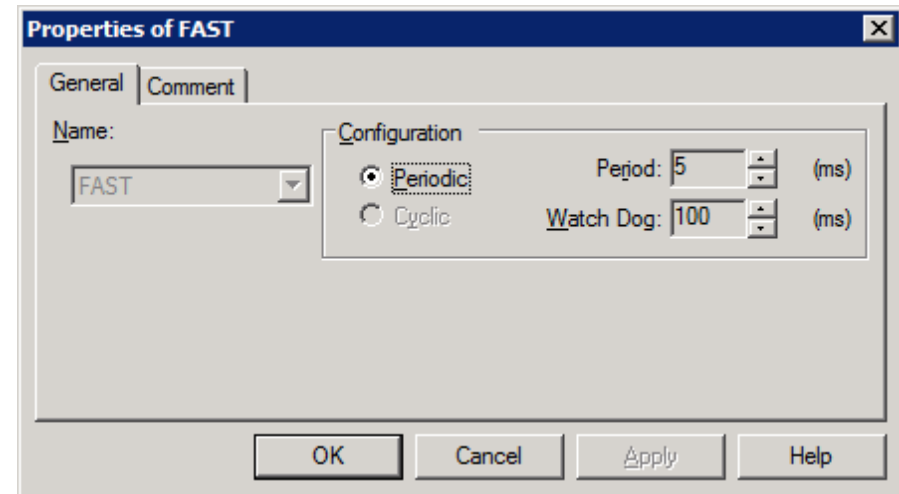

- Executed Periodically (1-255ms)
- Verified by a *Watchdog*, impacts on %S11
- %S31 *Enables* or *disables* a FAST
- %S33 gives the execution time for FAST

## Ladder diagram      **Software Organization**

**Event Processes** – Processes that can react to external changes  
(16 in the Micro 3722 EV0 to EV15)

**Priority greater than MAST and FAST!**

### Event Generators


- Inputs 0 to 3 in module 1, given transitions
- Counters
- Upon telegrams reception
- %S38 *Enables or disables* event processes

(also with MASKEVT() or UNMASKEVT())

# Ladder diagram Development tools

Each PLC has limitations in terms of connections

## Example:

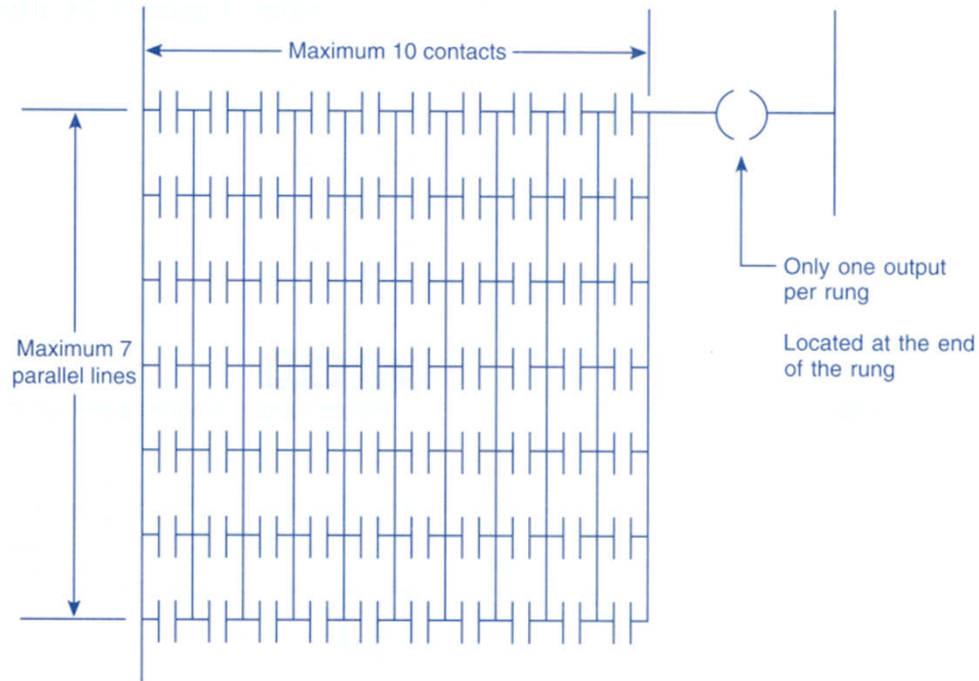


**Fig. 5-27**

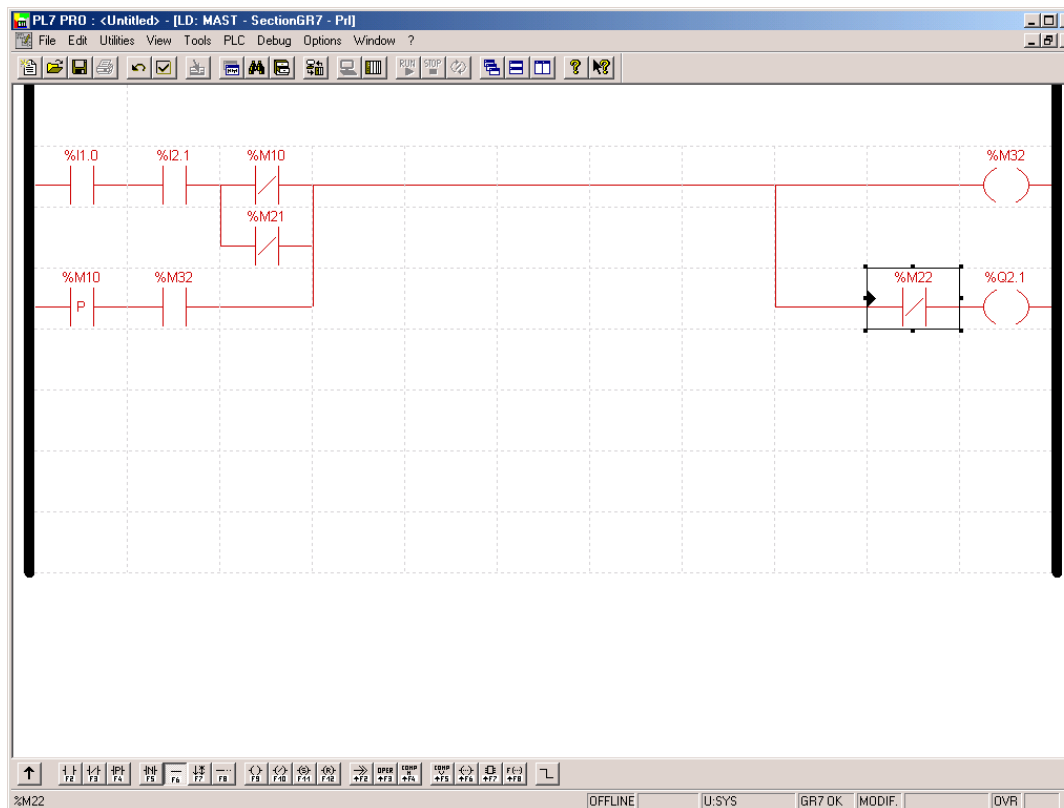Typical PLC matrix limitation diagram. The exact limitations are dependent on the particular type of PLC used. Programming more than the allowable series elements, parallel branches, or outputs will result in an error message being displayed.

## Ladder diagram **Development tools**

It is important to learn the potentialities and ...  
 the limitations of the developing tools,  
 i.e. ***STUDYING the manuals is a MUST.***





# Ladder diagram Development tools

Last but not least, *learn how to develop and debug programs*  
(and how to do some fine tuning).

1

2

3

4

Channel	Symbol	State	Error	Fallback	Function
0			ERR	STOP	ALARM
1		0	ERR		
2		F1	ERR		
3		F0	ERR		
4		F0	ERR		
5		0	ERR		
6		0	ERR		
7		0	ERR		
8		0	ERR	STOP	
9		0	ERR		
10		0	ERR		
11		0	ERR		
12		0	ERR		
13		0	ERR		
14		0	ERR		
15		0	ERR		

Channel 4 commands

Forcing

- F4 Force to 0
- F5 Force to 1
- F6 Unforce

Write

- F7 Set
- F8 Reset

# Ladder diagram Development tools

Last but not least, *learn how to develop and debug programs* (and how to do some fine tuning).

