

# Modeling and Automation of Industrial Processes

*Modelação e Automação de Processos Industriais / MAPI*

**GRAFCET**  
***(Sequential Function Chart, SFC) 3/3***

<http://www.isr.tecnico.ulisboa.pt/~jag/courses/mapi2122>

Prof. José Gaspar, rev. 2021/2022

## GRAFCET vs Ladder

**GRAFCET/SFC can be converted directly to ladder logic**

**Memory variables:**

Assign one Boolean variable to each step ( $s_i$ ) and transition ( $t_j$ )

**Code to run once:**

1. Initialize steps and transitions

Code to run at **every scan cycle:**

2. Check transitions and activate steps


3. Perform activities for steps

4. Enable transitions (jump to 2.)

Ref: [Hugh Jack 2008]

## GRAFCET/SFC can be converted directly to ladder logic

Ref: [Hugh Jack 2008]

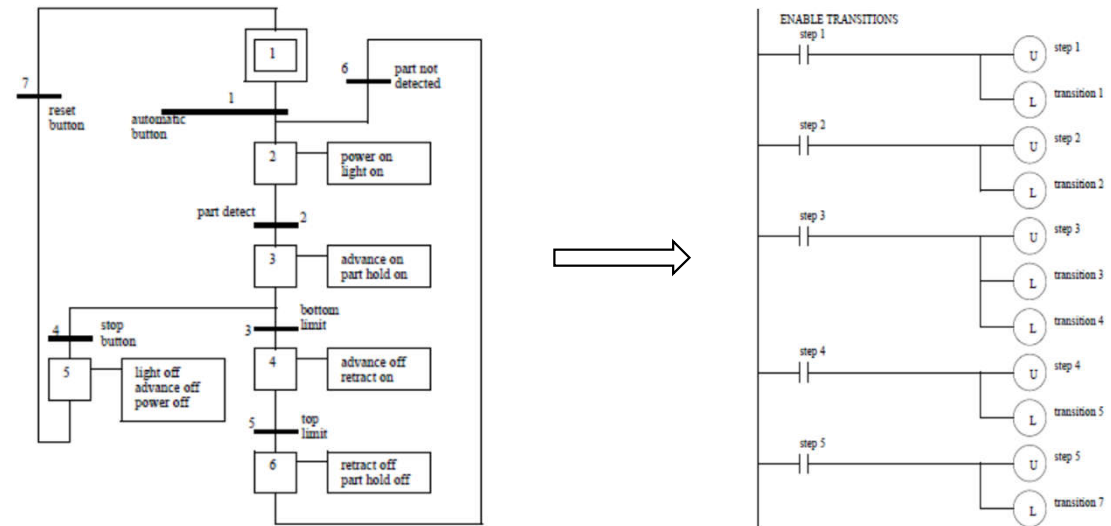

### Memory variables:

Assign one Boolean variable to each step ( $s_i$ ) and transition ( $t_j$ ).

Create memories to keep output values.

### Code to run once:


1. Initialize steps and transitions

### Code to run at every scan cycle:


2. Check transitions and activate steps
3. Perform activities for steps
4. Enable transitions (jump to 2.)

The complete program, four sections (to see separately in the next slides):


1. Initialize Steps and Transitions

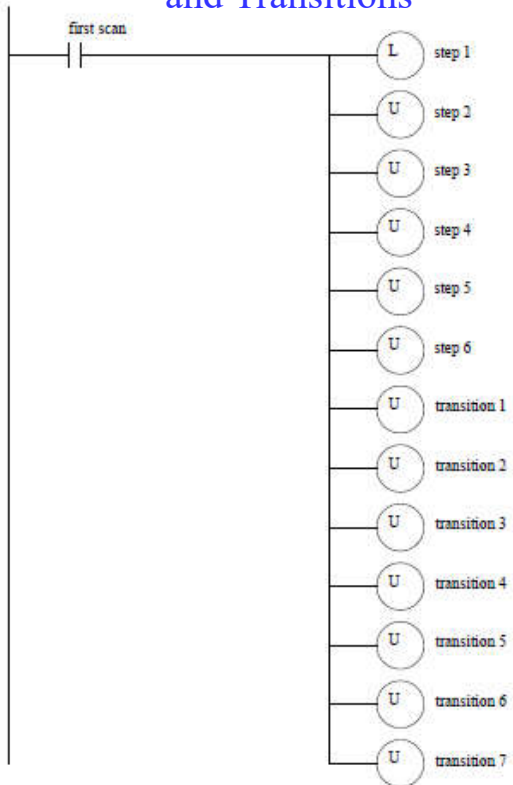


2. Check Transitions

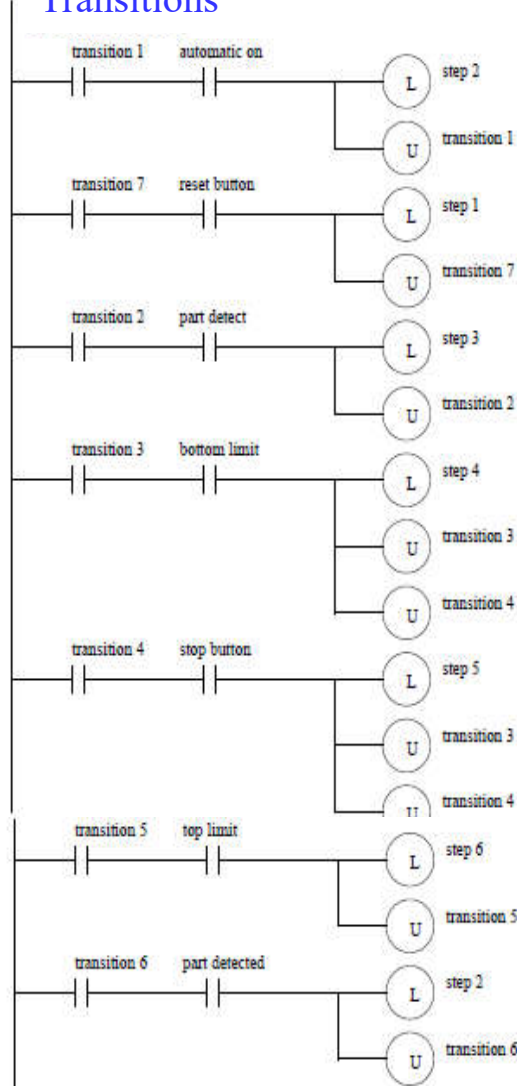



3. Perform Activities for Steps

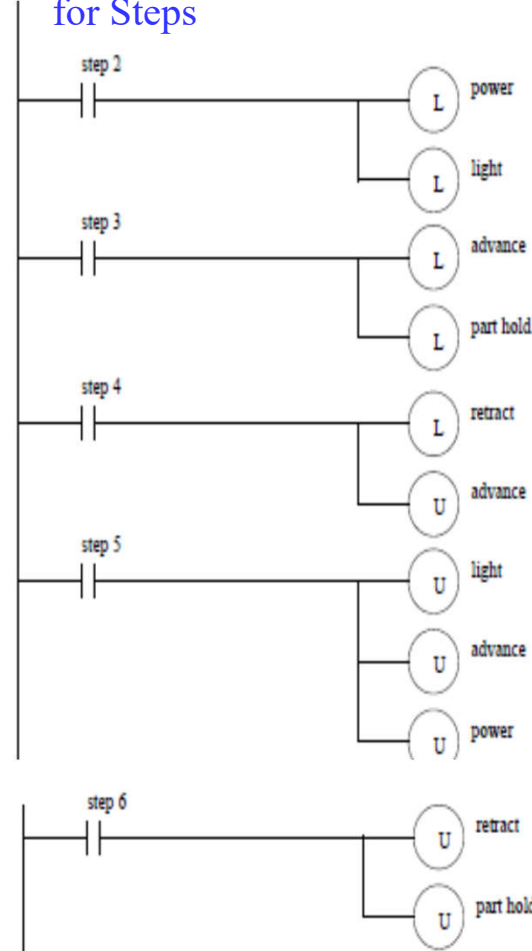

4. Enable Transitions

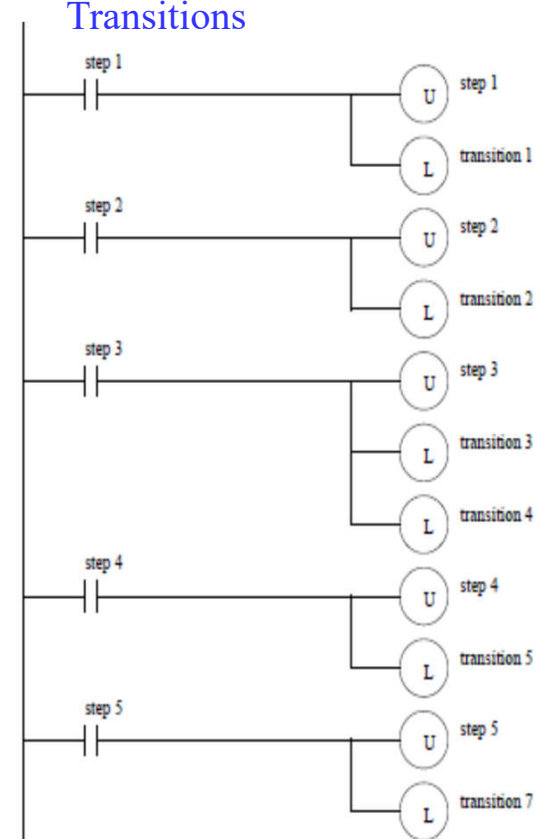

# 1. Initialize steps and transitions

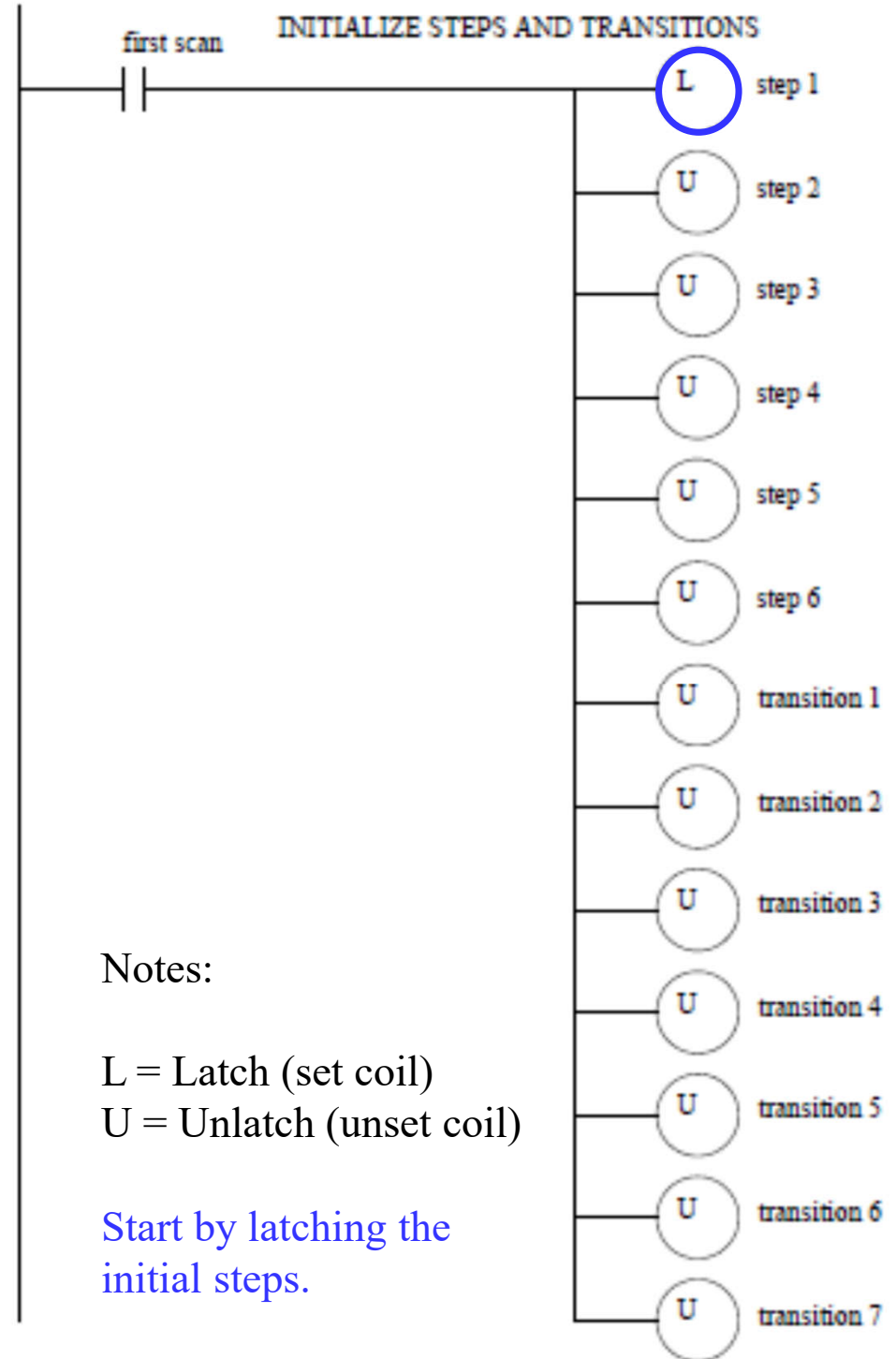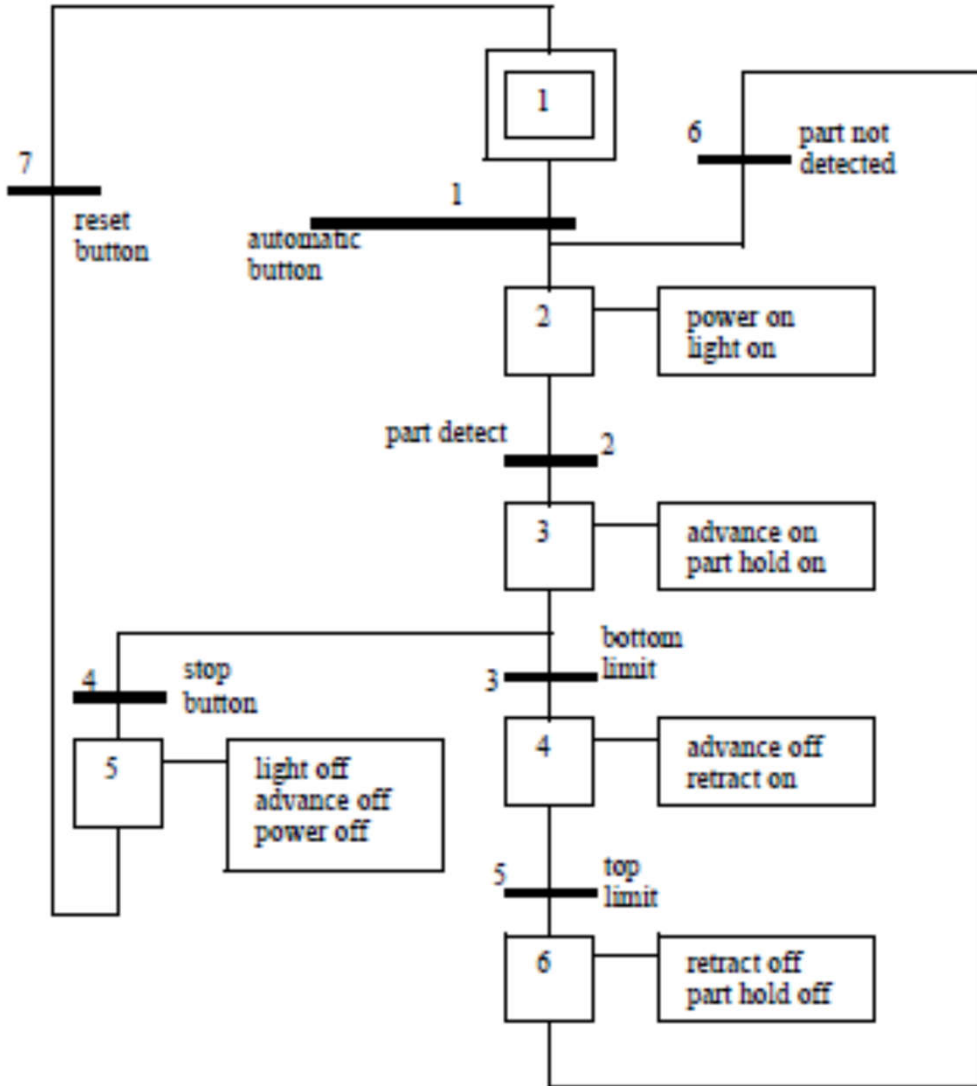



Notes:

L = Latch (set coil)



U = Unlatch (unset coil)

Start by latching the initial steps.



## 2. Check transitions & activate steps

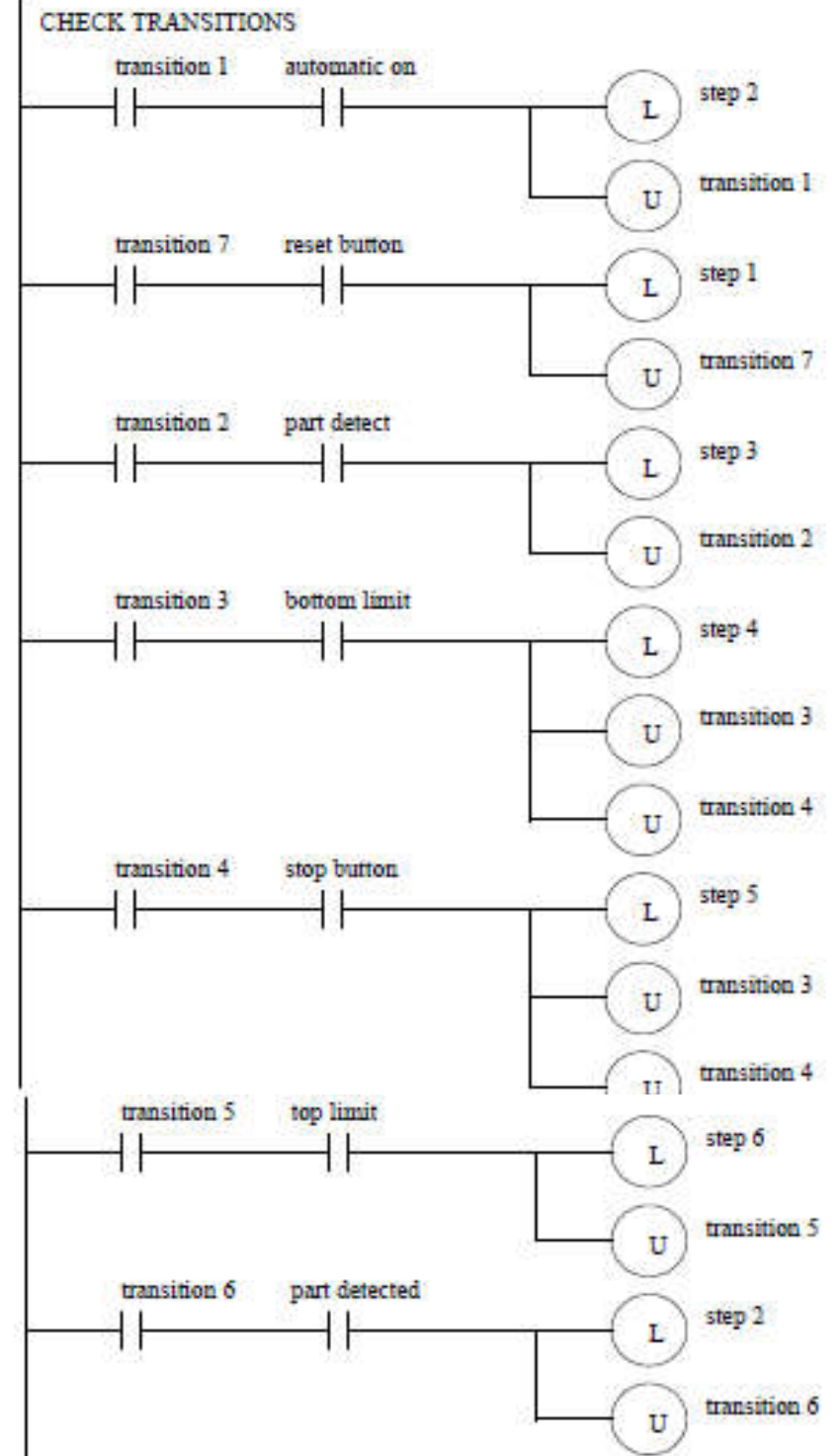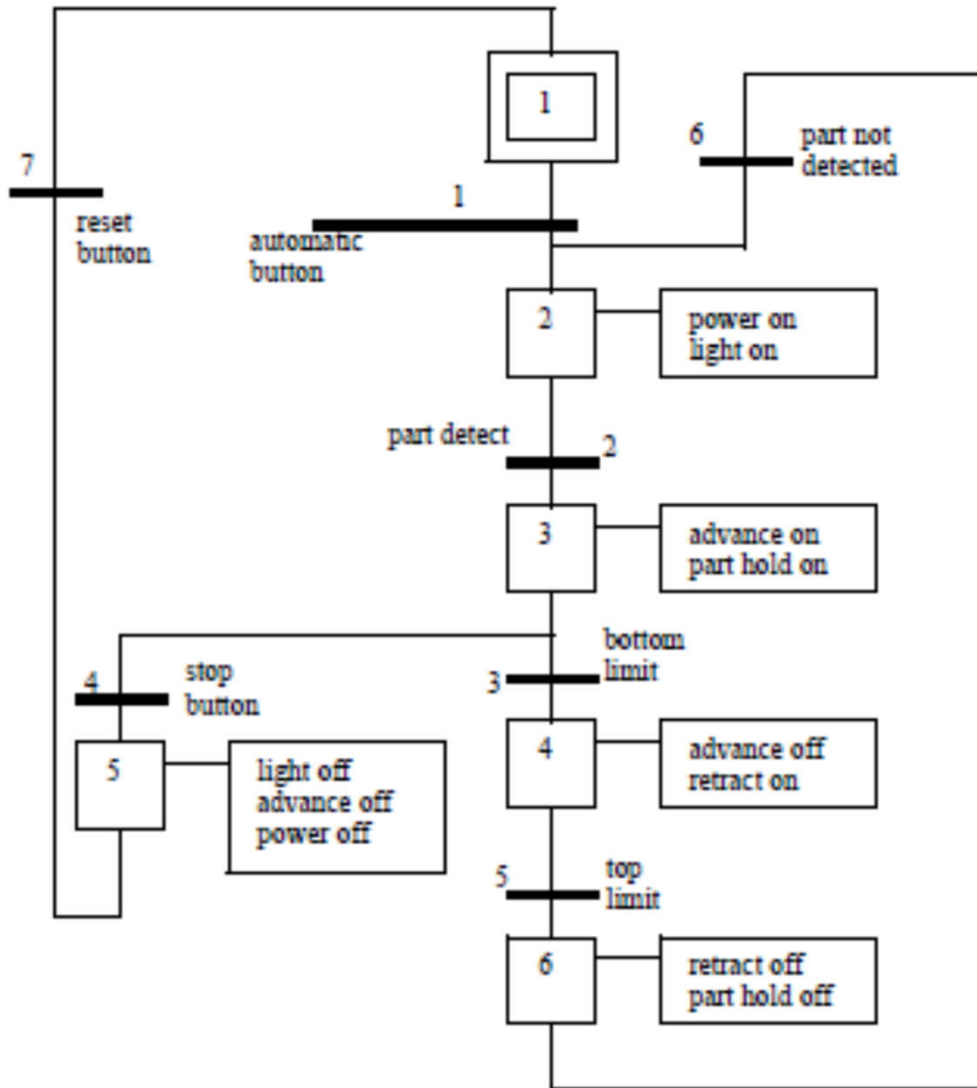

### 3. Perform activities for steps

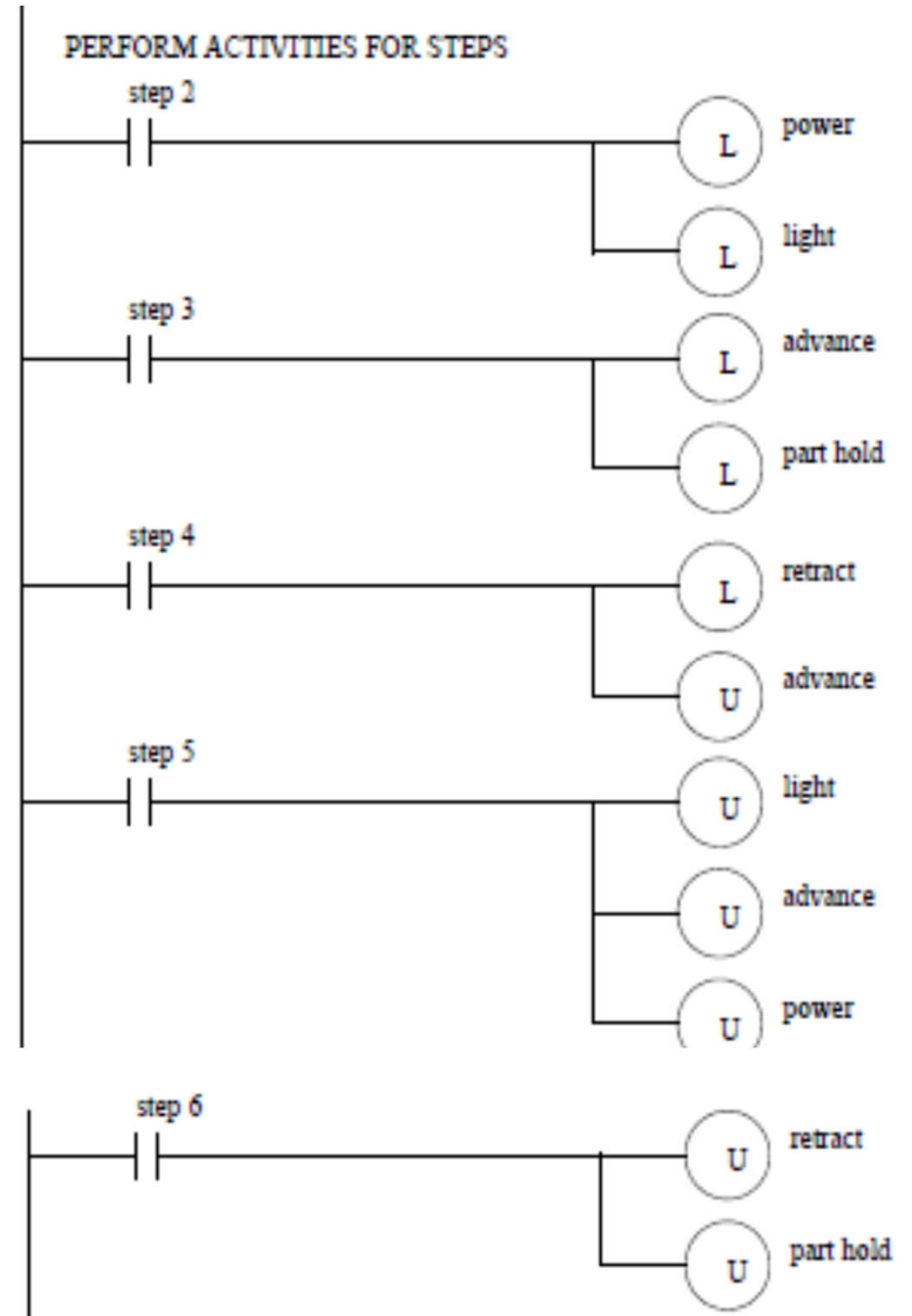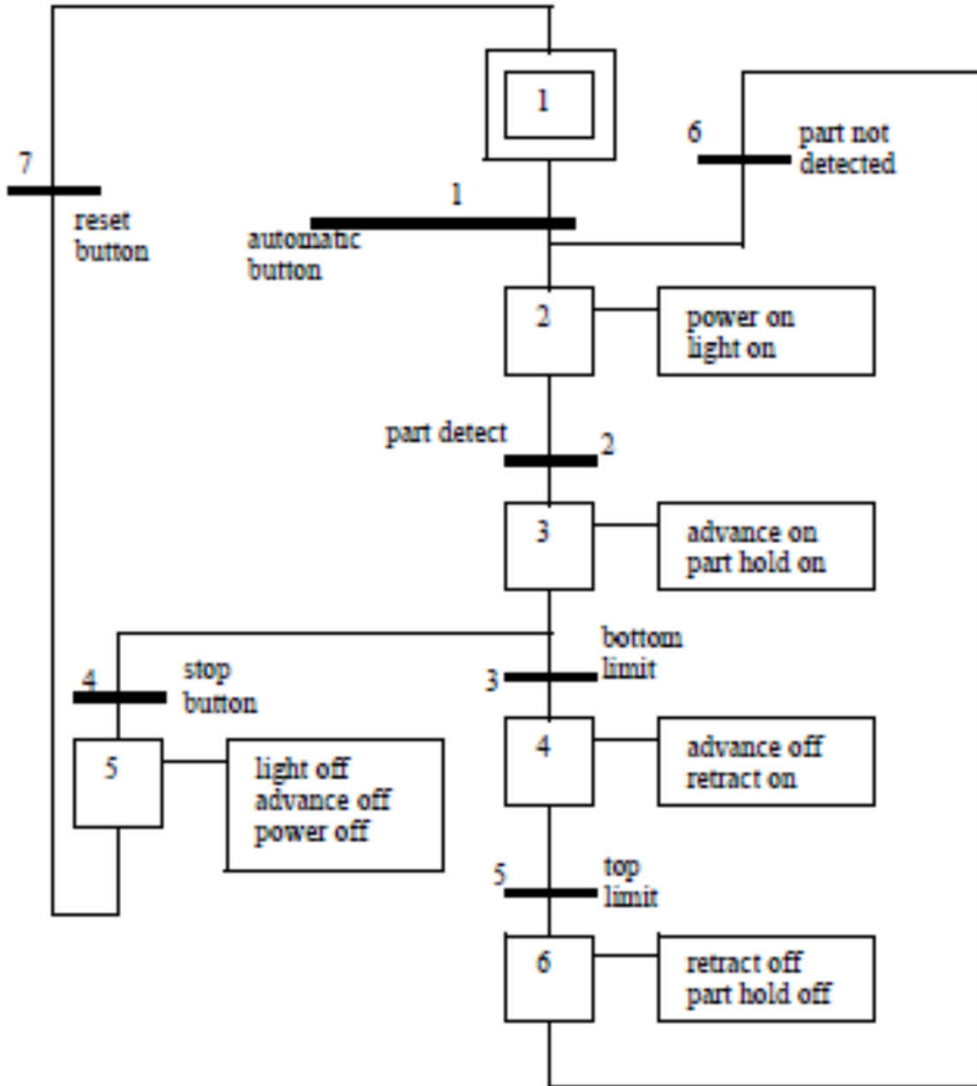

## 4. Enable transitions

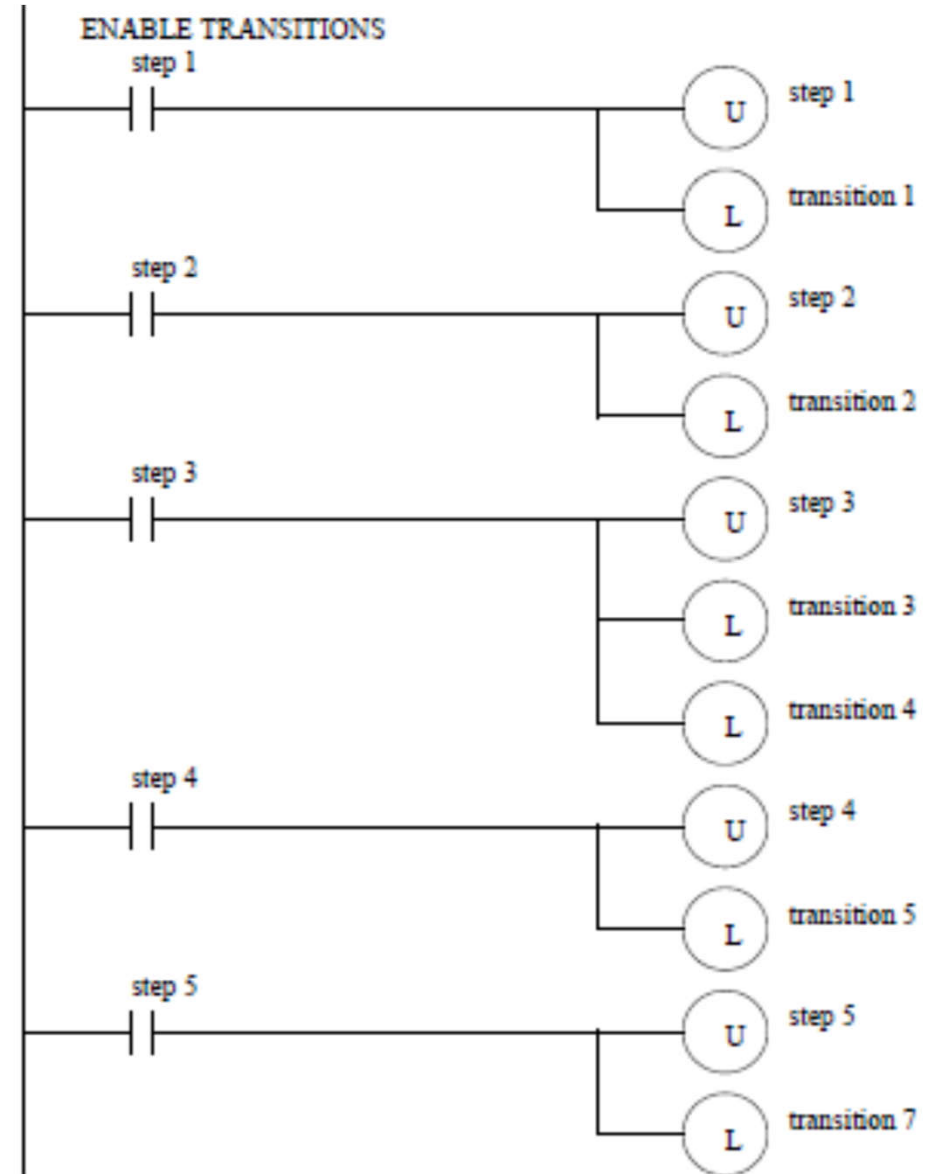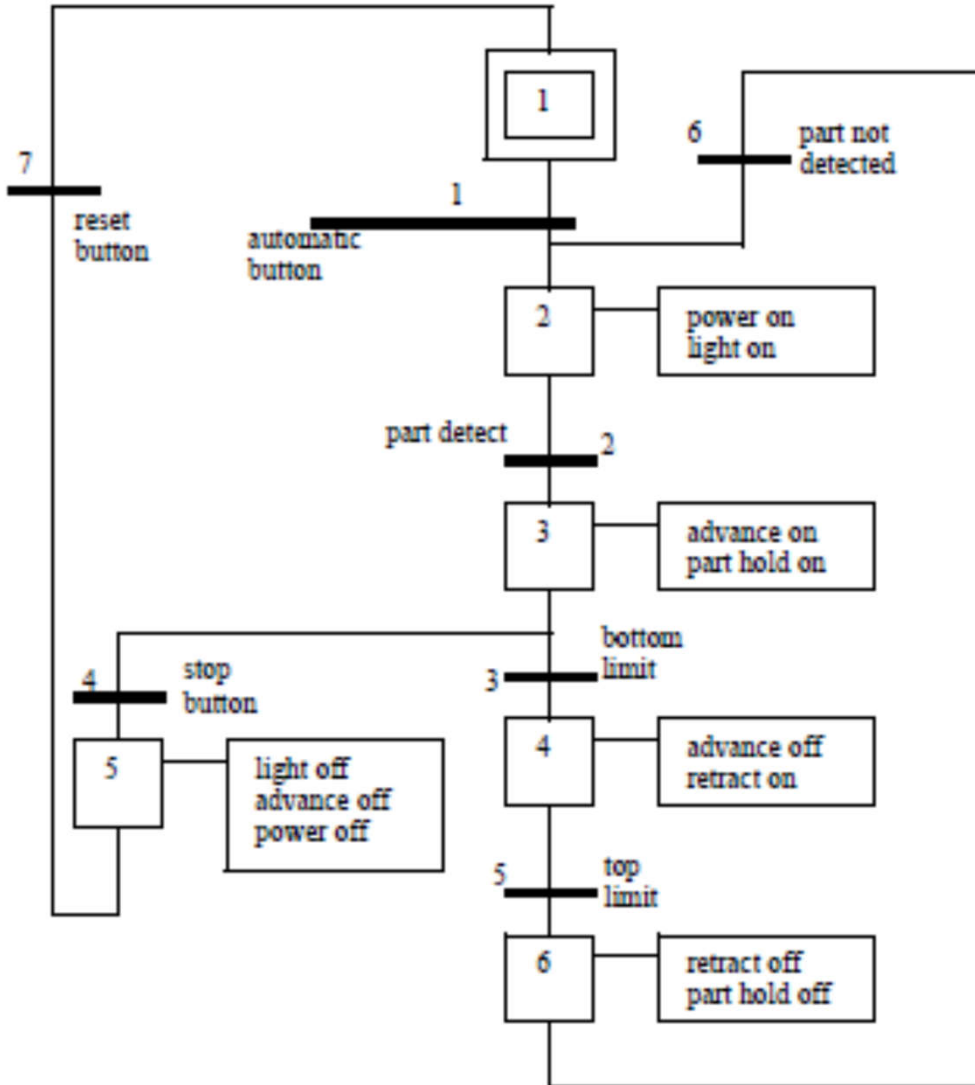


*Note: all active steps are made inactive.*





Discussion: not-keeping vs keeping steps active

1)

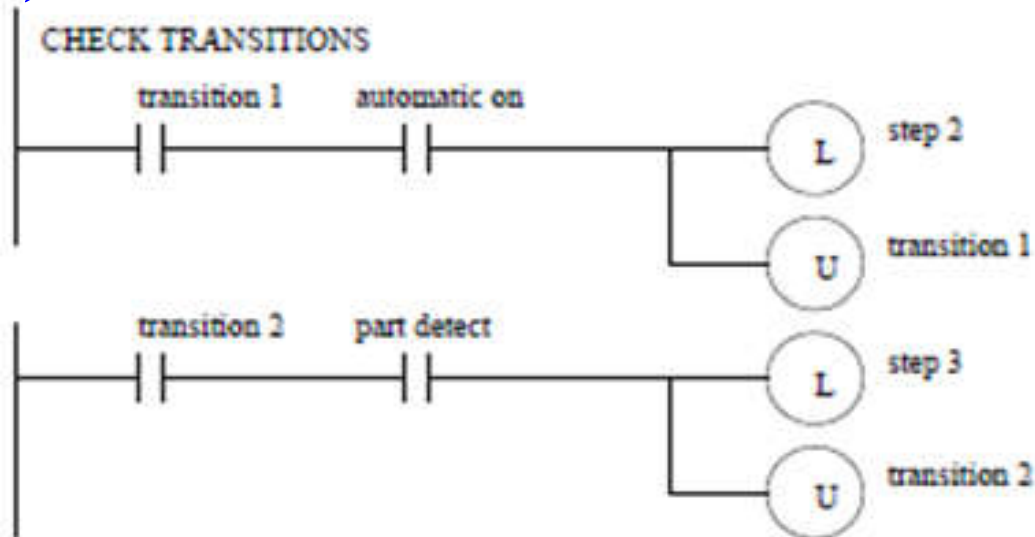


3)

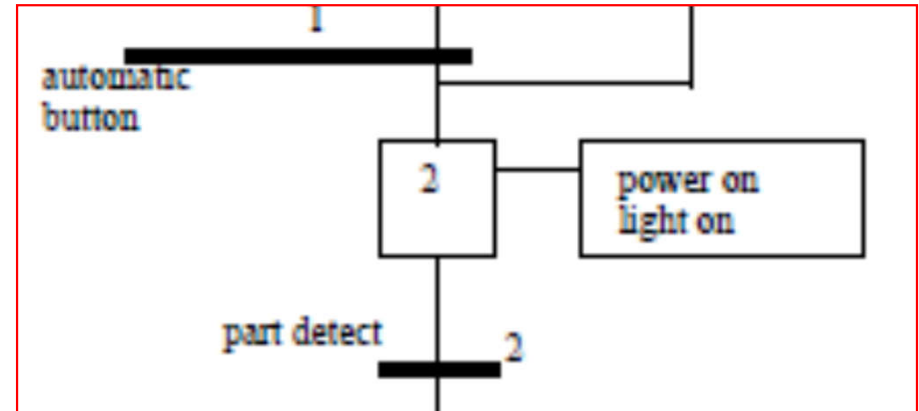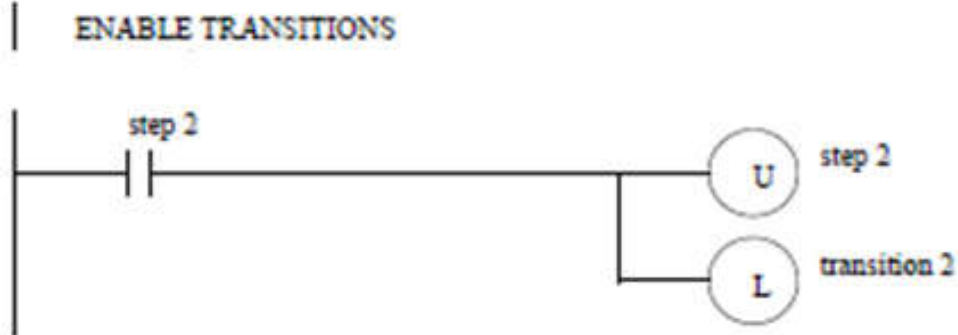

*Small part of the Grafset to analyse*

2)

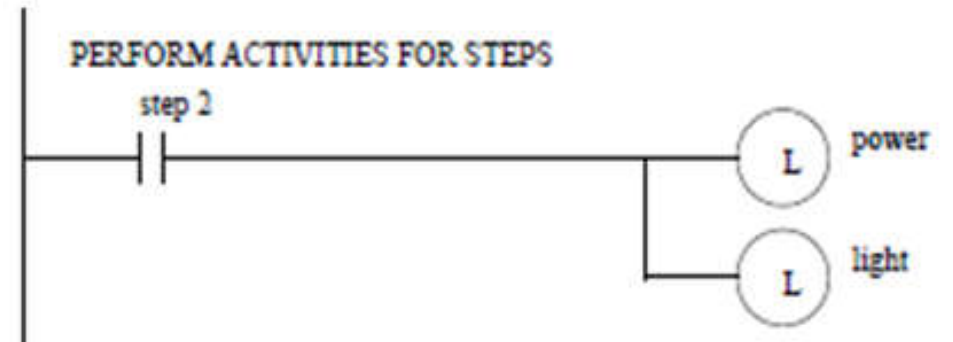

*If step2 is active in 1 then its work is done in 2 and it is going to be made inactive (unlatched) in 3.*

*Note: code parts 1, 2 and 3 run in a single scan cycle; latched outputs imply they have no spikes.*

*Note2: Unity Pro is not like this, step2 gets inactive only after transposing transitions2.*

## Homework challenges:

1. Convert the ladder code shown in the previous slides to a **structured text program**.

2. Consider simulating the ladder diagram, **ladder instructions one-by-one**, saving all variables:

- Steps (1..6)
- Transitions (1..6)
- Inputs (automatic button, part detect, ...)
- Outputs (power, light, advance, ...)

Confirm that:


- Step variables are active *at most one scan cycle*
- Outputs are set/unset (latched/unlatched) and therefore *do not need the steps being active all the time*.

## GRAFCET Practice Problem 1

Draw **one SFC** for one stamping press that can **advance and retract** when a **cycle button** is pushed, and then stop until the button is pushed again. The press has **limit switches** indicating stop advancing and stop retracting.


*Further study: discuss the advantages of using SFC as compared with using Ladder in this problem.*

*From [Hugh Jack 2008]*

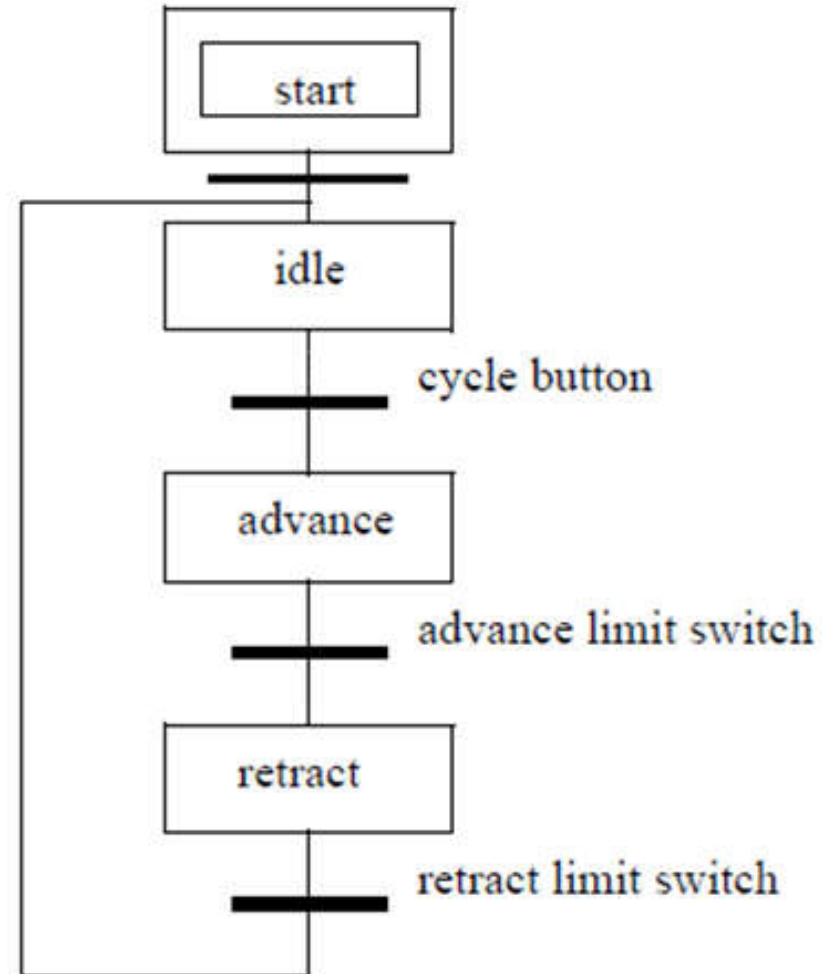
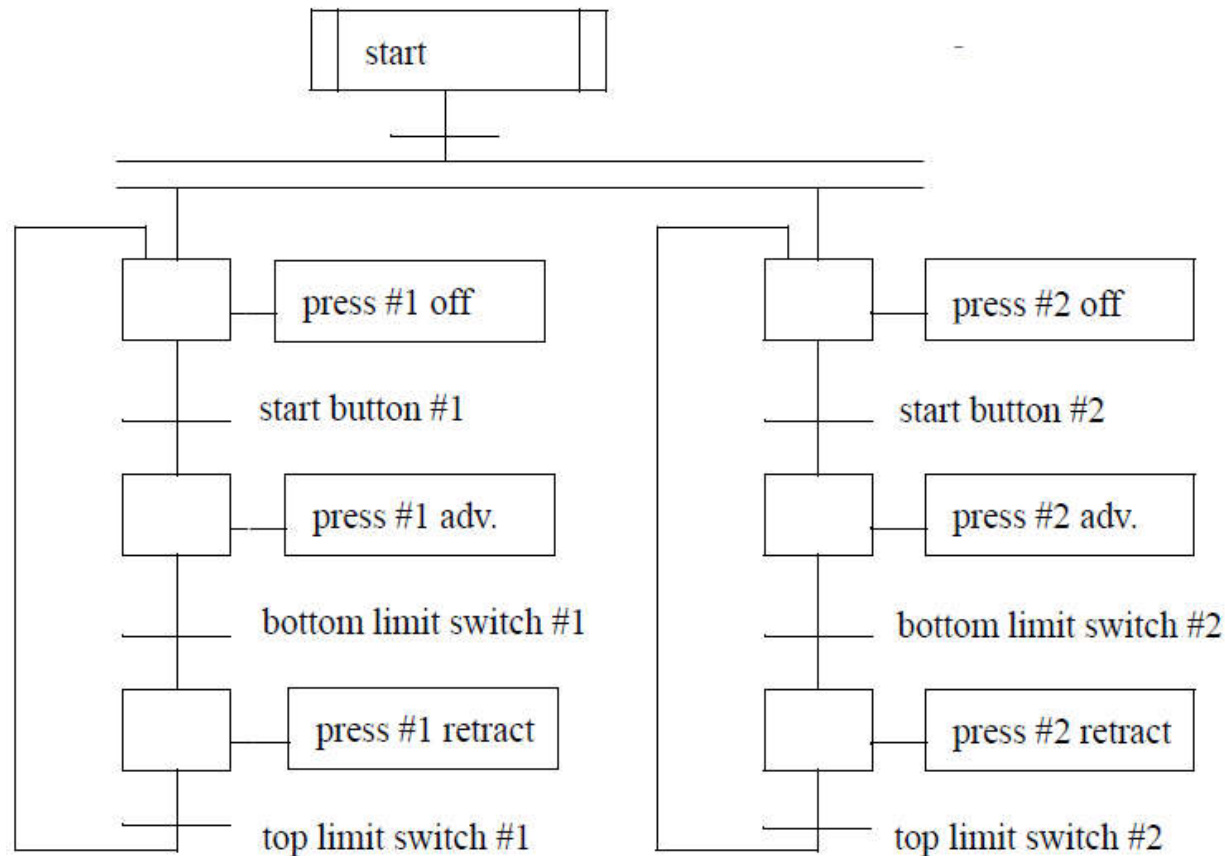
## GRAFCET Practice Problem 2

Develop **one SFC** for a two person assembly station. The station has **two presses** that may be used at the same time, **independently**. Each press has a cycle button that will start the advance of the press. A bottom limit switch will stop the advance, and the cylinder must then be retracted until a top limit switch is hit. The two presses are enabled only after a common starting procedure.



*From  
[Hugh  
Jack 2008]*

## GRAFCET Practice Problem 3

Design a garage door controller using an SFC. The behavior of the garage door controller is as follows:

- There is a **single button in the garage and a single button remote control**. When the button is pushed the door will move up or down.
- There are **top/bottom limit switches to stop** the motion of the door.
- If the button is pushed once while moving, the door will **stop**. A second push will start motion again in the **opposite direction**.
- There is a light beam across the bottom of the door. If the beam is cut while the door is closing the door will **stop and reverse**.
- There is a garage **light that will be on for 5 minutes** after the door opens or closes.

